

**Department of Electronics and Electrical Engineering
Indian Institute of Technology Guwahati**

EE101

Quiz#1


Problems

1. Consider the biasing circuit shown in the Fig. 1 where the transistor used has $\beta=20$ when working in the active region and $V_{CE,sat}=0.1$ V when it is in saturation.

(a) Give a logical argument (*No calculations!*) why the transistor cannot be in saturation. [1]

(b) Assuming that the transistor is working in the active region, calculate its bias point (i.e. V_{CE} , I_C , and I_B) [3]

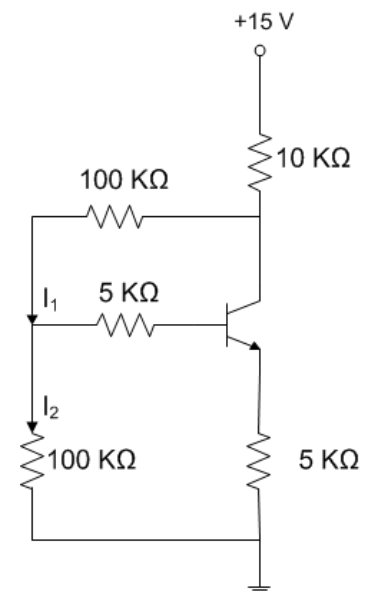(c) Confirm that the transistor is indeed in active region as assumed in part (b). [1]



2.

(a) The readings on the voltmeter and the ammeter (assumed ideal) were 14.4 V and 3.2 A respectively, when they were connected separately across terminals a and b of the linear network shown in Fig 2 (a). Draw the Thevenin's equivalent circuit and the Norton's equivalent circuit for the network showing the values of all necessary parameters. [1]

(b) Write and solve the mesh equations for the circuit shown in Figure 2(b) and calculate the total current through the 3Ω resistor. [2]

(c) Verify the result of Q 2(b) using nodal analysis. Take node 4 as the reference. [2]

