

# EE 101: Electrical Sciences

Tutorial-11, Nov. 17, 2017

## Question 1(Pre-tutorial question):

For the network shown below, find

- The resonant frequency  $\omega_0$
- $Z_{in}(j\omega_0)$

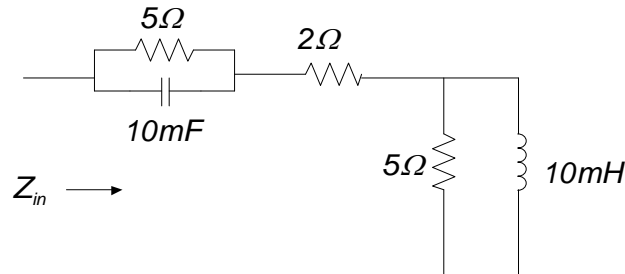


Figure 1

$$\text{Solution: } Z_{in} = \frac{-j500}{5\omega - j100} + 2 + \frac{j5\omega}{500 + j\omega}$$

$$(a) \text{ At resonance } I_m(Z_{in}) = 0$$

$$\Rightarrow \frac{-2500\omega_0}{25\omega_0^2 + 10^4} + \frac{2500\omega_0}{25 \times 10^4 + \omega_0^2} = 0$$

$$\Rightarrow -25 \times 10^4 - \omega_0^2 + 25\omega_0^2 + 10^4 = 0$$

$$\Rightarrow \omega_0^2 = 10^4 \Rightarrow \omega_0 = 100 \text{ rad/s}$$

$$(b) Z_{in}(j\omega_0) = \text{Re}\{Z_{in}(j\omega_0)\} = 2 + \frac{5 \times 10^4}{25\omega_0^2 + 10^4} + \frac{5\omega_0^2}{\omega_0^2 + 500}$$

$$= 2 + \frac{5}{26} + \frac{5}{26} = 2.385 \Omega$$

**Question 2:** A series resonant network consists of a  $50\Omega$  resistor, a  $4\text{mH}$  and a  $0.1\mu\text{F}$  capacitor. Calculate the values of:

- $\omega_0$
- $f_0$
- $Q_0$
- Bandwidth
- $\omega_1$
- $\omega_2$
- $Z_{in}$  at  $45 \text{ krad/s}$  and
- The ratio of magnitudes of capacitor impedance to resistor at  $45 \text{ krad/s}$ .

$$\text{Solution: } \omega_0 = \frac{1}{\sqrt{LC}} = 50 \text{ krad/s}$$

$$f_0 = \frac{\omega_0}{2\pi} = 7.96 \text{ kHz}$$

$$Q_0 = \omega_0 L / R = 4$$

$$\text{Bandwidth } B = \frac{\omega_0}{Q_0} = 12.5 \text{krad / s}$$

$$\omega_2, \omega_1 = \omega_0 \left[ 1 + \left( \frac{1}{2Q_0} \right)^2 \mp \frac{1}{2Q_0} \right]$$

$$\omega_2 = 56.65 \text{krad / s},$$

$$\omega_1 = 44.15 \text{krad / s}$$

$$Z_{in} = R_s + j \left( \omega L_s - \frac{1}{\omega C_s} \right)$$

$$\text{At } \omega = 45 \text{krad / s}, \quad Z_{in} = 65.4 \angle -40.2^\circ$$

$$\frac{Z_c}{R} = \frac{1}{\omega CR} = \frac{1}{45 \times 10^{-4} \times 50} = 4.44$$

**Question 3:** An AC-coupled amplifier is shown below.

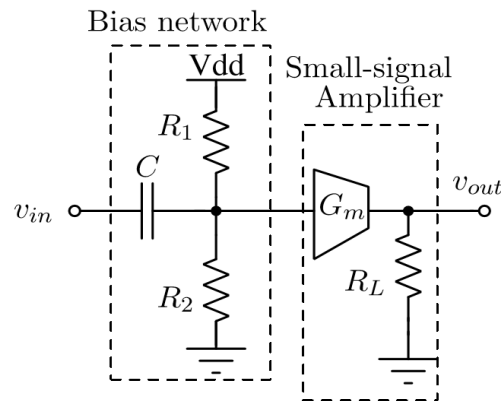


Figure 2: An AC-coupled amplifier

This circuit can be seen as a cascade of two networks. Assuming an ideal transconductor, derive the (frequency-dependent) transfer function of the above amplifier.

**Solution:**

Small signal voltage gain of the amplifier,  $= G_m R_L$

The resistors  $R_1$  and  $R_2$  come in parallel in the small-signal equivalent circuit. The parallel combination of the  $R_1$  and  $R_2$  forms a high-pass filter with the capacitor  $C$ .

Transfer function of this high-pass filter network is:  $\frac{j\omega RC}{1+j\omega RC}$

Where,  $R = \frac{R_1 R_2}{R_1 + R_2}$

Overall transfer function  $= \frac{j\omega RC}{1+j\omega RC} \times G_m R_L$