

INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI
DEPARTMENT OF ELECTRONICS & ELECTRICAL ENGINEERING
EE 101: Electrical Sciences
Tutorial-11

(First question is the **Pre-Tutorial Assignment problem** to be done in the space provided.)

Name:

Roll No.:

Tutorial Group:

Question 1: For the network shown below, find

- (a) The resonant frequency ω_0
- (b) $Z_{in}(j\omega_0)$

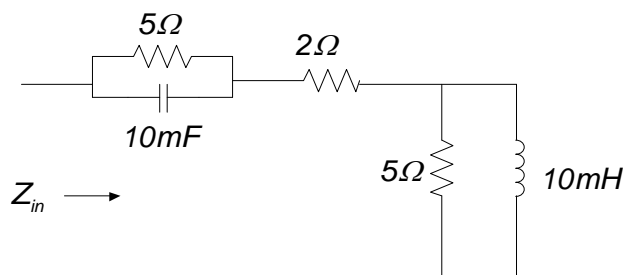


Figure 1

Question 2: A series resonant network consists of a 50Ω resistor, a $4mH$ and a $0.1\mu F$ capacitor. Calculate the values of:

- (a) ω_0
- (b) f_0
- (c) Q_0
- (d) Bandwidth
- (e) ω_1
- (f) ω_2
- (g) Z_{in} at 45 krad/s and
- (h) The ratio of magnitudes of capacitor impedance to resistor at 45krad/s .

Question 3: An AC-coupled amplifier is shown below.

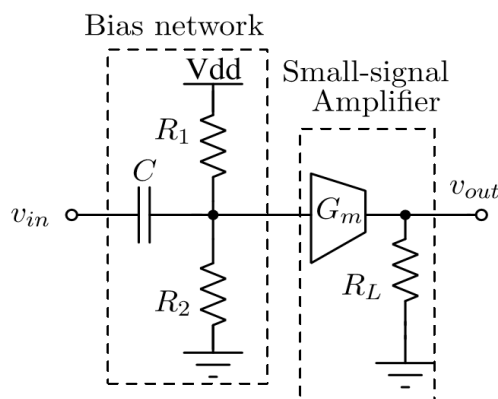


Figure 2: An AC-coupled amplifier

This circuit can be seen as a cascade of two networks. Assuming an ideal transconductor, derive the (frequency-dependent) transfer function of the above amplifier.