

Tutorial-7

Question-1(Pre Tutorial Question): Three star connected impedances $Z_1 = 20 + j37.7 \Omega$ per phase are in parallel with three delta connected impedances $Z_2 = 30 - j159.3 \Omega$ per phase. The line voltage is **398 volts rms**. Find the line currents, power factor, power and reactive volt ampere taken by the combination. **(Hint: Convert impedances connected in delta into their equivalent star connected configuration. For a balanced network, $Z_{Star} = \frac{Z_{Delta}}{3}$)**

Solution: Converting delta connected load to star connected load $Z_2' = \frac{Z_2}{3} = \frac{30 - j159.3}{3} = 10 - j53.1$

$$\text{Total impedance per phase} = \frac{Z_1 Z_2'}{Z_1 + Z_2'} = \frac{(20 + j37.7)(10 - j53.1)}{30 - j15.4} = 68.38 \angle 9.89^\circ \Omega$$

a) Line current $= \frac{398}{\sqrt{3}} \times \frac{1}{68.38 \angle 9.89^\circ} = 3.36 \angle -9.89^\circ \text{ A}$

b) P.F. $= \cos 9.89^\circ = 0.985$ lagging

c) Total power $= \sqrt{3} V_L I_L^* = \sqrt{3} \times 398 \times 3.36 \angle 9.89^\circ$

Reactive VA = **397.83 VAR**

Question-2: In the balanced three phase system of Fig. 1, let $Z_P = 12 + j5 \Omega$ and $I_{bB} = 20 \angle 0^\circ \text{ A rms}$ with (+) phase sequence. If the source is operating with a power factor of 0.935, find (a) R_w (b) V_{bn} (c) V_{AB} (d) complex power supplied by the source.


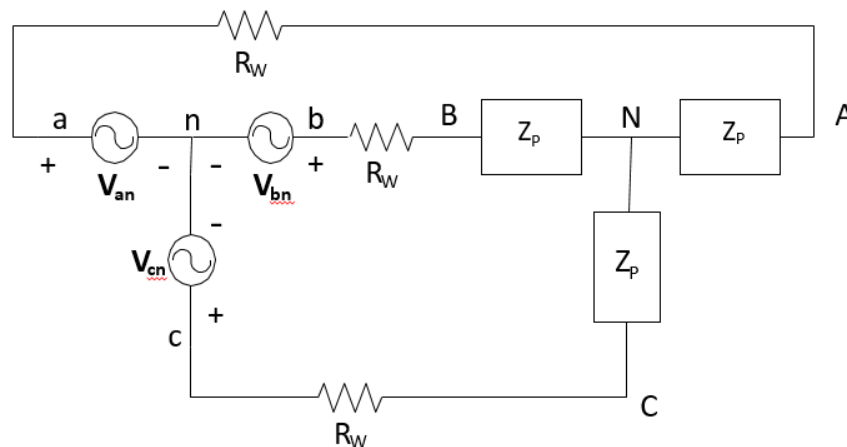


Figure -1


Solution:

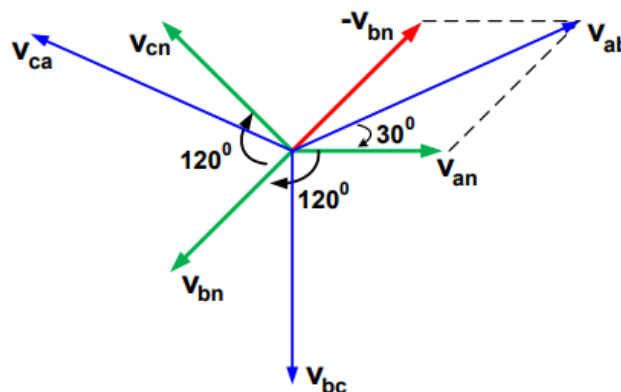

(Phase and Line voltages for a balanced star connected 3-Ø circuit)

Tutorial-7

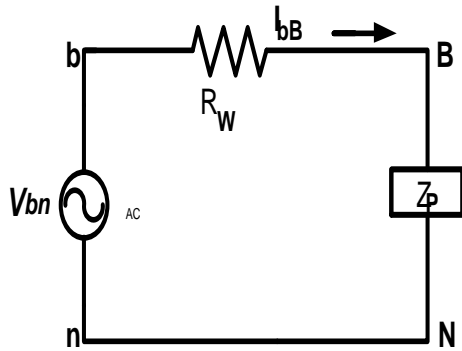a) Considering only phase b-B, the equivalent circuit is:



b) n-N is the virtual neutral line

$$Z_P = 12 + j5 \, \Omega$$

$$I_{bB} = 20 \angle 0^\circ \, \text{A}$$

Source power factor is 0.935 which corresponds to an angle of 20.77° ($\cos^{-1} 0.935$)

P.F. angle = 20.77° , Power factor angle is the angle of load.

As this is the source power factor, this angle corresponds to the angle of load Z_P and line resistance R_W .

$$\text{So, } \tan^{-1} \left(\frac{5}{12 + R_W} \right) = 20.77^\circ \Rightarrow \frac{5}{12 + R_W} = 0.38 \Rightarrow 13.18 = 12 + R_W \Rightarrow R_W = 1.18 \, \Omega$$

$$\text{b) } V_{bn} = I_{bB} (Z_P + R_W) = 20 \angle 0^\circ (12 + j5 + 1.18) = 20 (13.18 + j5) = 263.6 + j100 = 282 \angle 20.77^\circ \, \text{V.}$$

Since, for a balanced star connected 3-phase circuit,


$$|V_{line}| = \sqrt{3} |V_{phase}| \text{ and it leads corresponding phase voltage by } 30^\circ.$$

$$V_{BC} = \sqrt{3} \times 282 \angle (20.77^\circ + 30^\circ) = 488.44 \angle 50.77^\circ \, \text{V}$$

$$\text{c) } V_{AB} = 488.44 \angle 170.77^\circ \, \text{V}$$

$$\text{d) Total complex power supplied by the source} = \sqrt{3} V_L I_L = 16.92 \, \text{KVA}$$

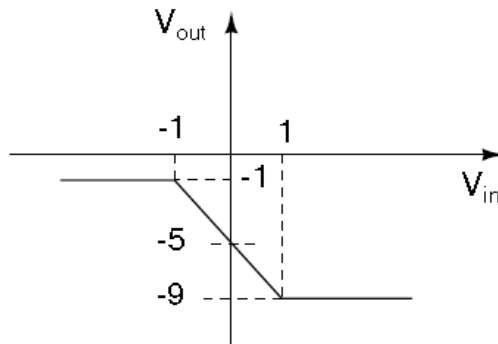
Question-3: Transfer characteristics of a circuit are shown below.




Draw the output (as a function of time) of this circuit for the following inputs: $5 + \cos \omega t$, $0.2 \cos \omega t$, $1.2 \cos \omega t$

Tutorial-7


Solution:

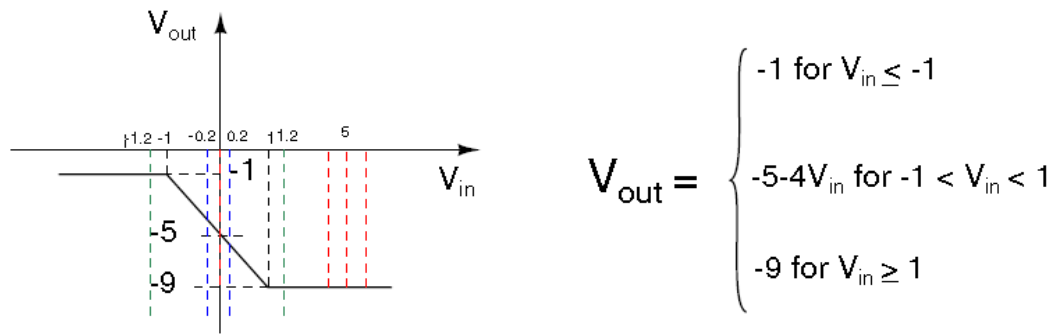

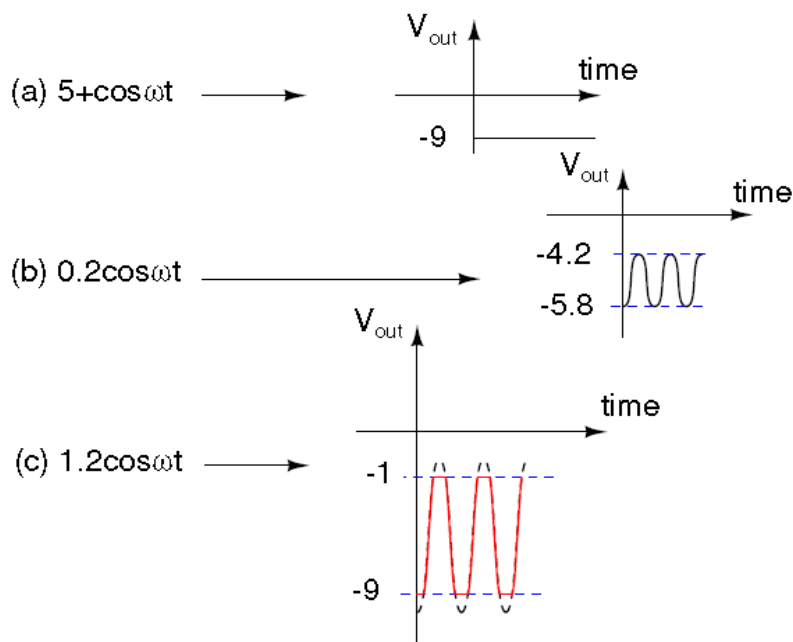
Inputs: $5 + \cos \omega t$, $0.2 \cos \omega t$, $1.2 \cos \omega t$




Question-4:

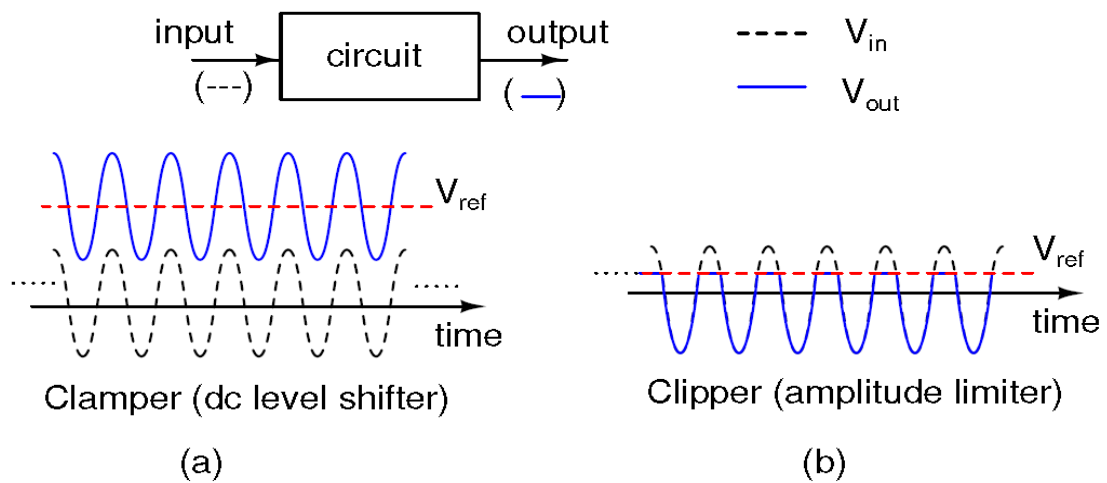

Tutorial-7

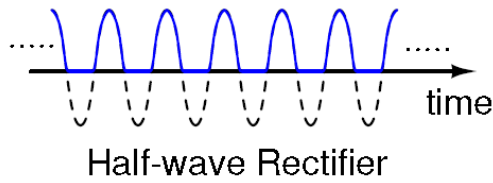

(c)

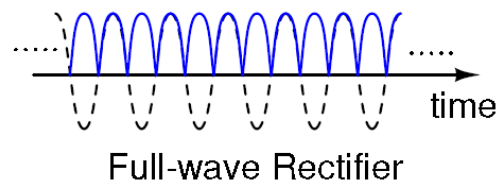

(d)

Draw the transfer (output amplitude w.r.t. input amplitude) characteristics of the above circuits.

Solution:

<p style="text-align: center;">Clamper (dc level shifter)</p> <p style="text-align: center;">(a)</p>	$V_{out} = V_{in} + V_{ref}$	
<p style="text-align: center;">Clipper (amplitude limiter)</p> <p style="text-align: center;">(b)</p>	$V_{out} = \begin{cases} V_{in} & \text{for } V_{in} < V_{ref} \\ V_{ref} & \text{for } V_{in} > V_{ref} \end{cases}$	
<p style="text-align: center;">Half-wave Rectifier</p> <p style="text-align: center;">(c)</p>	$V_{out} = \begin{cases} V_{in} & \text{for } V_{in} \geq 0 \\ 0 & \text{for } V_{in} < 0 \end{cases}$	
<p style="text-align: center;">Full-wave Rectifier</p> <p style="text-align: center;">(d)</p>	$V_{out} = \begin{cases} V_{in} & \text{for } V_{in} \geq 0 \\ -V_{in} & \text{for } V_{in} < 0 \end{cases}$	


Tutorial-7

Question-5:


A voltage controlled resistor R_{AB} has the following characteristics.

$$R_{AB} = \begin{cases} \infty & \text{for } V_{AB} < 0 \\ 0 & \text{for } V_{AB} \geq 0 \end{cases}$$

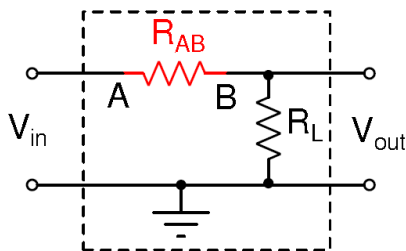Plot the transfer characteristics of the following circuits. R_L is a normal resistor.



(a)

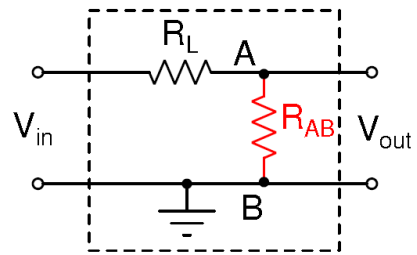

(b)

Solution:

Circuit	<p style="text-align: center;">(a)</p>	<p style="text-align: center;">(b)</p>
Math. Relation	$V_{out} = \{R_L / (R_L + R_{AB})\} V_{in}$ $V_{out} = \begin{cases} V_{in} & \text{for all } V_{in} \geq 0 \\ 0 & \text{for all } V_{in} < 0 \end{cases}$	$V_{out} = \{R_{AB} / (R_L + R_{AB})\} V_{in}$ $V_{out} = \begin{cases} 0 & \text{for all } V_{in} \geq 0 \\ V_{in} & \text{for all } V_{in} < 0 \end{cases}$
Transfer Characteristics		