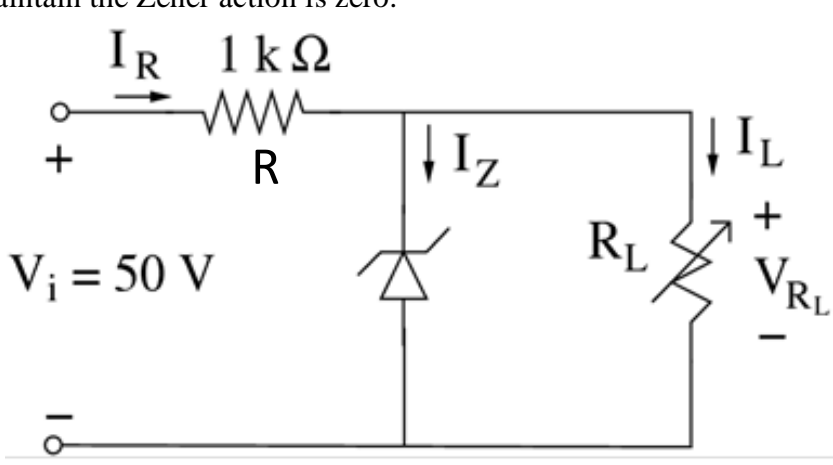


EE101
Tutorial-1 (07 Aug 2014)

Q1.	<p>A Si diode operating at 27°C having the ideality factor of 1 is forward biased by a voltage of 0.8 V. If the operating temperature changes to 47°C, what voltage should now be applied across the diode so that the current through the diode remains constant?</p> <p>[Given that Boltzmann's constant $k = 1.38 \times 10^{-23} \text{ J/K}$ and the magnitude of electronic charge $q = 1.6 \times 10^{-19} \text{ C}$]</p>
Q2.	<p>For the network shown below, determine the range of R_L and I_L that will result in the load voltage V_{R_L} being maintained at 10 V. The Zener diode in the circuit has a breakdown voltage of 10 V and the maximum wattage rating of 320 mW. Assume that the minimum current required to maintain the Zener action is zero.</p> 
Q3.	<p>For the circuit shown below, sketch the voltage developed across the resistance R_3 and also determine the dc voltage available at R_3. Assume that the diodes are ideal.</p> 