

EE 101 Tutorial Problems 2
(14 August 2014)

Q 1. For the circuit shown in Figure 1, compute the voltage V_0 . Use nodal analysis.

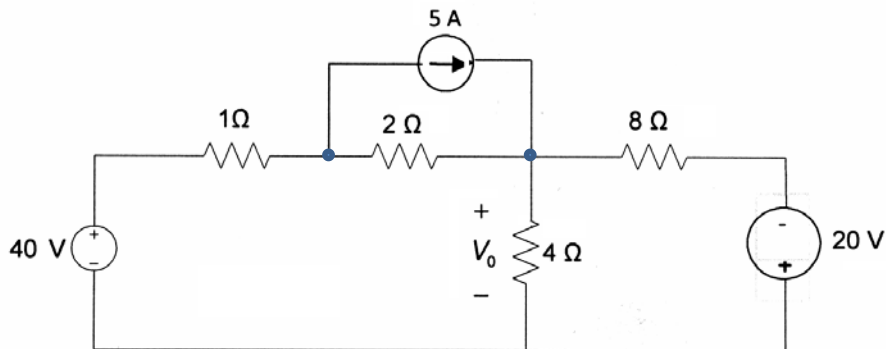


Figure 1

Q 2. Use mesh analysis on the circuit shown in Figure 2 to find the power being supplied by the dependent voltage source.

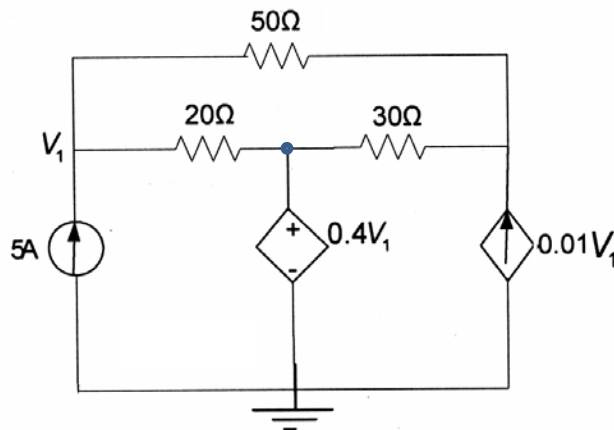


Figure 2

Q 3. Figure 3a shows a circuit supplied by a practical voltage source V . The characteristic of the source (terminal voltage v_t vs output current i_o) is shown in Figure 3b. Calculate voltages v_2 , v_3 and currents i_1 , i_2 , i_3 , and i_4 , whose directions are indicated in the figure arbitrarily.

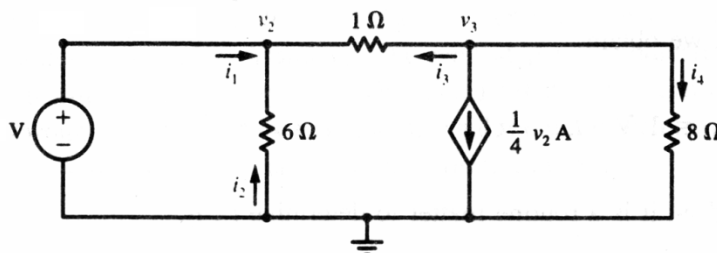


Figure 3a

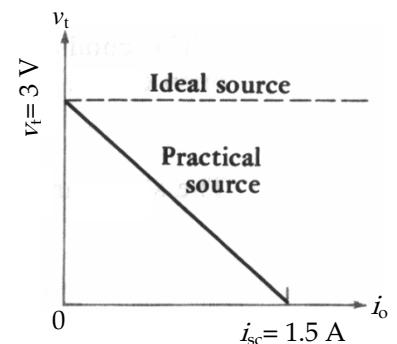


Figure 3b