

Department of Electronics and Electrical Engineering
Indian Institute of Technology Guwahati
EE101 Quiz1 Problem and Solution

1. Consider the biasing circuit shown in the Fig. 1 where the transistor used has $\beta=20$ when working in the active region and $V_{CE,sat}=0.1$ V when it is in saturation.

(a) Give a logical argument (*No calculations!*) why the transistor cannot be in saturation.


[1]

(b) Assuming that the transistor is working in the active region, calculate its bias point (i.e. V_{CE} , I_C , and I_B).

[3]

(c) Confirm that the transistor is indeed in active region as assumed in part (b).

[1]

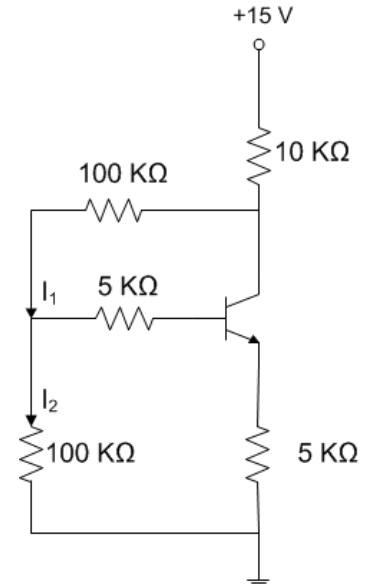

Solution

(a) I_B must be +ive (i.e. going into the base) for a transistor in saturation. Therefore I_2 must also be +ive. This implies that I_1 must also be +ive. However, if that is the case then the B-C junction must be reverse-biased so the transistor cannot be in saturation. **(1 Mark)**

(b) Assuming transistor is in the active region, $I_C=20I_B$ and $I_E=21I_B$

$$V_E=105I_B \quad V_B=0.7+105I_B \quad I_2=0.01(0.7+105I_B+5I_B)=0.007+1.1I_B \quad I_1=0.007+2.1I_B$$

$$\text{This gives } V_C=V_B+5I_B+100I_1=1.4+320I_B$$

$$\text{But, we also have } V_C=15-10(I_1+I_C)=15-10(0.007+22.1I_B)=14.93-221I_B$$

$$\text{Therefore, } I_B=0.025 \text{ mA, } I_C=0.5 \text{ mA and } I_E=0.525 \text{ mA also } I_1=0.0595 \text{ mA}$$

$$V_E=2.625 \text{ V} \quad V_B=3.325 \text{ V} \quad V_C=V_B+100I_1+5I_B=9.4 \text{ V}$$

$$\text{Bias Point: } V_{CE}=6.775 \text{ V} \quad I_C=0.5 \text{ mA} \quad I_B=0.025 \text{ mA} \quad \textbf{(3 Marks)}$$

(c) Since $V_B=3.325$ V and $V_C=9.4$ V, the B-C junction is reverse biased as it should be **(1 Mark)**

2.

(a) The readings on the voltmeter and the ammeter (assumed ideal) were 14.4 V and 3.2 A respectively, when they were connected separately across terminals a and b of the linear network shown in Fig. 2 (a). Draw the Thevenin's equivalent circuit and the Norton's equivalent circuit for the network showing the values of all necessary parameters. [1]

(b) Write and solve the mesh equations for the circuit shown in Fig. 2(b) and calculate the total current through the $3\ \Omega$ resistor. [2]

(c) Verify the result of 2(b) using nodal analysis. Take node 4 as the reference. [2]

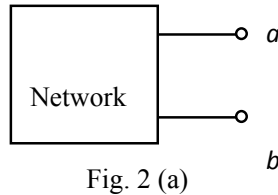


Fig. 2 (a)



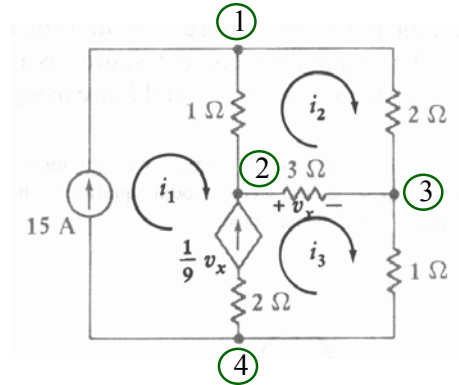


Fig. 2 (b)

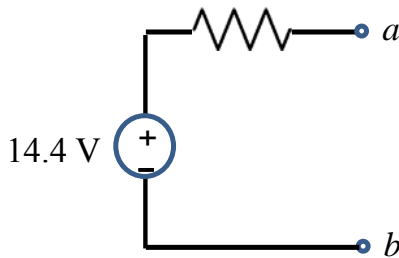(a) Open circuit voltage = 14.4 V, Short circuit resistance = $14.4/3.2 = 4.5\ \Omega$. Therefore the equivalents are as shown below:



Thevenin's equivalent

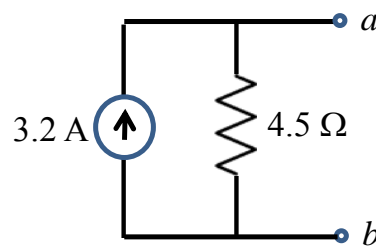

Norton's Equivalent

(0.5+0.5)

(b) The mesh equations are:

$$i_1 = 15,$$

$$v_x = 3 \times (i_3 - i_2)$$

$$i_3 - i_1 = v_x / 9 = (i_3 - i_2) / 3 \quad \Rightarrow \quad 2i_3 + i_2 = 45$$

$$(i_2 - i_1) \times 1 + 2i_2 = (i_3 - i_2) \times 3 \quad \Rightarrow \quad 2i_2 - i_3 = 5$$

(0.5+0.5+0.5)

Solving, $i_1 = 15\text{ A}$, $i_2 = 11\text{ A}$, $i_3 = 17\text{ A}$

Current through $3\ \Omega$ resistor = $i_3 - i_2 = 6\text{ A}$

(0.5)

(c) The node equations are:

$$1. \quad \frac{v_1 - v_2}{1} + \frac{v_1 - v_3}{2} = 15 \quad \Rightarrow \quad 3v_1 - 2v_2 - v_3 = 30$$

$$2. \quad \frac{v_2 - v_3}{9} = \frac{v_2 - v_1}{1} + \frac{v_2 - v_3}{3} \quad \Rightarrow \quad 9v_1 - 11v_2 + 2v_3 = 0 \quad (0.5+0.5+0.5)$$

$$3. \quad \frac{v_3 - v_1}{2} + \frac{v_3 - v_2}{3} + \frac{v_3}{1} = 0 \quad \Rightarrow \quad 3v_1 + 2v_2 - 11v_3 = 0$$

Solving, $v_1 = 39\text{ V}$, $v_2 = 35\text{ V}$, $v_3 = 17\text{ V}$

Current through $3\ \Omega$ resistor = $\frac{v_2 - v_3}{3} = 6\text{ A}$

(0.5)