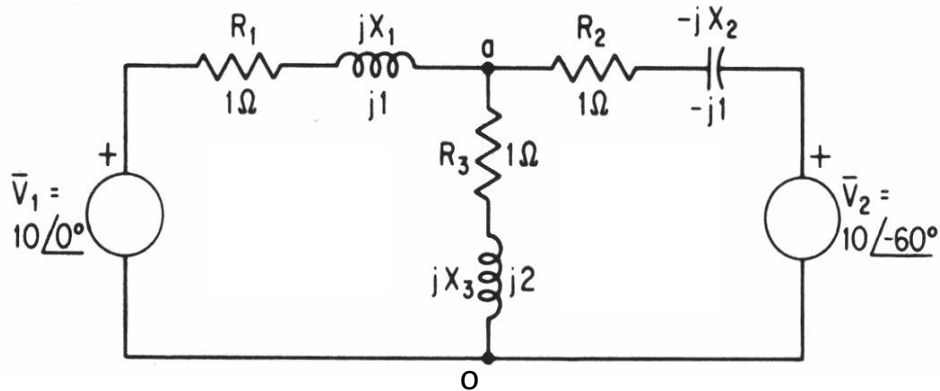


**EE101**  
**Tutorial-5 (11 Sep 2014)**

Q1. Use Norton's theorem to find the current through  $R_3$ ,  $X_3$  branch in the circuit shown below.



Q2. For the transistor amplifier circuit with collector-emitter feedback biasing shown in Figure 1, find the value of

- $I_B$
- $V_C$
- $V_E$
- $V_{CE}$

(Assume that  $V_{BE} = 0.7\text{ V}$  in forward biased condition)

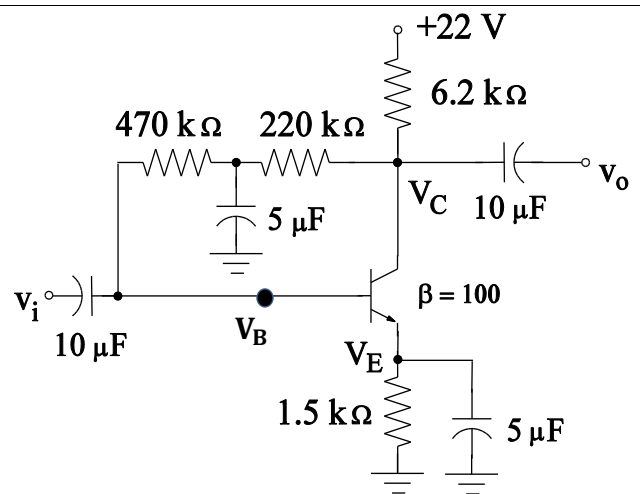


Figure 1

Q3. In Figure 2, the transistor is in active region with the quiescent C-E voltage  $V_{CEQ} = 4\text{ V}$ . Assume that  $V_{BE} = 0.7\text{ V}$ ,  $V_T = 26\text{ mV}$ , BJT output resistance  $r_o$  is very high ( $> 100\text{ k}\Omega$ ), and all capacitors are short-circuited at applied signal frequency. Find the value of

- $R_1$
- $r_e$
- $A_v = \frac{v_o}{v_i}$
- $A_v$ , if a load  $R_L = 2\text{ k}\Omega$  is connected across A-B.
- $A_{v_s} = \frac{v_o}{v_s}$ , if  $R_L = 2\text{ k}\Omega$  is connected across A-B and assuming that applied voltage source has a resistance of  $R_s = 0.5\text{ k}\Omega$ .

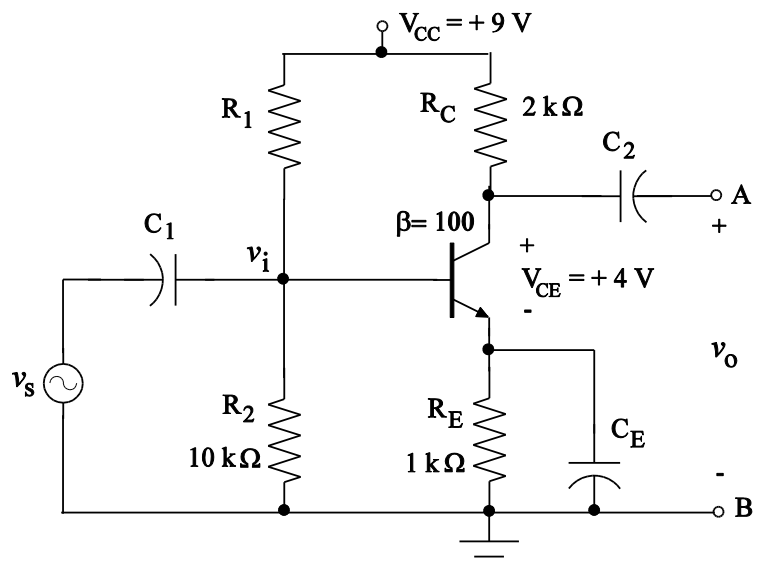


Figure 2

**EE101**  
**Tutorial-5 (11 Sep 2014)**  
**Solutions**

Q1. Impedance between the terminals a-o,

$$Z_N = (R_1 + jX_1) \parallel (R_2 - jX_2)$$


Therefore,

$$Z_N = (1 + j1) / (1 - j1) = \frac{\sqrt{2} \angle 45^\circ \times \sqrt{2} \angle -45^\circ}{1 + j1 + 1 - j1} = 1 \angle 0^\circ \Omega$$

Short circuit current across a-o,

$$\begin{aligned} I_{sc} &= \frac{V_1}{R_1 + jX_1} + \frac{V_2}{R_2 - jX_2} = \frac{10 \angle 0^\circ}{1 + j1} + \frac{10 \angle -60^\circ}{1 - j1} = 5\sqrt{2} \angle -45^\circ + 5\sqrt{2} \angle -15^\circ \\ &= 6.83 - j1.83 + 5 - j5 = 11.83 - j6.83 \\ &= 13.66 \angle -30^\circ \text{ A} \end{aligned}$$

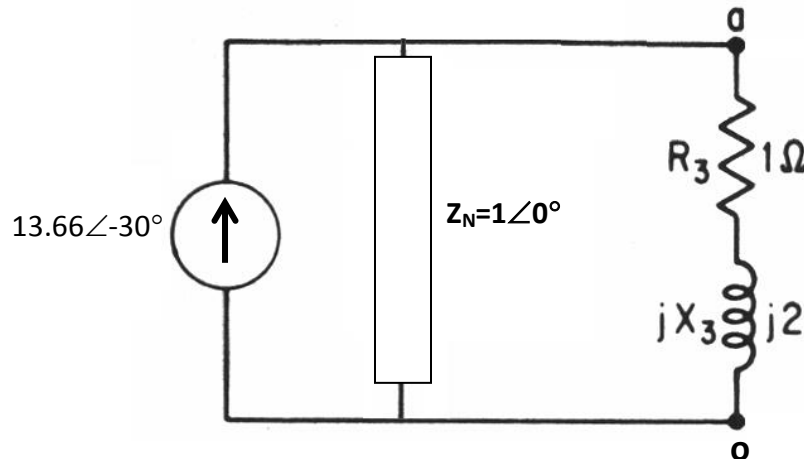The Norton's equivalent circuit is as shown below,




And the current through  $R_3$ ,  $X_3$  is computed as:

$$\begin{aligned} I_3 &= I_{sc} \times \frac{1 \angle 0^\circ}{1 \angle 0^\circ + 1 + j2} = 13.661 \angle -30^\circ \times \frac{1}{2\sqrt{2} \angle 45^\circ} \\ &= 4.83 \angle -75^\circ \text{ A} \end{aligned}$$

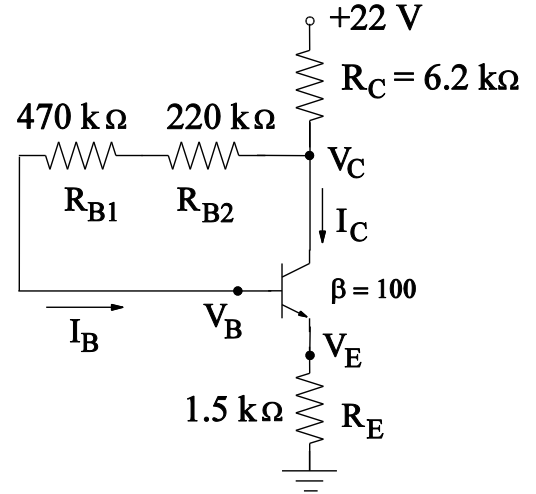Q2. For determining the dc current and voltages, the DC-equivalent circuit for the given transistor amplifier is shown below.

In the given circuit  $V_B$  is expected to be higher than  $V_E$ , so the B-E junction would be forward biased and we assume that the transistor is in **active region** of operation, i.e.,  $I_C = \beta I_B$



(a) On applying KVL in the input (base) loop we have

$$V_{CC} = I_B(R_{B1} + R_{B2}) + V_{BE} + (I_B + I_C)(R_C + R_E)$$

$$I_B = \frac{V_{CC} - V_{BE}}{(R_{B1} + R_{B2}) + (\beta + 1)(R_C + R_E)}$$

$$I_B = \frac{22\text{ V} - 0.7\text{ V}}{(470\text{ k}\Omega + 220\text{ k}\Omega) + 101(6.2\text{ k}\Omega + 1.5\text{ k}\Omega)} \cong 14.51\text{ }\mu\text{A}$$

$$\begin{aligned} \text{(b) } V_C &= V_{CC} - (\beta + 1)I_B R_C = 22\text{ V} - 101 \times 14.51\text{ }\mu\text{A} \times 6.2\text{ k}\Omega \\ &= 22\text{ V} - 9.09\text{ V} \\ &= 12.91\text{ V} \end{aligned}$$

$$\text{(c) } V_E = (\beta + 1)I_B R_E = 101 \times 14.51\text{ }\mu\text{A} \times 1.5\text{ k}\Omega \cong 2.20\text{ V}$$

$$\text{(d) } V_{CE} = V_C - V_E = 12.91\text{ V} - 2.20\text{ V} = 10.71\text{ V}$$

**Check:**  $V_B = V_E + 0.7\text{ V} = 2.9\text{ V}$  and so  $V_{CB} = 12.91\text{ V} - 2.9\text{ V} = 10.01\text{ V}$ . Thus C-B junction is reversed biased and assumption about transistor being in active region is valid.

Q3. Given that  $V_{CEQ} = 4\text{ V}$  and the transistor is in active region, so  $I_C = \beta I_B$

(a) On applying KCL in the output (collector) loop, we have

$$V_{CC} = I_C R_C + V_{CEQ} + I_E R_E = I_C R_C + V_{CEQ} + \left(1 + \frac{1}{\beta}\right) I_C R_E$$

$$I_C = \frac{V_{CC} - V_{CEQ}}{R_C + \left(1 + \frac{1}{\beta}\right) R_E} = \frac{9\text{ V} - 4\text{ V}}{2\text{ k}\Omega + 1.01 \times 1\text{ k}\Omega} = 1.66\text{ mA}$$

and

$$I_B = \frac{I_C}{\beta} = \frac{1.66\text{ mA}}{100} = 0.0166\text{ mA}$$

For the voltage-divider biasing, find the Thevenin's equivalent as seen by B-E terminals of BJT as

$$V_{Th} = \left(\frac{9 \times 10\text{ k}\Omega}{10\text{ k}\Omega + R_1}\right) V \quad \text{and} \quad R_{Th} = (10\text{ k} \parallel R_1) \Omega$$

Now applying KVL in the input (base) loop, we have


$$\left(\frac{9 \times 10\text{ k}\Omega}{10\text{ k}\Omega + R_1}\right) V = \left(\frac{R_1 \times 10\text{ k}\Omega}{10\text{ k}\Omega + R_1}\right) I_B + V_{BE} + (1 + \beta) I_B R_E$$

$$\left(\frac{90\text{ k}\Omega - 0.166 R_1}{10\text{ k}\Omega + R_1}\right) V = 0.7\text{ V} + 101(0.0166\text{ mA} \times 1\text{ k}\Omega) \cong 2.38\text{ V}$$

$$90\text{ k}\Omega - 0.166 R_1 = 23.8\text{ k}\Omega + 2.38 R_1 \Rightarrow R_1 = \frac{66.2\text{ k}\Omega}{2.546} = 26\text{ k}\Omega$$

$$(b) \quad I_E = (1 + \beta) I_B \cong 1.68\text{ mA}, \quad \text{so} \quad r_e = \frac{26\text{ mV}}{I_E} = \frac{26\text{ mV}}{1.68\text{ mA}} \cong 15.5\text{ }\Omega$$

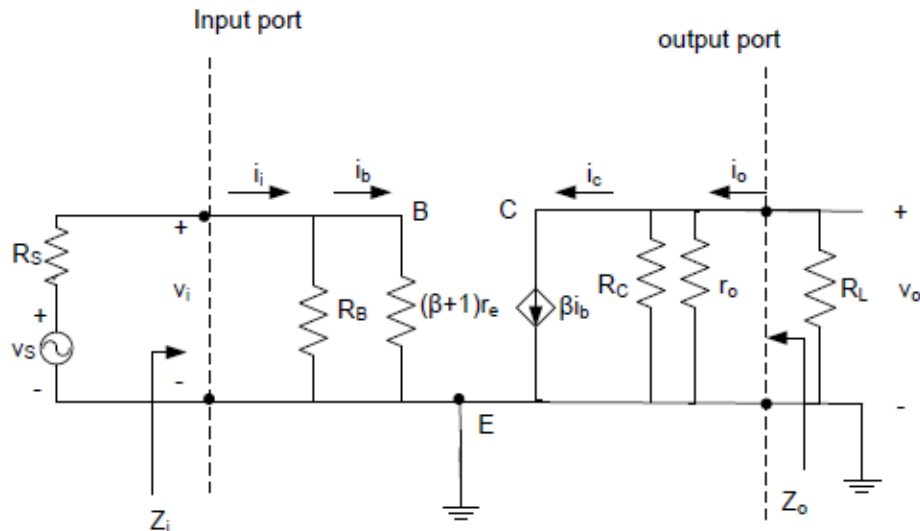The AC equivalent circuit of the given amplifier circuit (Given for reference purpose only)




(c) Using the derived expression, the voltage gain,

$$A_v = \frac{v_o}{v_i} = -\frac{R_C \parallel r_o}{r_e} \cong -\frac{R_C}{r_e} = -\frac{2 \text{ k}\Omega}{15.5 \Omega} = -129$$

(d) The voltage gain with load  $R_L$  connected across A-B,

$$A'_v = -\frac{R_C \parallel R_L}{r_e} = -\frac{2 \text{ k}\Omega \parallel 2 \text{ k}\Omega}{15.5 \Omega} = -64.5$$

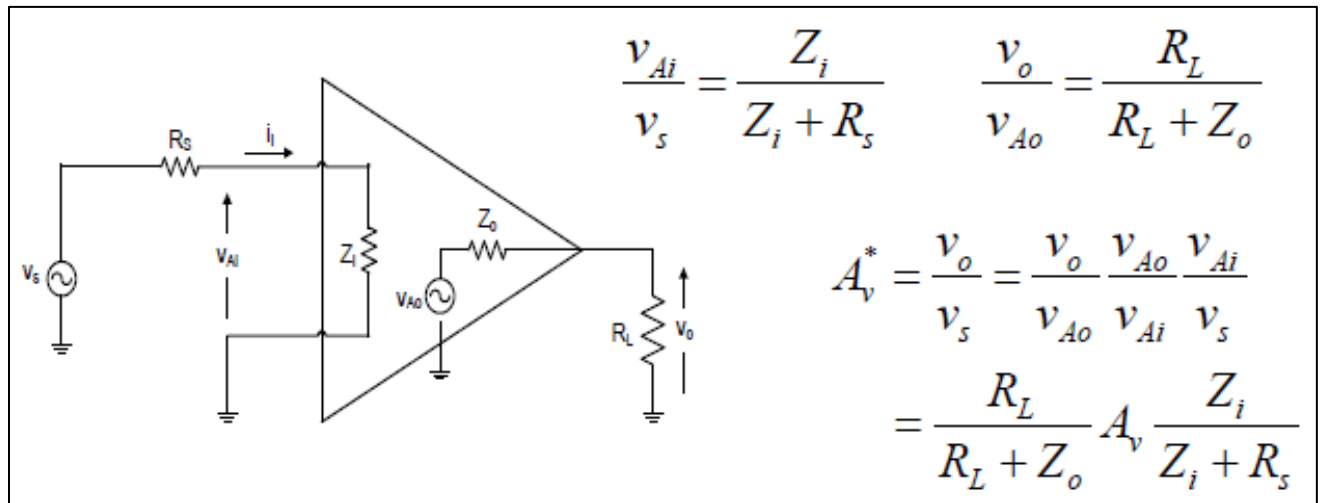(e) The voltage gain of amplifier with source resistance  $R_s$  and load resistance  $R_L$  included, is derived as below (the below material is copied from that in slides)



$$A_{v_s} = \frac{v_o}{v_s} = \frac{Z_i}{R_s + Z_i} \times A_v \times \frac{R_L}{Z_o + R_L}$$

where  $Z_i$  is the input resistance and  $Z_o$  is the output resistance of amplifier, respectively

$$Z_i = (R_1 \parallel R_2) \parallel (\beta + 1)r_e = (26 \text{ k}\Omega \parallel 10 \text{ k}\Omega) \parallel (101 \times 15.5 \Omega) \cong 1.29 \text{ k}\Omega$$

$$Z_o \cong R_C = 2 \text{ k}\Omega$$

$$A_{v_s} = \frac{1.29 \text{ k}\Omega}{0.5 \text{ k}\Omega + 1.29 \text{ k}\Omega} \times (-129) \times \frac{2 \text{ k}\Omega}{2 \text{ k}\Omega + 2 \text{ k}\Omega} \cong -46.5$$

**Note for the reduction in the overall gain of the amplifier due to inclusion of load resistance and/or source resistance.**