

INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI  
DEPARTMENT OF ELECTRONICS & ELECTRICAL ENGINEERING  
**EE 101: Electrical Sciences**  
**Tutorial-7**

*(First question is the **Pre-Tutorial Assignment problem** to be done in the space provided.)*

Name:

Roll No.:

Tutorial Group:

---

**Question-1(Pre Tutorial Question):** Three star connected impedances  $Z_1 = 20 + j37.7 \, \Omega$  per phase are in parallel with three delta connected impedances  $Z_2 = 30 - j159.3 \, \Omega$  per phase. The line voltage is **398 volts rms**. Find the line currents, power factor, power and reactive volt ampere taken by the combination. **(Hint: Convert impedances connected in delta into their equivalent star connected configuration. For a balanced network,  $Z_{Star} = \frac{Z_{Delta}}{3}$  )**

**Question-2:** In the balanced three phase system of Fig. 1, let  $Z_P = 12 + j5 \Omega$  and  $I_{bB} = 20 \angle 0^\circ$  A rms with (+) phase sequence. If the source is operating with a power factor of 0.935, find (a)  $R_W$  (b)  $V_{bn}$  (c)  $V_{AB}$  (d) complex power supplied by the source.


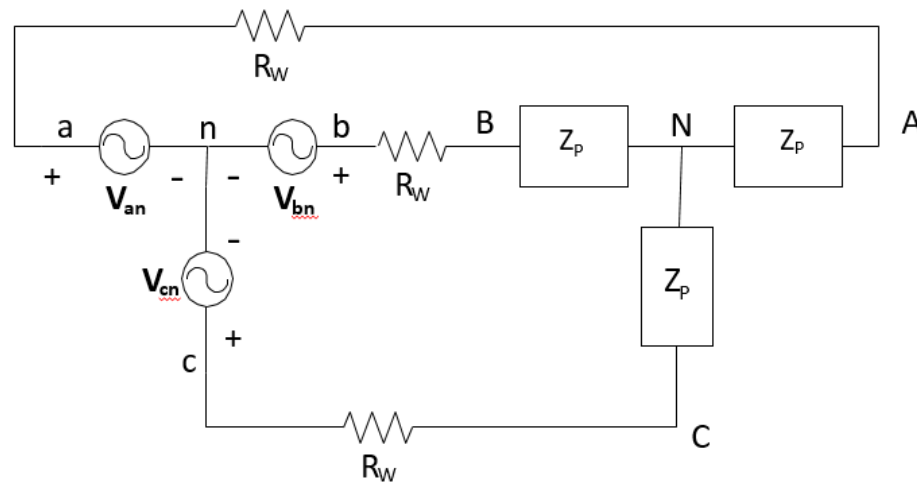


Figure -1

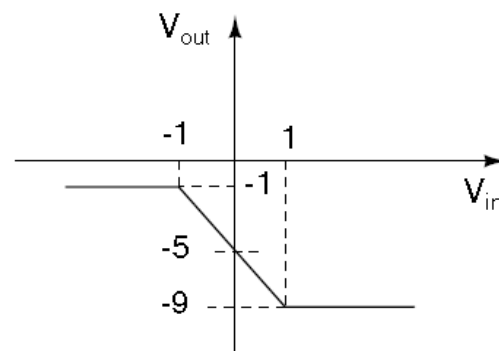
**Question-3:**


Transfer characteristics of a circuit are shown below.




Draw the output (as a function of time) of this circuit for the following inputs:  $5 + \cos \omega t$ ,  $0.2 \cos \omega t$ ,  $1.2 \cos \omega t$

**Question-4:**

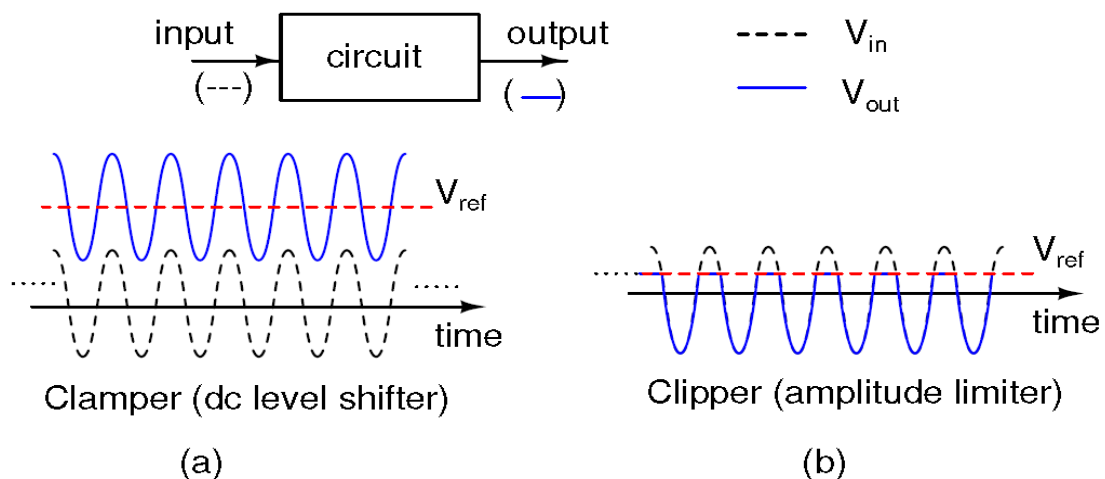

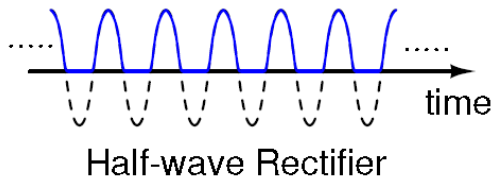

(c)

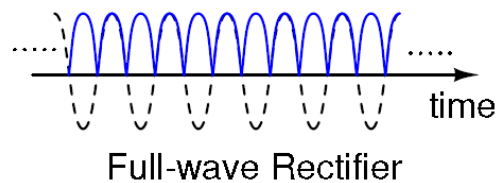

(d)


Draw the transfer (output amplitude w.r.t. input amplitude) characteristics of the above circuits.

**Question-5:**


A voltage controlled resistor  $R_{AB}$  has the following characteristics.

$$R_{AB} = \begin{cases} \infty & \text{for } V_{AB} < 0 \\ 0 & \text{for } V_{AB} \geq 0 \end{cases}$$

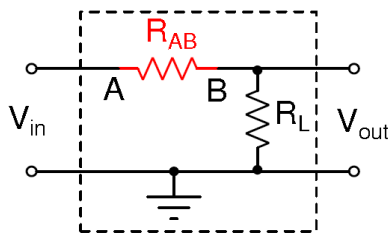Plot the transfer characteristics of the following circuits.  $R_L$  is a normal resistor.



(a)

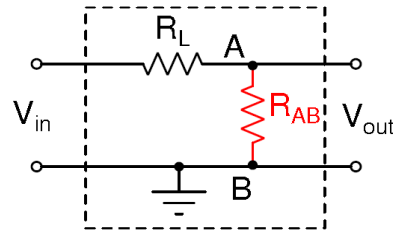

(b)