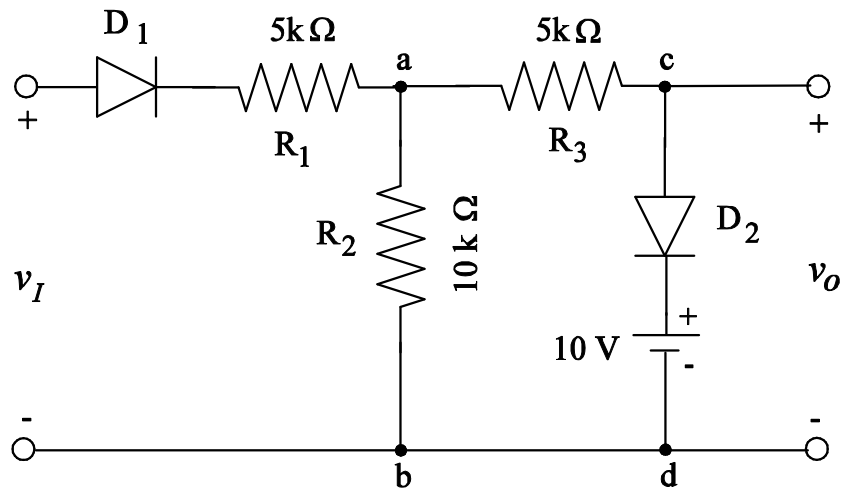


EE101
Tutorial-3(21 Aug 2014)


Q1. For the circuit shown in Figure, assume that the diodes are ideal.

(a) Sketch the transfer characteristic of the circuit for $-20\text{ V} \leq v_I \leq 20\text{ V}$.

(b) If the diode D_2 in the circuit is reversed, sketch the resulting transfer characteristics for $-20\text{ V} \leq v_I \leq 20\text{ V}$.



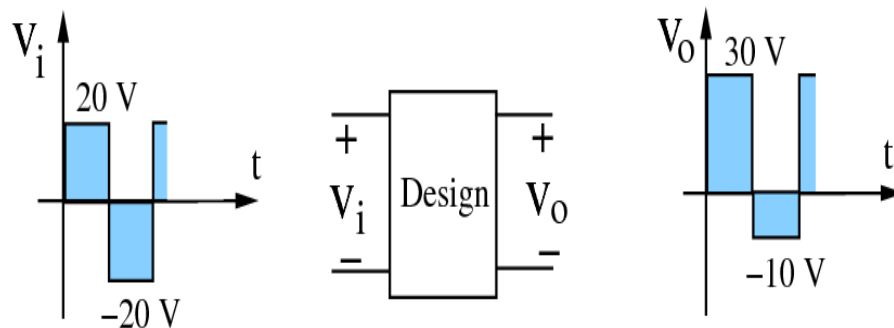Q2. Design a clamper using a diode with forward voltage of 0.7 V to perform the wave shaping shown in Figure below. The frequency of the square-wave input is 1 kHz .



Q3. A transistor has $\beta = 100$. Given that for this transistor base current I_B is set in such a way that $I_B = 10 \times I_{CO}$. If $I_B = 20\text{ }\mu\text{A}$, find I_C and I_E .


EE101
Tutorial-3 (21 Aug 2014)
Solutions

1. (a) For $-20\text{ V} \leq v_i < 0\text{ V}$, both diodes D_1 and D_2 are OFF, so $v_o = 0\text{ V}$. Now for $v_i > 0\text{ V}$, D_1 starts conducting being an ideal diode, but D_2 remains OFF till the voltage $V_{ab} < 10\text{ V}$. Thus for $v_i > 0\text{ V}$ and till D_2 is OFF, we have


$$v_o = V_{ab} = \frac{R_2}{R_1 + R_2} v_i \Rightarrow v_o = \frac{2}{3} v_i$$

Diode D_2 turns ON as soon as $V_{ab} = 10\text{ V}$ or $v_i = \frac{3}{2} \times 10 = 15\text{ V}$.

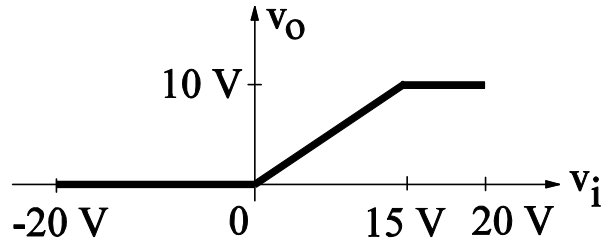So for $v_i \geq 15\text{ V}$, the diode D_2 conducts and $v_o = 10\text{ V}$. The transfer characteristics of the given circuit is shown below,




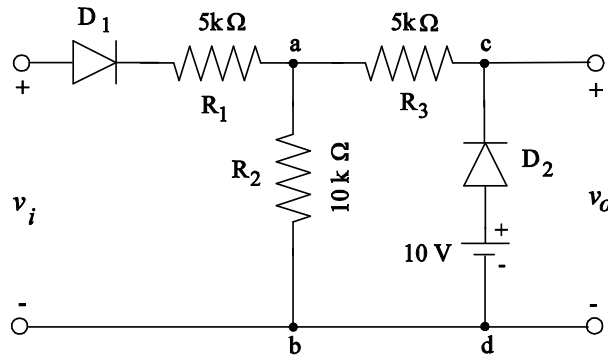- (b) The modified circuit is shown below.



As long as the voltage $V_{ab} < 10\text{ V}$, the diode D_2 remains ON and $v_o = 10\text{ V}$. Note $V_{ab} = 10\text{ V}$ when $v_i = 15\text{ V}$ as already calculated in part (a). So for $v_i \geq 15\text{ V}$ we have $V_{ab} \geq 10\text{ V}$ and D_2 is OFF, the output voltage would be proportional to the input voltage, i.e., $v_o = \frac{2}{3} v_i$

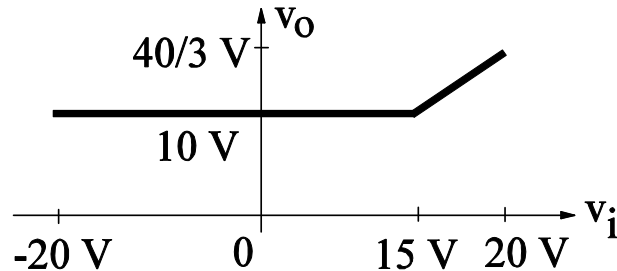While for $-20\text{ V} \leq v_i < 15\text{ V}$ and $V_{ab} < 10\text{ V}$, the diode D_2 remains ON and $v_o = 10\text{ V}$. The transfer characteristics of modified circuit is shown below,



- Q2. On comparing the input and output waveforms of the clamper, we can deduce that it is a positive clamper with negative bias.

The period of the square-wave input is 0.001 sec (= 1/ 1000 Hz).

For the faithful reproduction of the input waveform shape at the output, the time-constant of clamper circuit should at least 50 times that of the period of input signal.

Thus by choosing $R = 100 \text{ k}\Omega$ and $C = 1 \text{ }\mu\text{F}$, we have time-constant $RC = 0.1 \text{ sec}$ and it satisfies that condition, well enough.


From given figure, the shift in the peak positive voltage is noted as

$$V_{\text{shift}} = V_{o \text{ max}} - V_{i \text{ max}} = 30 - 20 = 10 \text{ V}$$

The required negative DC bias,

$$V_{\text{dc}} = V_{i \text{ max}} - V_{\text{shift}} - V_{\text{DO}} = 20 - 10 - 0.7 = 9.3 \text{ V}$$

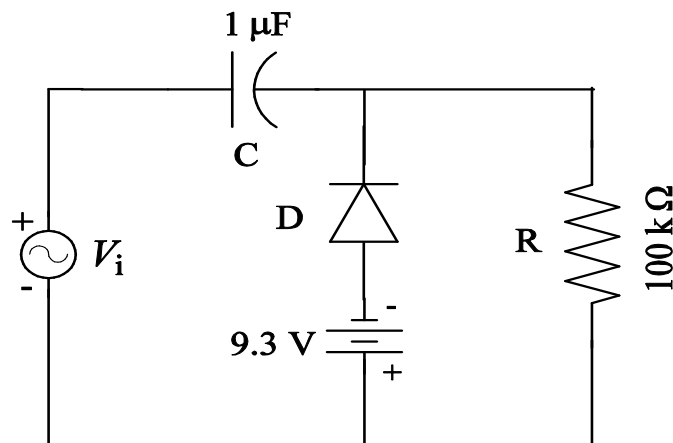The overall design of clamper is shown as



- Q3.

$$I_C = \alpha I_E + I_{CO}$$

$$I_E = I_C + I_B = \alpha I_E + I_{CO} + I_B$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$I_E = \frac{1}{1 - \alpha} (I_{CO} + I_B) = (\beta + 1) \times 1.1 I_B = 101 \times 1.1 \times 20 = 2222 \text{ }\mu\text{A} = 2.222 \text{ mA}$$

$$I_C = 2.222 - 0.02 = 2.202 \text{ mA}$$

Alternatively,

$$I_C = \beta I_B + (\beta + 1) I_{CO} = 100 \times 0.02 + 101 \times \frac{0.02}{10} = 2.202 \text{ mA}$$