
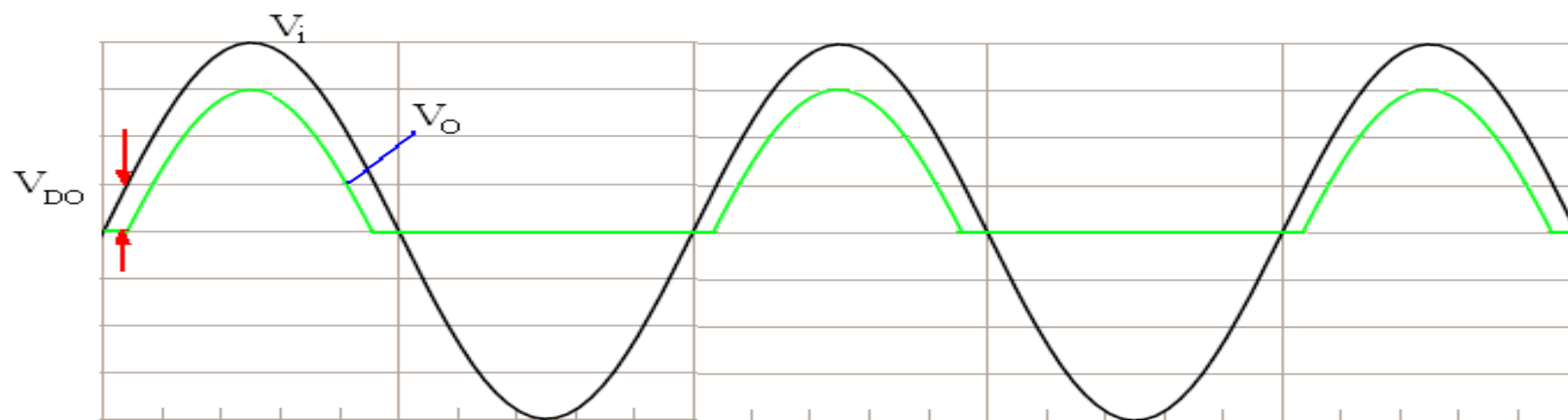



# Rectifier Circuits

## Half-wave rectifier (HWR)

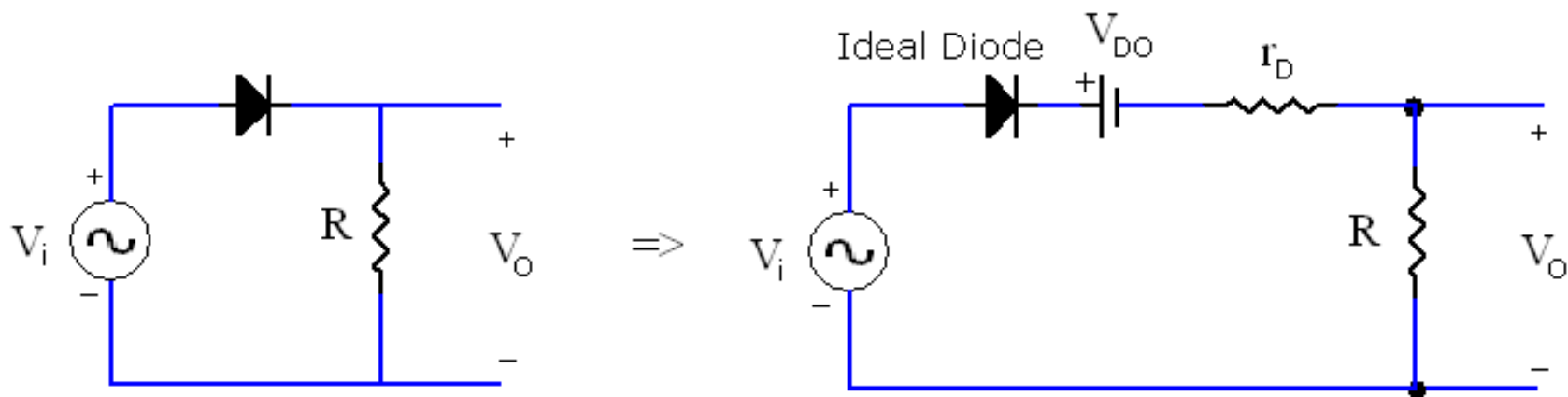

Input & output waveforms, assuming  $r_D \ll R$

## Considering the diode to be ideal

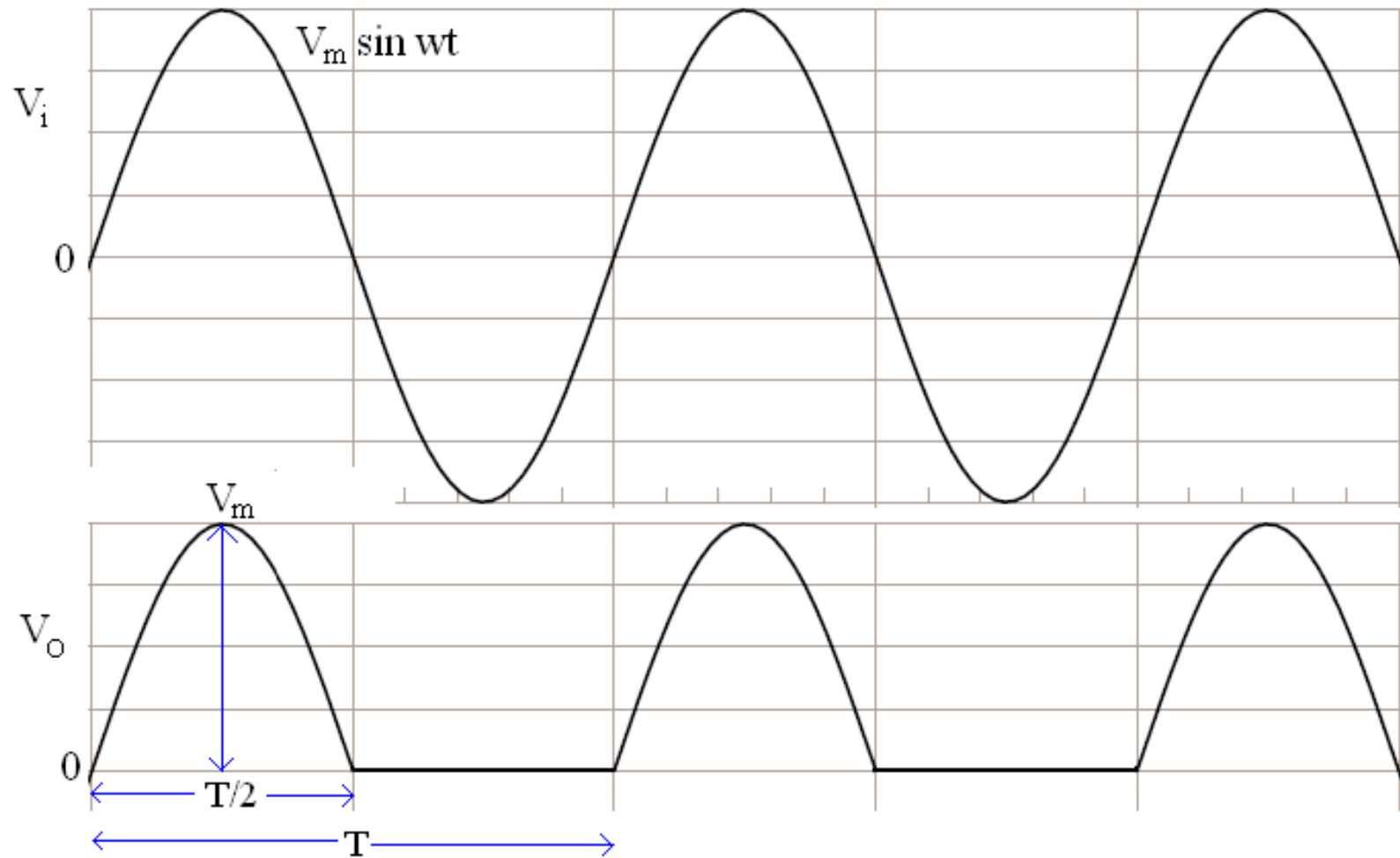

$$V_{DC}$$

$$V_{DC} = \frac{1}{T} \int_0^{T/2} V_m \sin \omega t dt$$

$$\frac{2\pi}{\omega} = T$$

$$= \frac{-V_m}{\omega T} [\cos \omega t]_0^{T/2}$$

$$= \frac{V_m}{\pi}$$

$$V_{DC} = 0.318 V_m$$

If Si diode is used,  $V_K = 0.7V$

$$\& V_o = V_i - V_K$$



The effect is reduction of area above the axis, which reduces the resulting DC voltage level.

For  $V_m \gg V_K$ , we can write

$$V_{DC} = 0.318 (V_m - V_K) \text{ (approx.)}$$


# Full Wave Rectifier (FWR)

## 1. Bridge Network

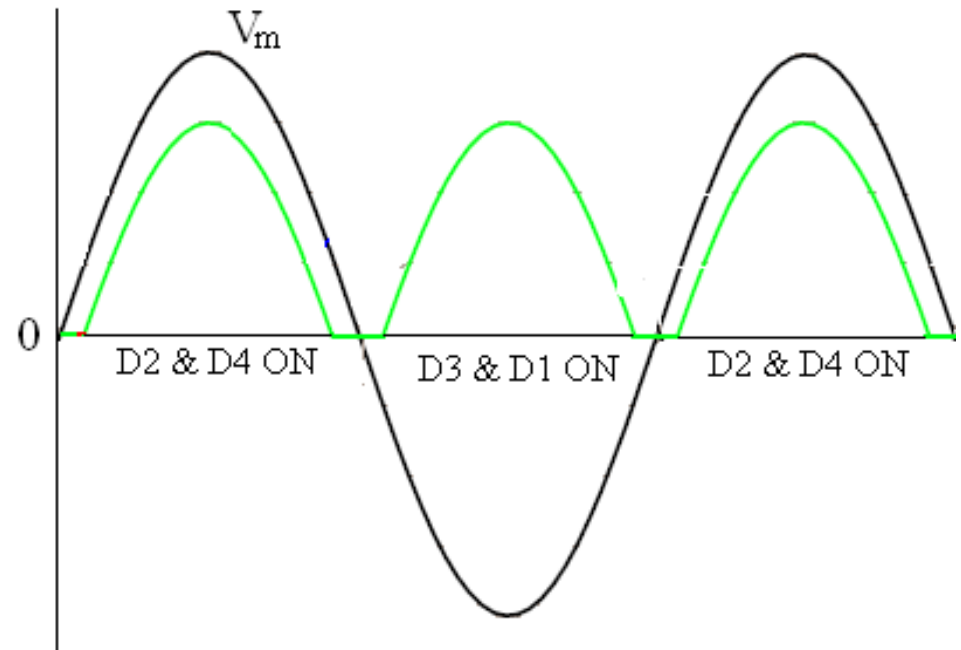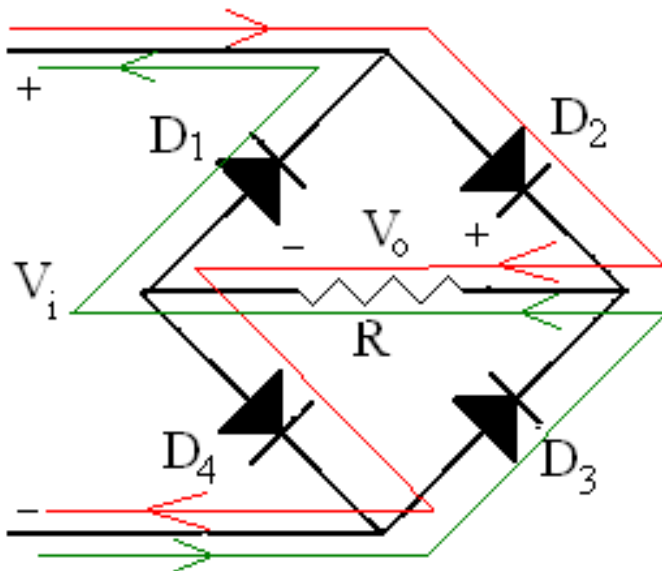

Assuming ideal diode,
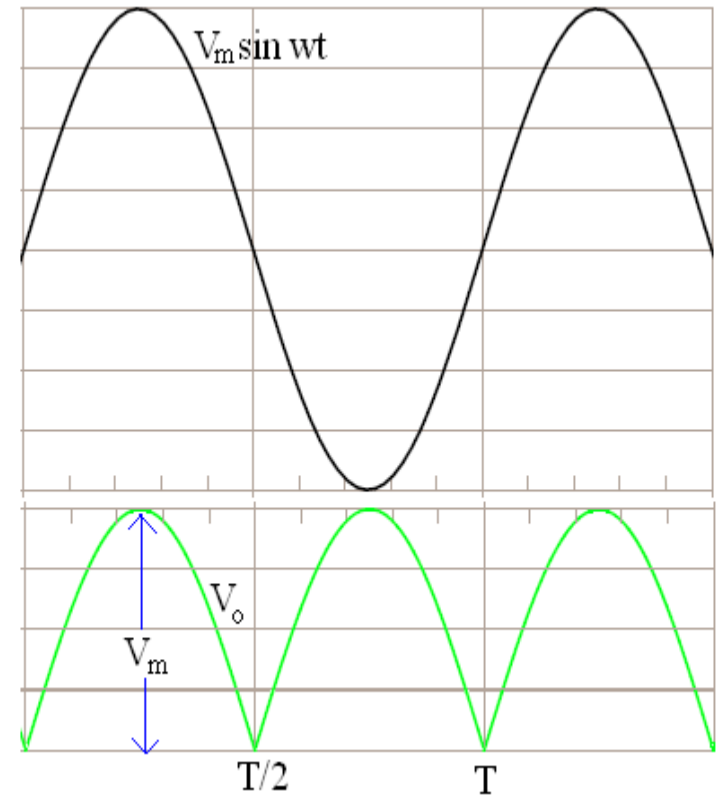
$$\begin{aligned} V_{\text{DC}} &= \frac{2}{T} \int_0^{T/2} V_m \sin \omega t dt \\ &= \frac{-2V_m}{\omega T} [\cos \omega t]_0^{T/2} \\ &= \frac{2V_m}{\pi} \end{aligned}$$



Assuming ideal diode

$$V_{dc}=0.636V_m$$


Peak value of the output voltage

$$V_{0max}=V_m-2V_k$$


For  $V_m \gg 2V_k$ ,  $V_{dc} \approx 0.636(V_m - 2V_k)$

$$PIV \geq V_m - V_k$$

# Using Centre-Tapped Transformer

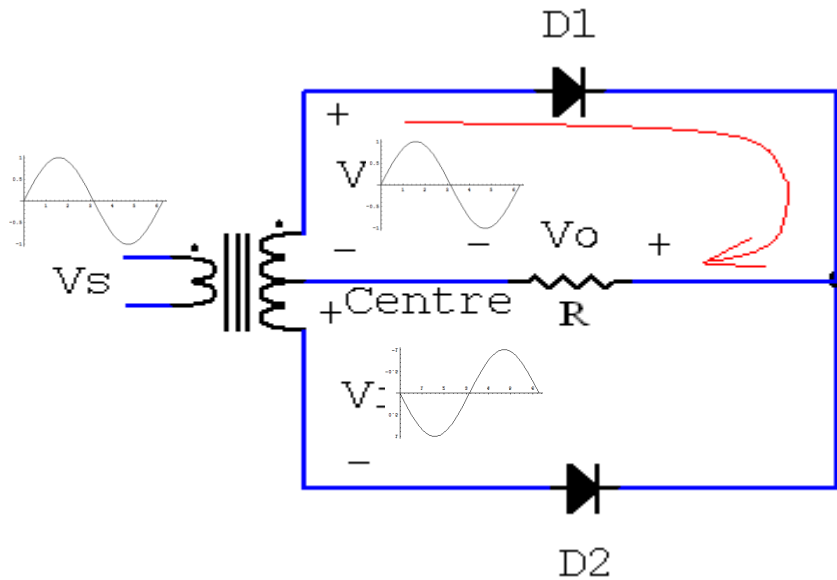


PIV across each diode  
is  $2V_m - V_k$

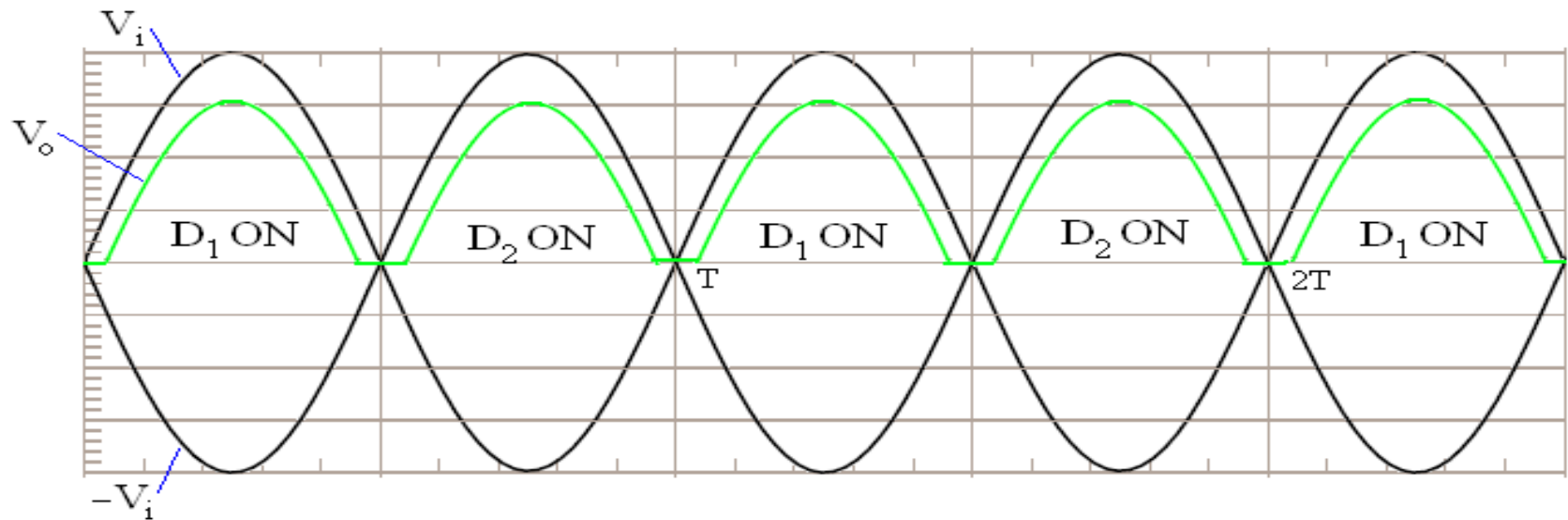





# HWR with Capacitor Filter

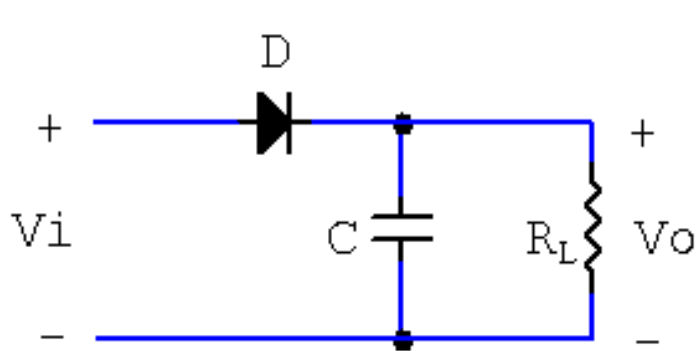

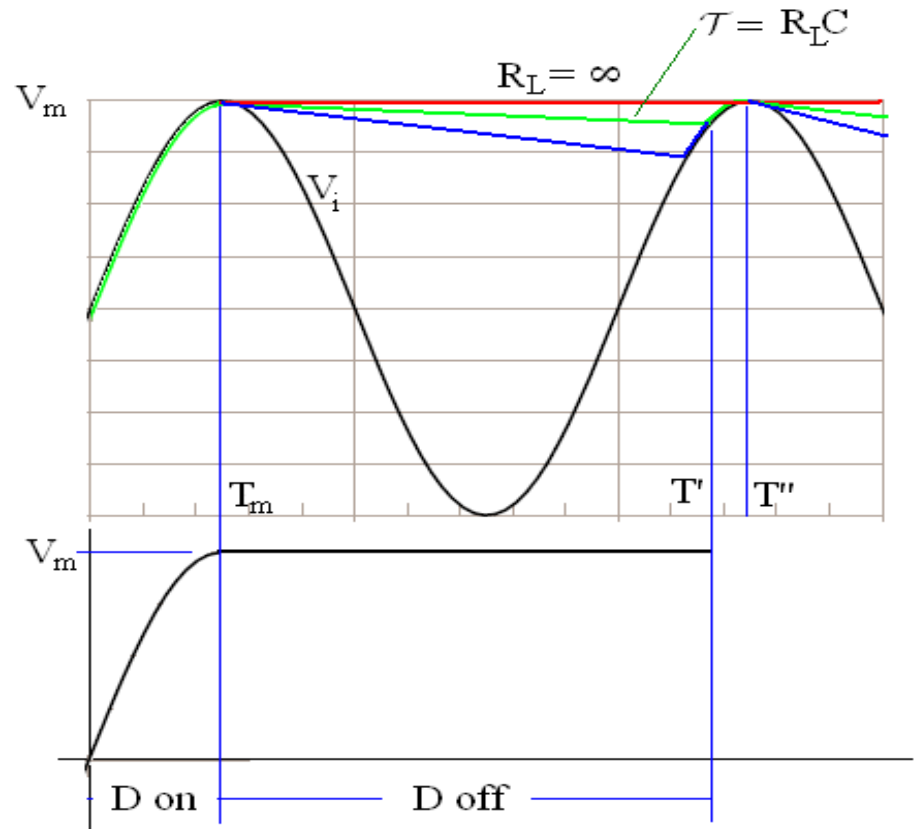Assuming ideal diode  
for simplicity,  
 $V_D = 0$ ,  $R_f = 0$




# FWR with Capacitor Filter

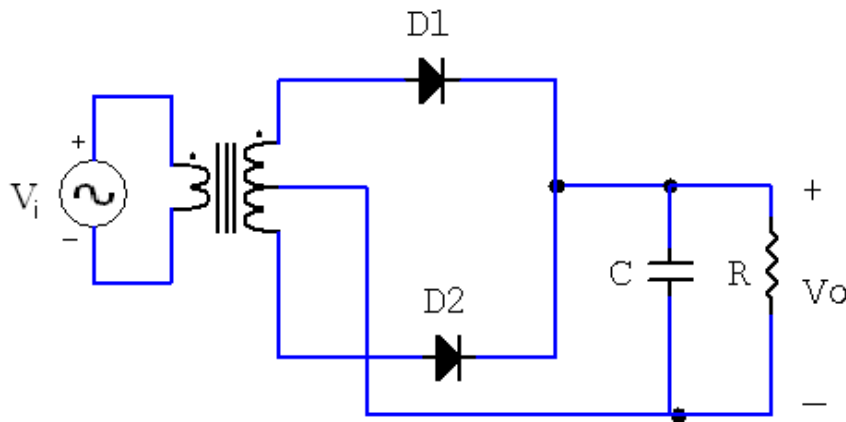

Assuming triangular ripple waveform,  
 $V_o(\text{dc}) = V_m - V_{r(\text{p-p})}/2$

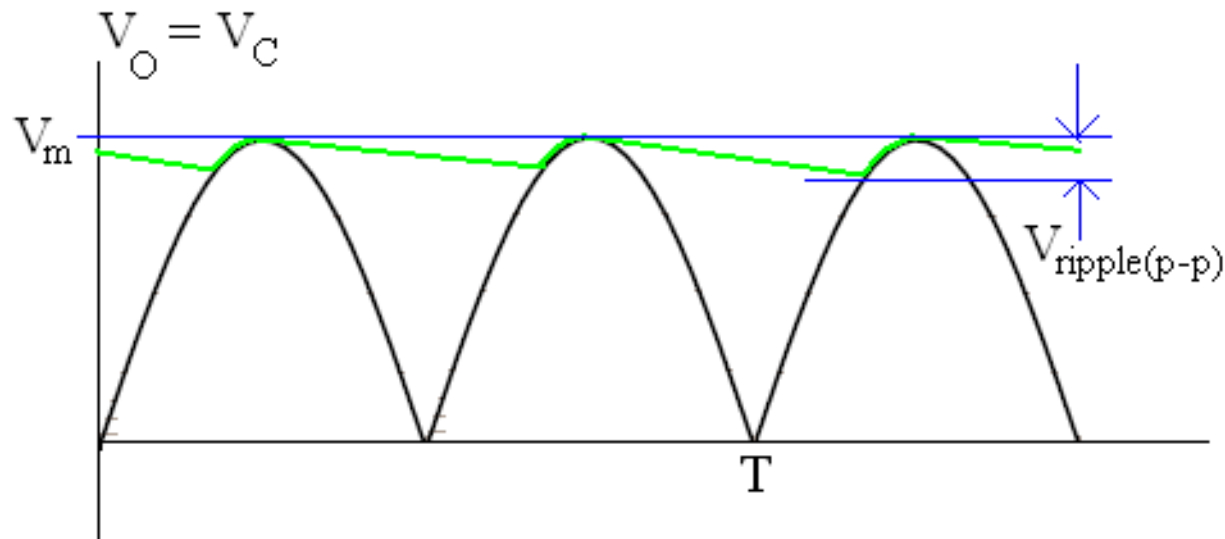Ripple factor  $r$   
 $= V_{r(\text{rms})}/V_{\text{dc}}$






# Wave Shaping Circuits




Diodes can be used in waveshaping circuits that either limit or “clip” portions of a signal, or shift the dc voltage level. These circuits are called **clippers** and **clampers** respectively.

Clippers are networks that employ diodes to clip away a portion of the input signal without distorting the remaining part of the applied waveform

## Example 1: Clipper Circuit

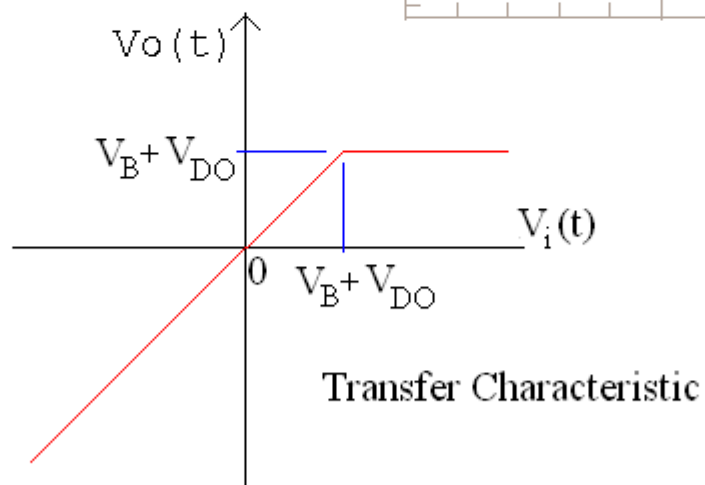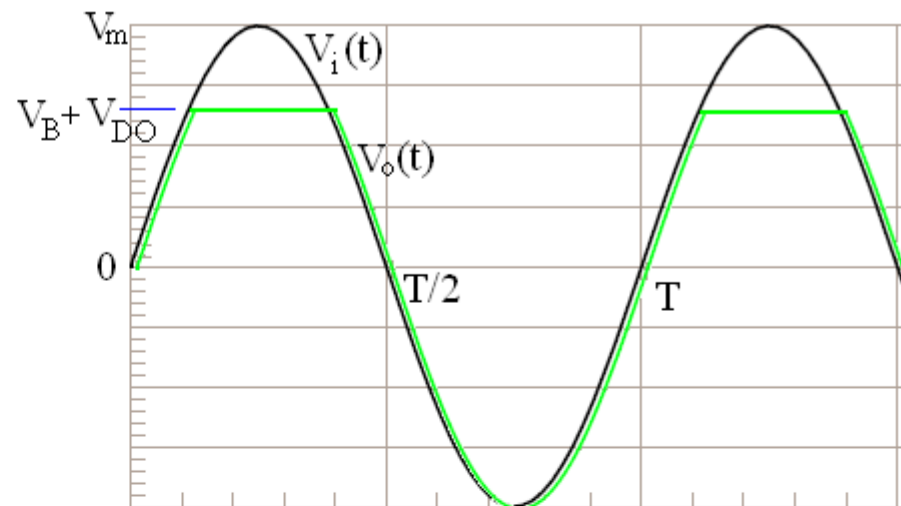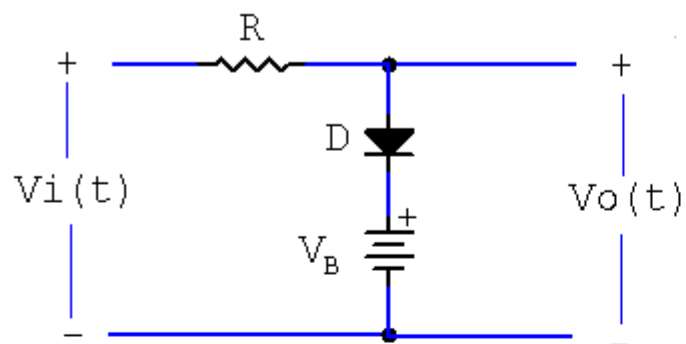


## Example 2

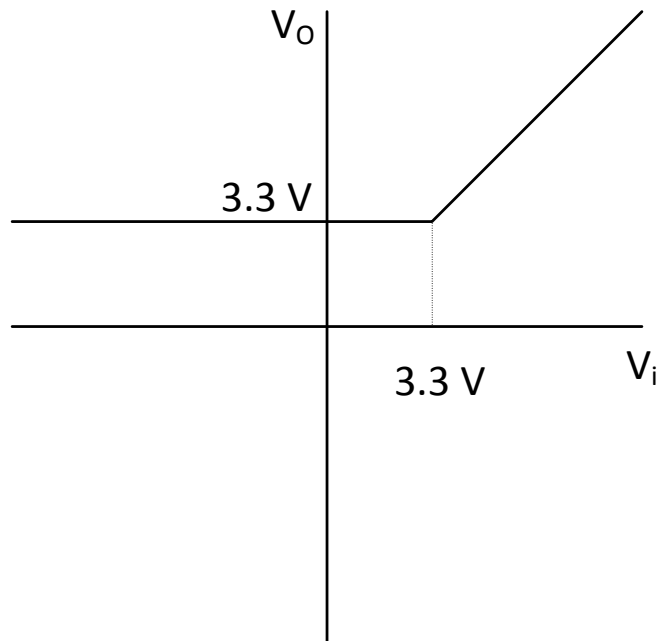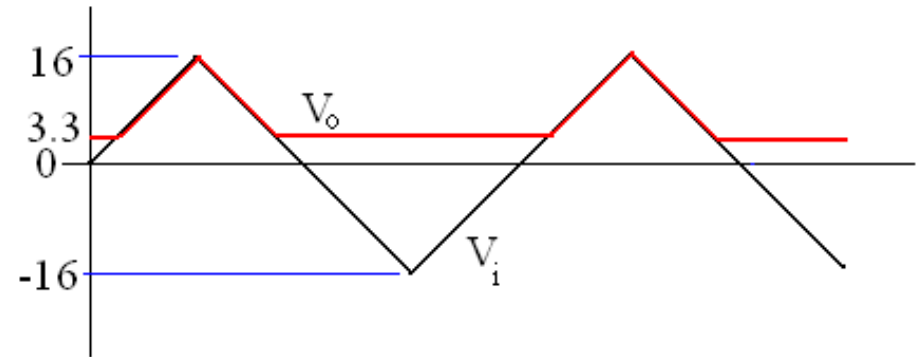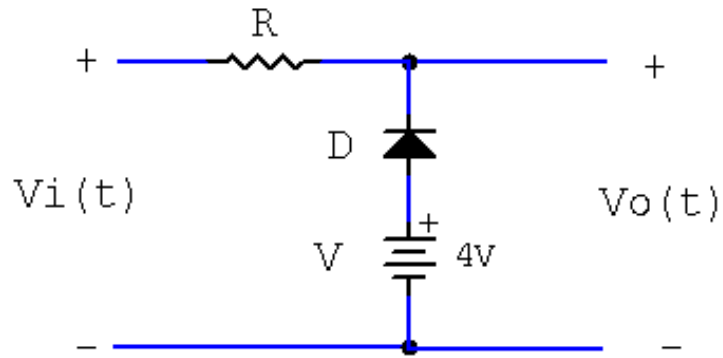


$$\begin{aligned}
 V_{DO} &= 0.7V \\
 V_o &= (4 - 0.7)V \\
 &= 3.3V
 \end{aligned}$$

## Example 3

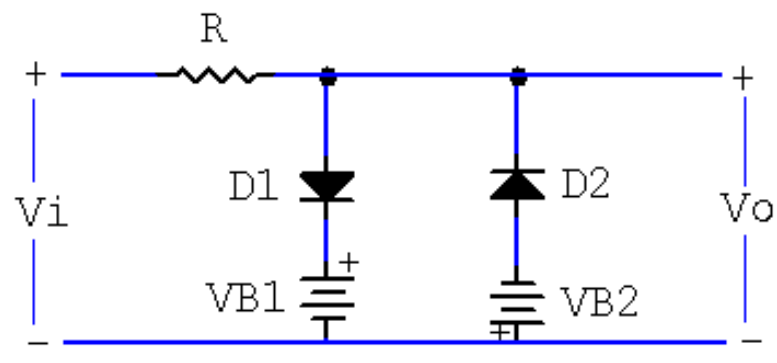

$$(V_{B1} + V_{DO})$$


$$-(V_{B2} + V_{DO})$$

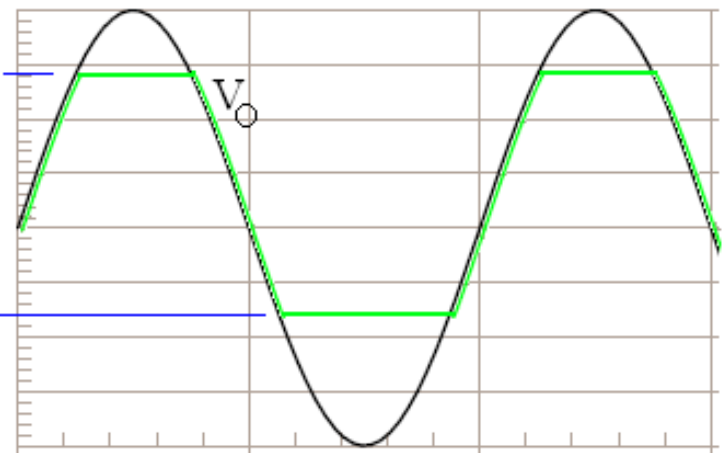

# Clampers

A clamper is a network constructed of a diode, a resistor and a capacitor that shifts a **periodic** waveform to a different DC level without changing the appearance of the applied signal.

## Example

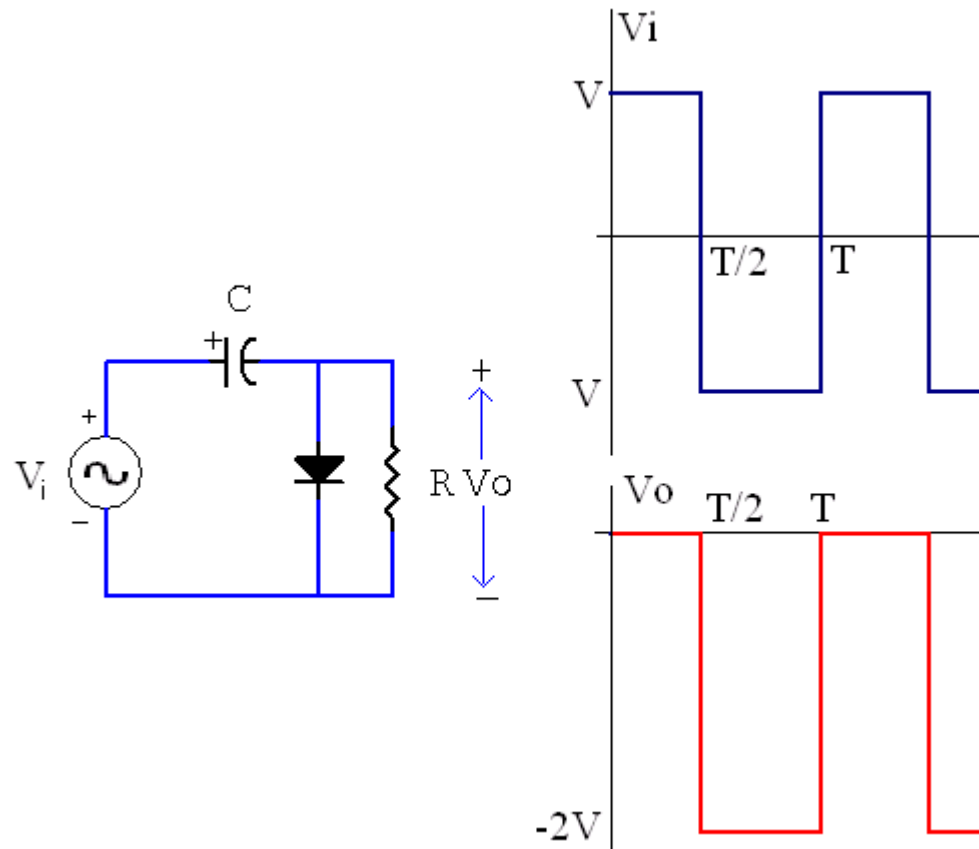


# Clampers

Try the following on your own –

1. Reverse the direction of the diode  
Signal is now clamped to positive levels
2. Add a battery in series with the diode – try both polarities of the battery  
Clamping level is now decided by the battery voltage
3. See what happens when the input is a **sine wave** (or any arbitrary waveform)  
We still get clamping action



## Example 4

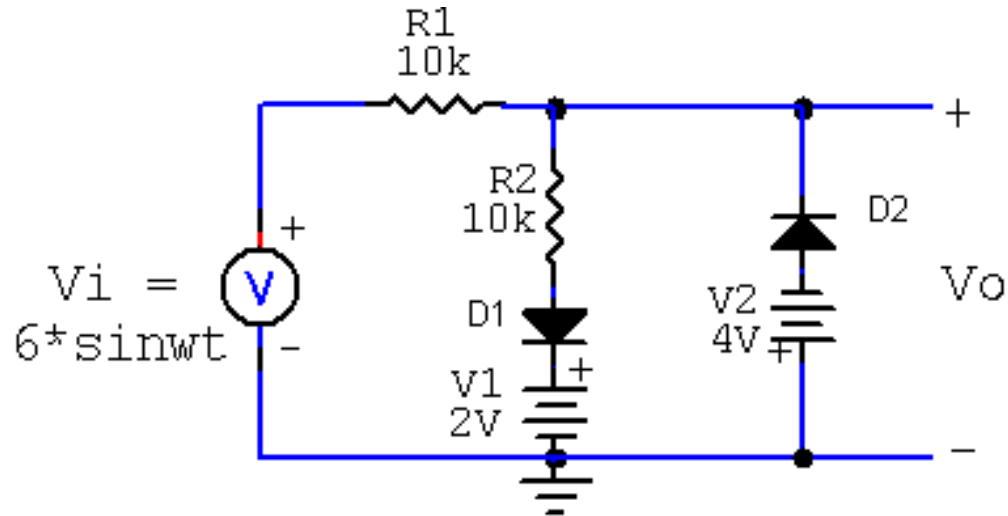

**Find  $V_o$**

Assume ideal diodes, i.e.

$V_{D0} = 0$ ,  $R_f = 0$  for both diodes.

## Solution:

For  $0 < V_i < 2V$ ,  $D_1$  &  $D_2$  are OFF as these are reverse biased.

Therefore,  $V_o = V_i$

For  $V_i > 2V$ ,  $D_1$  turns ON and

$$i_1 = (V_i - 2)/(10 + 10)$$



Also,  $V_o = i_1 R_2 + 2 = (V_i - 2)/20 \times 10 + 2$


$$= V_i/2 - 1 + 2 = V_i/2 + 1$$

(e.g. If  $V_i = 6V$ ,  $V_o = 6/2 + 1 = 4V$ )

For  $-4 < V_i < 0$ , both  $D_1$  &  $D_2$  are OFF  
&  $V_o = V_i$

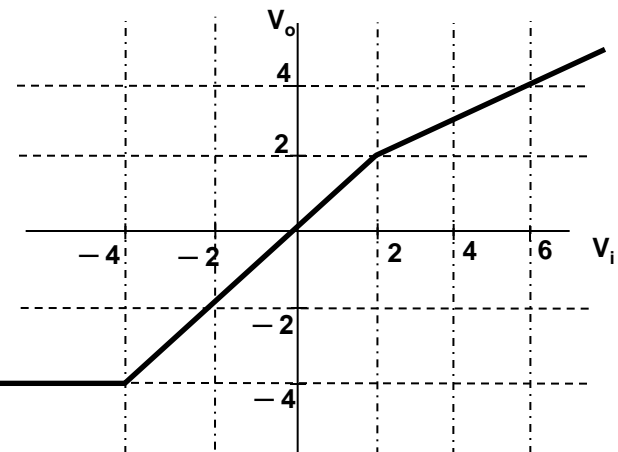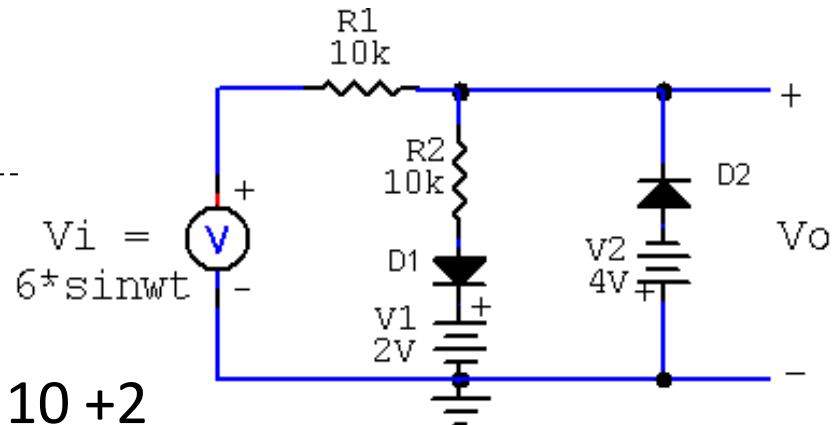
For  $V_i < -4V$ ,  $D_2$  turns ON and  $V_o = -4V$



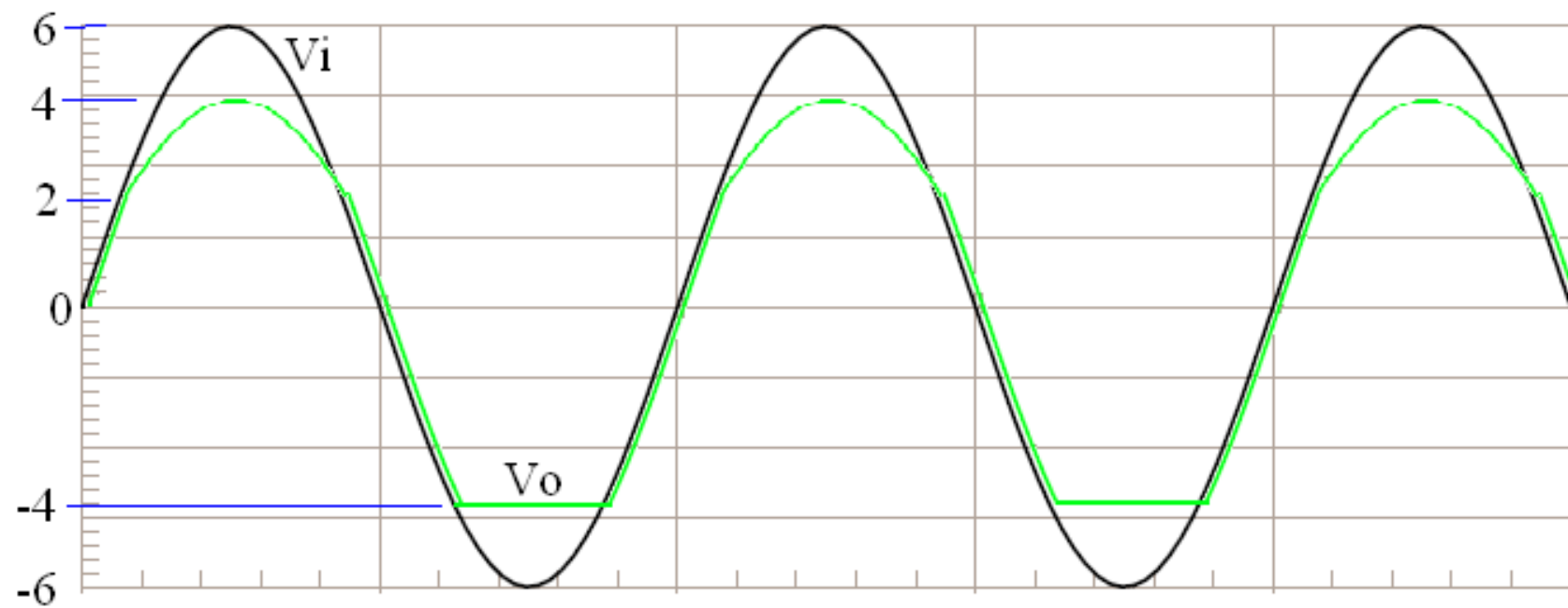
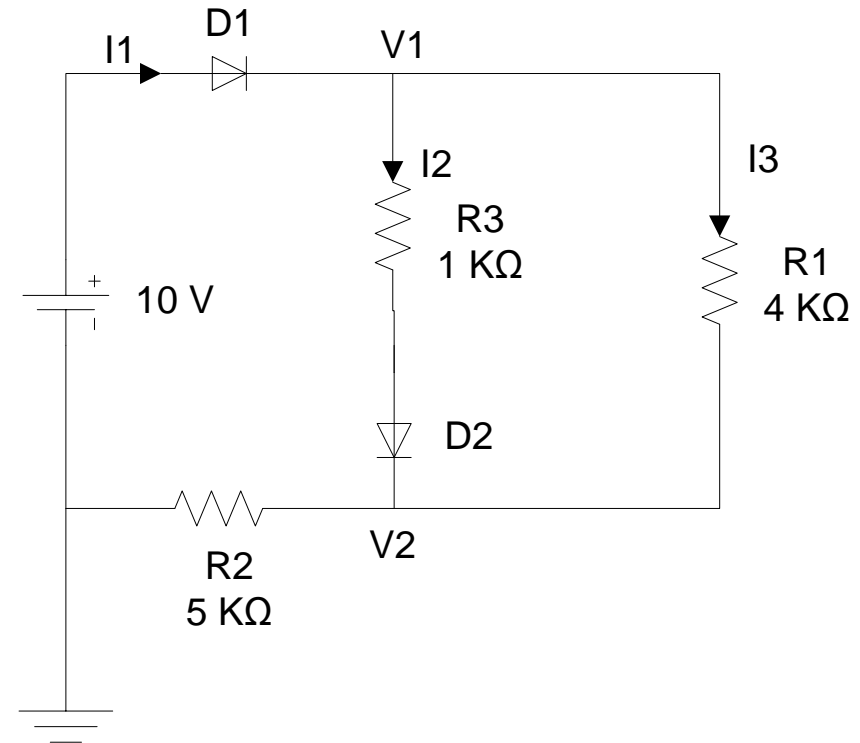
## Example 5

For the circuit shown, find the voltages  $V_1$  and  $V_2$  and the currents  $I_1$ ,  $I_2$  and  $I_3$ . Assume the diodes to be ideal with a forward voltage drop of  $0.7\text{ V}$ .



Answer: (D1 and D2 ON)

$$\begin{aligned} V_1 &= 9.3\text{ V} & V_2 &= 7.53\text{ V} \\ I_1 &= 1.51\text{ mA} & I_2 &= 1.07\text{ mA} \\ I_3 &= 0.44\text{ mA} \end{aligned}$$

Check to see what happens if you assume D1 is ON but D2 is OFF

Will get  $V_1 = 9.3\text{ V}$  &  $V_2 = 5.17$  which is clearly impossible as then D2 will be ON

What will be the states (ON/OFF) of the two diodes, D1 and D2?

Find the currents  $I_{D1}$  and  $I_{D2}$

Try all combinations of D1 and D2 ON/OFF. Only one combination will give logically consistent results. That one is the one which will be the correct choice

**ANSWER:**

D1 ON & D2 OFF

$I_{D1}=0.953 \text{ mA}$     $I_{D2}=0$

