

EE101: Electrical Sciences

Long-Assignment-2, Due date: Nov. 15, 2017

Analog Electronics

Question-1: The symbol of an npn-BJT (Bipolar Junction Transistor) is shown in Fig. 1(a). It has three terminals base (B), collector (C), and emitter (E). The DC characteristics of the BJT are given by

$$I_C = I_E = \beta I_B = I_S e^{\frac{V_{BE}}{\eta V_T}},$$

where I_S , η , β , and V_T are all constants.

Fig. 1(b) shows an amplifier using the npn-BJT. In this amplifier, the coupling capacitors C_c are very large. For a DC analysis assume the coupling capacitors are open circuited and for a small-signal analysis assume the coupling capacitors act as short circuits. In Fig. 1(b), $V_{dd} = 15\text{ V}$, $R_1 = 100\text{ k}\Omega$, $R_2 = 50\text{ k}\Omega$, $R_L = 5\text{ k}\Omega$, $\beta = 100$, and $R_E = 3\text{ k}\Omega$.

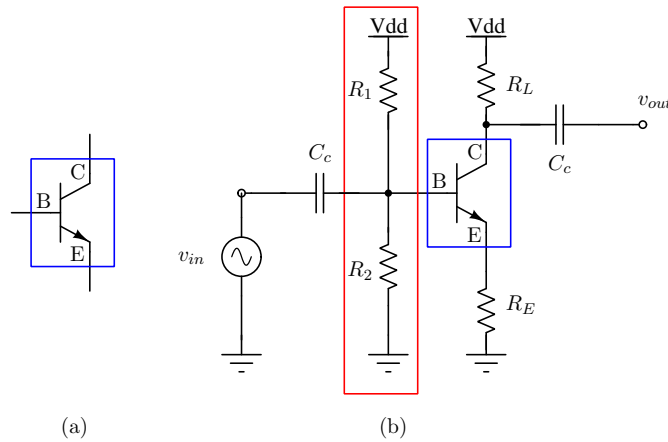


Figure 1: (a) The symbol of an npn-BJT, and (b) an amplifier using the BJT.

- Write the equations involving I_E and V_{BE} . (Do not try to solve these equations at this step).
- All silicon-based npn-BJTs maintain $V_{BE} = 0.7\text{ V}$ while conducting (reasons will be discussed in the class). Assuming $V_{BE} = 0.7\text{ V}$, solve the above equations to find V_E and I_E .
- What is the base voltage V_B ? Remember: $I_E = \beta I_B$ and some current can flow into the base terminal of the BJT.
- What is the collector voltage V_C ?
- What is the purpose of the resistive divider (R_1 and R_2) and the coupling capacitors?
- What is the voltage gain of this circuit? Remember: for small-signal analysis $v_{be} \neq 0.7\text{ V}$.

Polyphase Circuits/Magnetic Circuits

Question-2: Let $I_s = 2 \cos(10t)$ A in the circuit shown in Figure 2. Find the total energy stored at $t = 0$ if,

- (i) a-b is open circuited,
- (ii) a-b is short circuited.

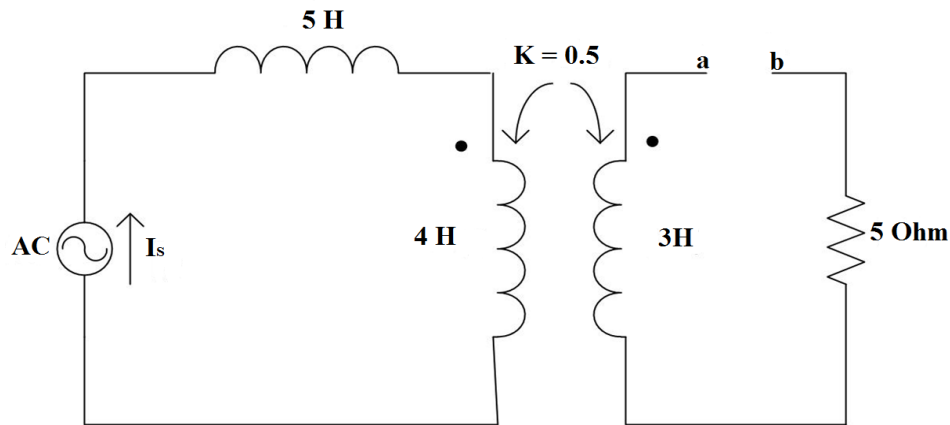


Figure 2

Question-3: An electromagnet of square cross section, shown in Figure 3, has a coil of 1500 turns. The inner and outer radii of the core are 10 cm and 12 cm respectively and the air gap is 1 cm. If the current in the coil is 4 A and the relative permeability of the core material is 1200, determine the flux density in the circuit (Core thickness is 2 cm).

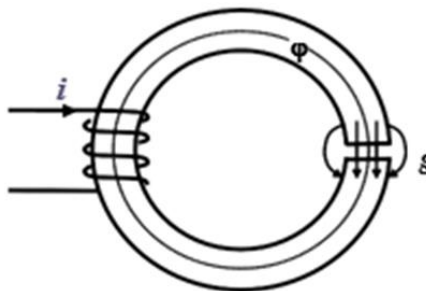


Figure 3: Magnetic circuit with airgap

Question-4: A three-phase, 400 V source supplies a load with an equivalent star impedance of $60 + j15 \text{ } \Omega$ per phase through a transmission line of impedance $0.3 + j1.0 \text{ } \Omega$ per phase. Compute:

- (i) the line current,
- (ii) the load voltage,
- (iii) the power, the reactive power and the VA consumed by the load,
- (iv) the power and the reactive power loss in the line and
- (v) the power, the reactive power and the VA supplied by the source.