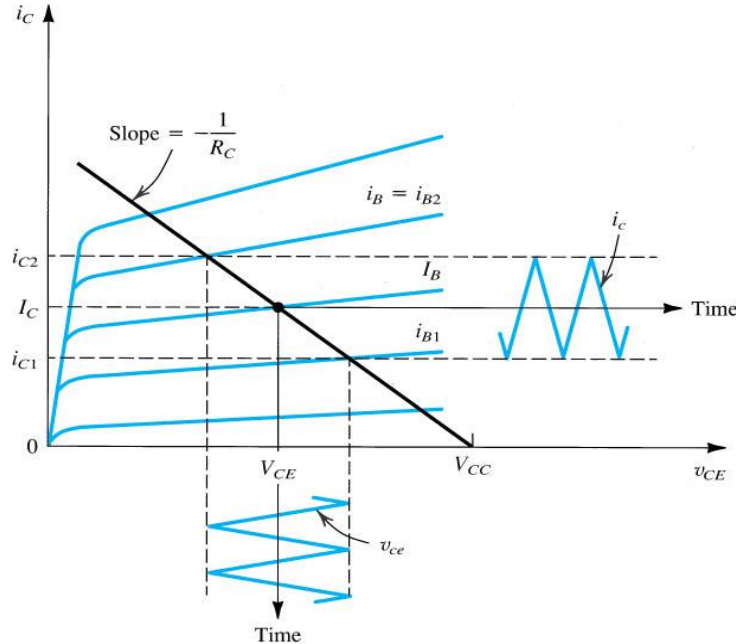


# **Bipolar Junction Transistors - III**

## **(BJT-III )**

### **Analyzing Transistor Amplifiers**

# Transistor as an Amplifier




- Choose a proper Q-point
- Make sure that the input is such that the transistor does not get driven outside its active region

## To Analyze a BJT Amplifier –

- Short all the bypass capacitors and connect power supplies (i.e.  $V_{CC}$ ,  $V_{BB}$  etc.) to ground. *From the point of view of AC signals, capacitors are SHORT-CIRCUITS and the power supply points are equivalent to GROUND.*
- Replace transistor with its *small signal equivalent model*

# Basic BJT Amplifier

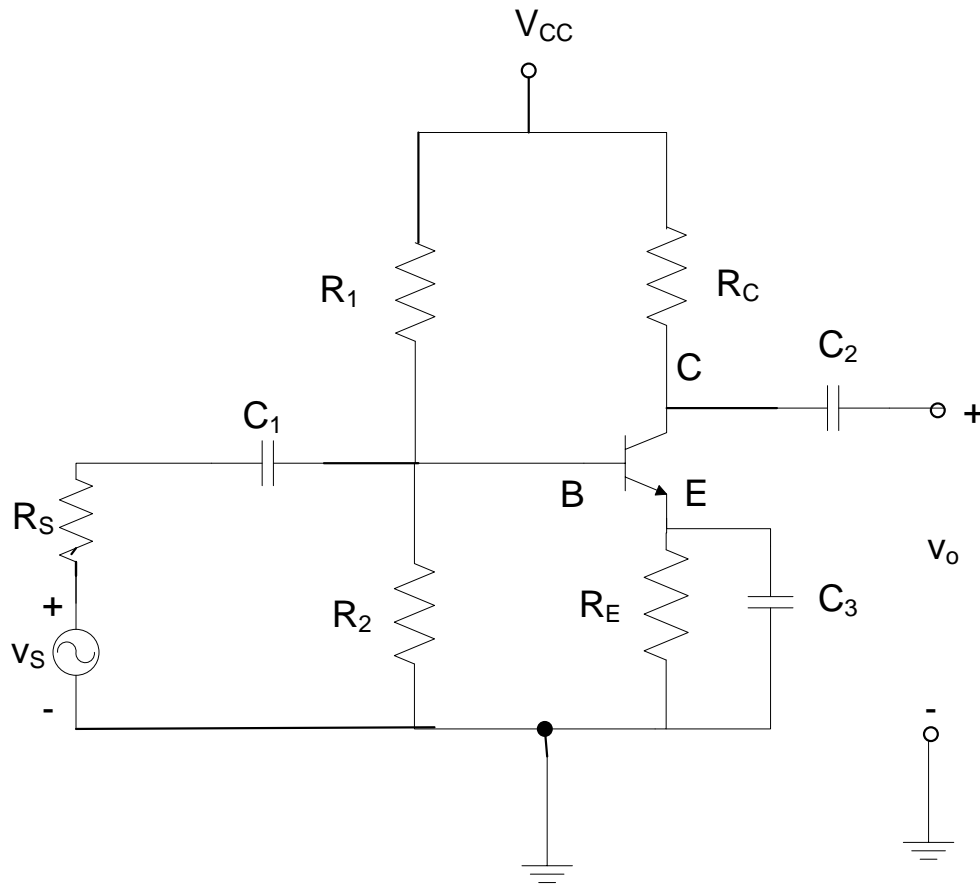

$C_1, C_2$  - Coupling Capacitors

$C_3$  - Emitter Bypass Capacitor

$C_1, C_2, C_3$  values are chosen high enough so that under ac these act as a short circuit.

The coupling capacitor ( $C_1, C_2$ ) is used to pass the ac input signal and block the dc voltage from the preceding circuit. (AC-Coupled Amplifier)

This prevents dc in the circuitry on the left of the coupling capacitor from affecting the bias.



The coupling capacitor also blocks the bias of the transistor from affecting the input signal source.

*Special DC-Coupled Amplifiers needed if you want to amplify a signal which has a DC component!*

The emitter bypass capacitor ( $C_3$ ) is used to bypass the  $R_E$  and short circuits the ac signal through  $C_3$  since voltage gain decreases because of presence of  $R_E$

## **A.C. Equivalent Circuit is obtained by :**

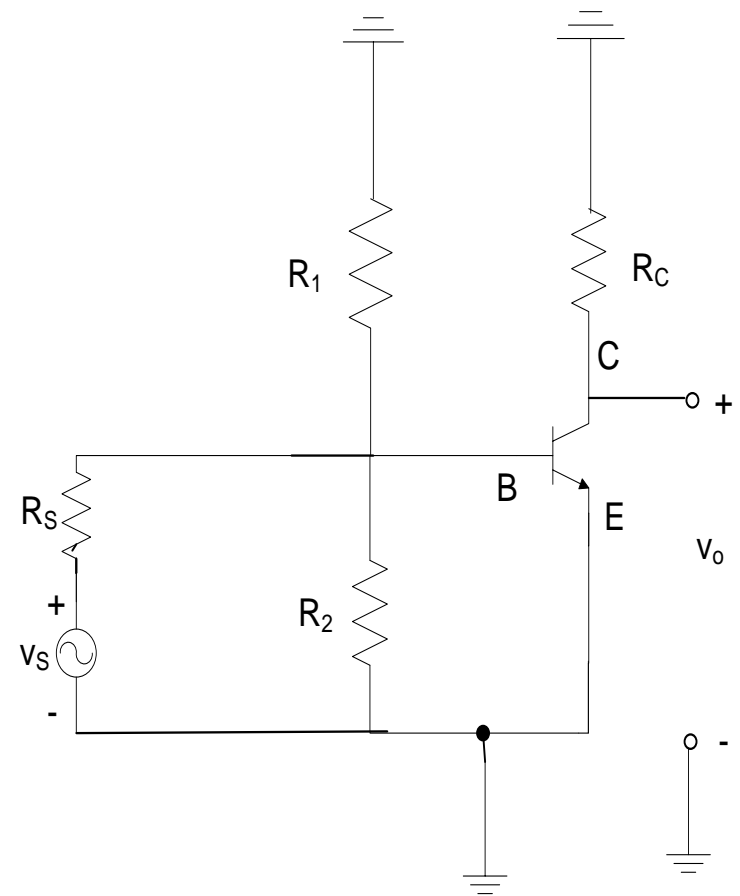
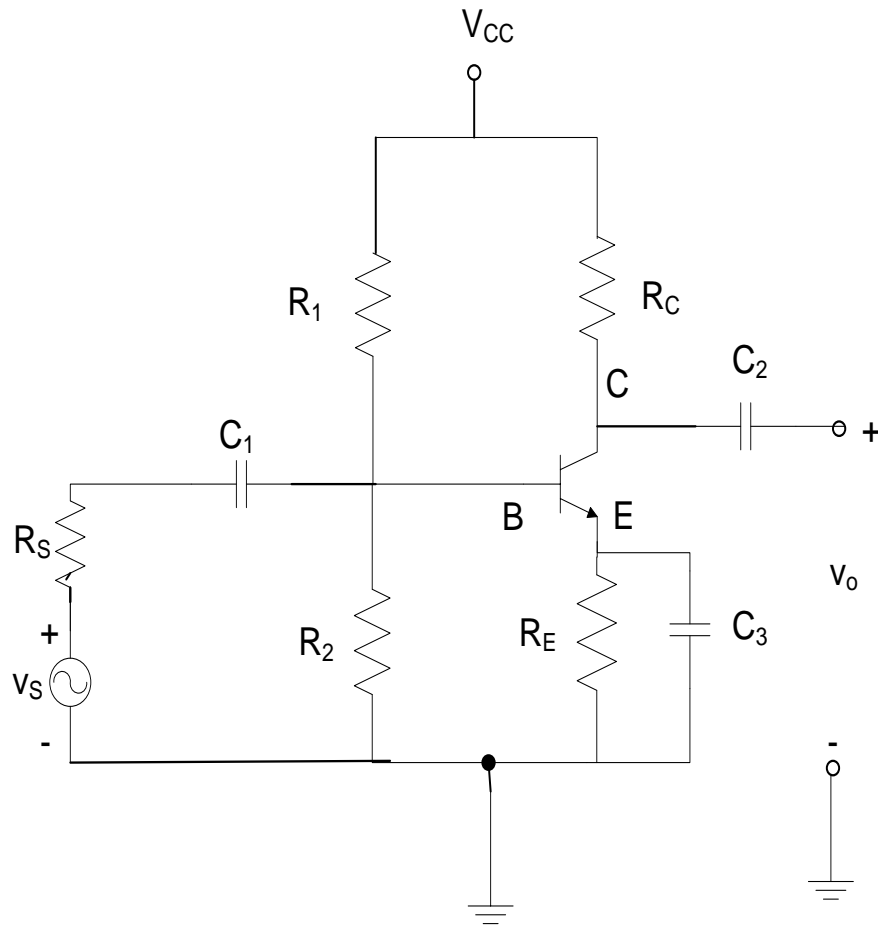
1. Setting all D.C. sources to 0 and replacing them by a short circuit equivalent
2. Replacing all capacitors by a short circuit equivalent
3. Removing all elements bypassed by the short circuit equivalents introduced in steps 1 and 2
4. Redrawing the network in a more convenient and logical form



**Basic BJT Amplifier**



**A.C. Equivalent Circuit**

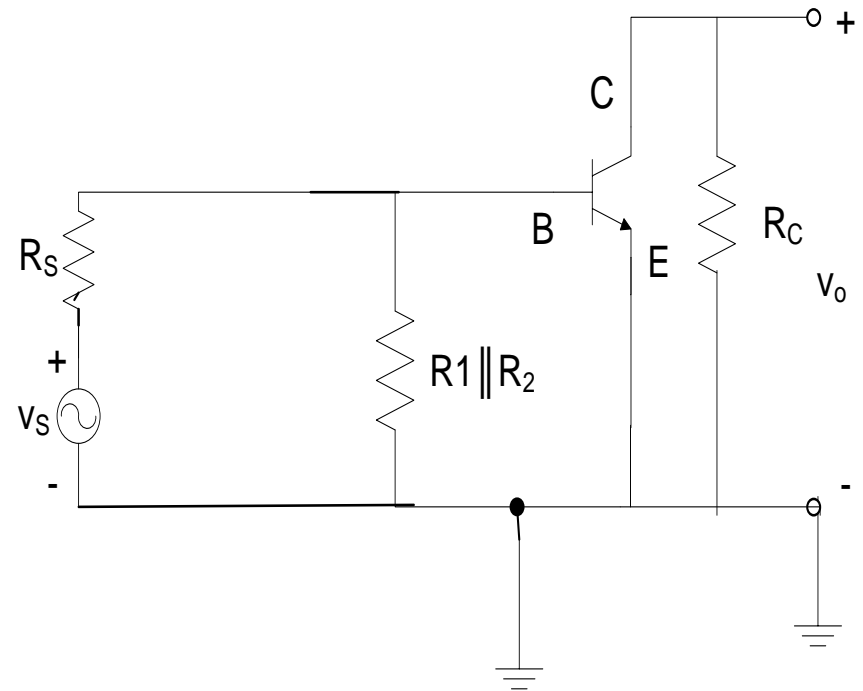
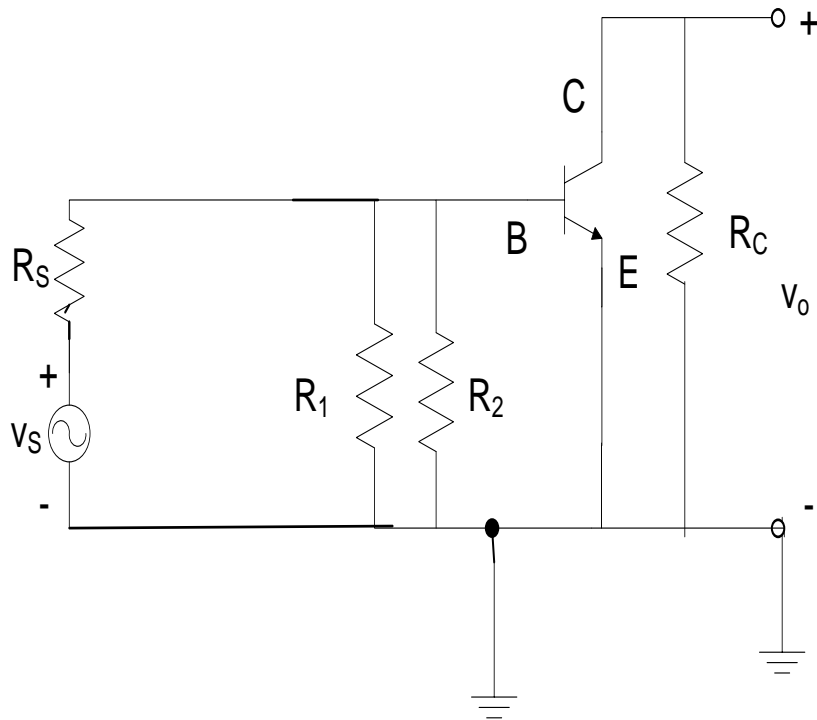


Simplify circuit by replacing  $R_1$  and  $R_2$  with  $R_B$   $R_B = R_1 \parallel R_2$


We now replace the transistor with its *small signal equivalent circuit*.  
The details of this would be available from the manufacturer's specifications for the transistor.
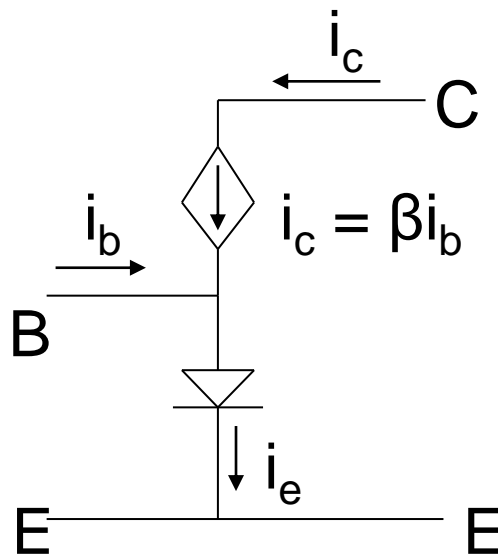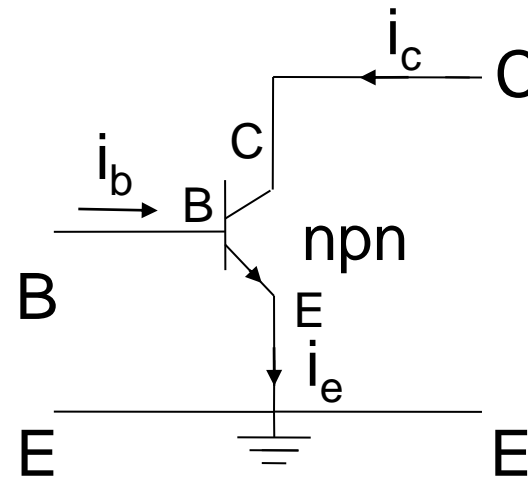
# Small Signal AC Equivalent Model for an NPN Transistor used in the Common Emitter Configuration

(Reverse the current and diode directions for PNP)



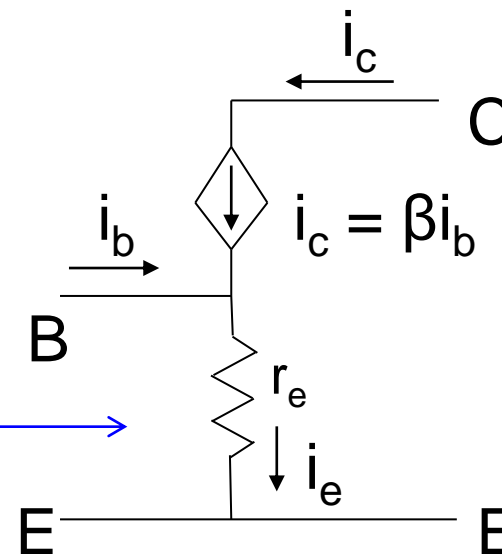Replace BE diode by its equivalent resistance  $r_e$






$$r_e = \frac{V_T}{I_E} = \frac{26 \text{ mV}}{I_E}$$

$I_E$  is the DC Emitter Current


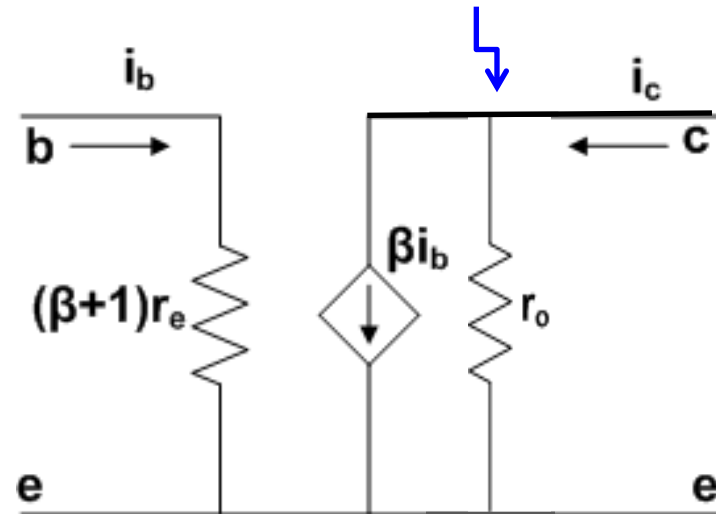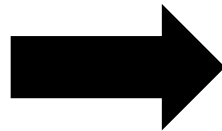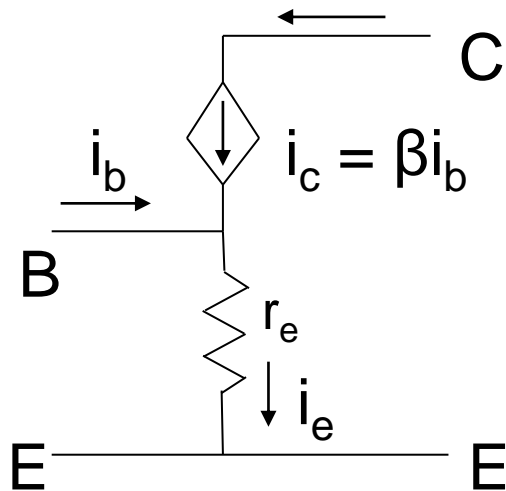
# Small Signal AC Equivalent Model for an NPN Transistor used in the Common Emitter Configuration





This is known as the  $r_e$  Model for the Common Emitter configuration

$r_o$  large (typically 40-50 K $\Omega$  and may be ignored in simplified analysis! (When can we ignore it?))

# Using the $r_e$ small signal model (for AC signal analysis)

(Without Source and Load Resistances)

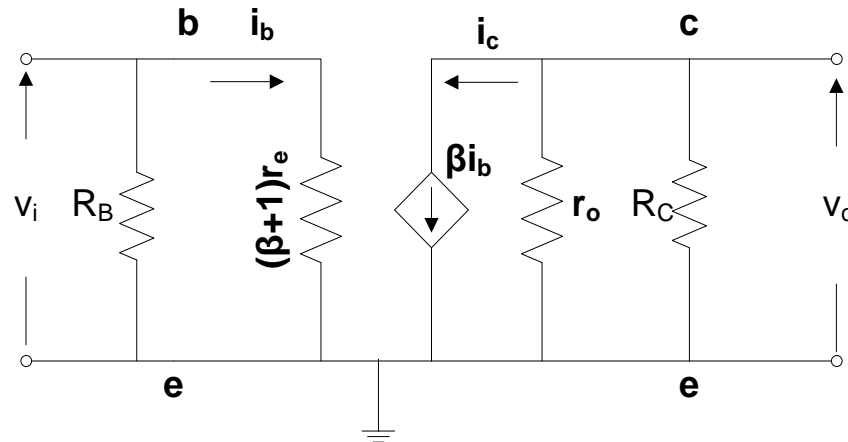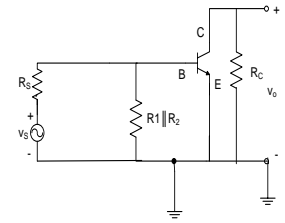

$$i_b = \frac{v_i}{(\beta+1)r_e}$$



$$\frac{v_o}{r_o \parallel R_C} = -\beta i_b$$

$$A_v = \frac{v_o}{v_i} = -\left(\frac{\beta}{\beta+1}\right) \frac{R_C \parallel r_o}{r_e}$$

For  $r_o \gg R_C$  and  $\beta \gg 1$   $A_v = -\frac{R_C}{r_e}$

Note the phase reversal between input and output

(Without Source and Load Resistances)

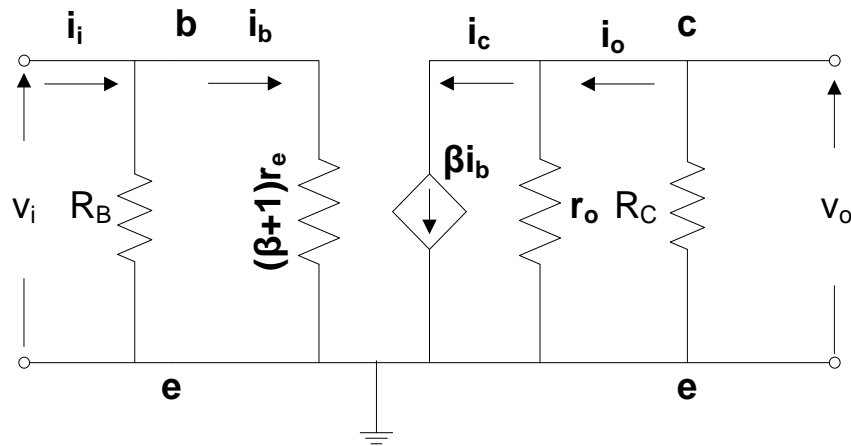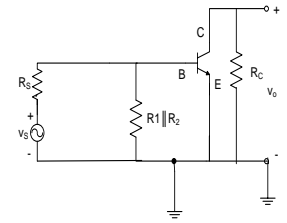


Output Impedance

$$Z_o = R_C \parallel r_o$$

$$i_i = \frac{v_i}{[R_B \parallel (\beta + 1)r_e]} \Rightarrow \text{Input Impedance} \quad Z_i = \frac{v_i}{i_i} = R_B \parallel (\beta + 1)r_e$$

$$\left. \begin{aligned} i_b &= i_i \frac{R_B}{R_B + (\beta + 1)r_e} \\ i_o &= \beta i_b \frac{r_o}{r_o + R_C} \end{aligned} \right\} \text{Current Gain} \quad A_i = \frac{i_o}{i_i} = \beta \left( \frac{R_B}{R_B + (\beta + 1)r_e} \right) \left( \frac{r_o}{r_o + R_C} \right)$$

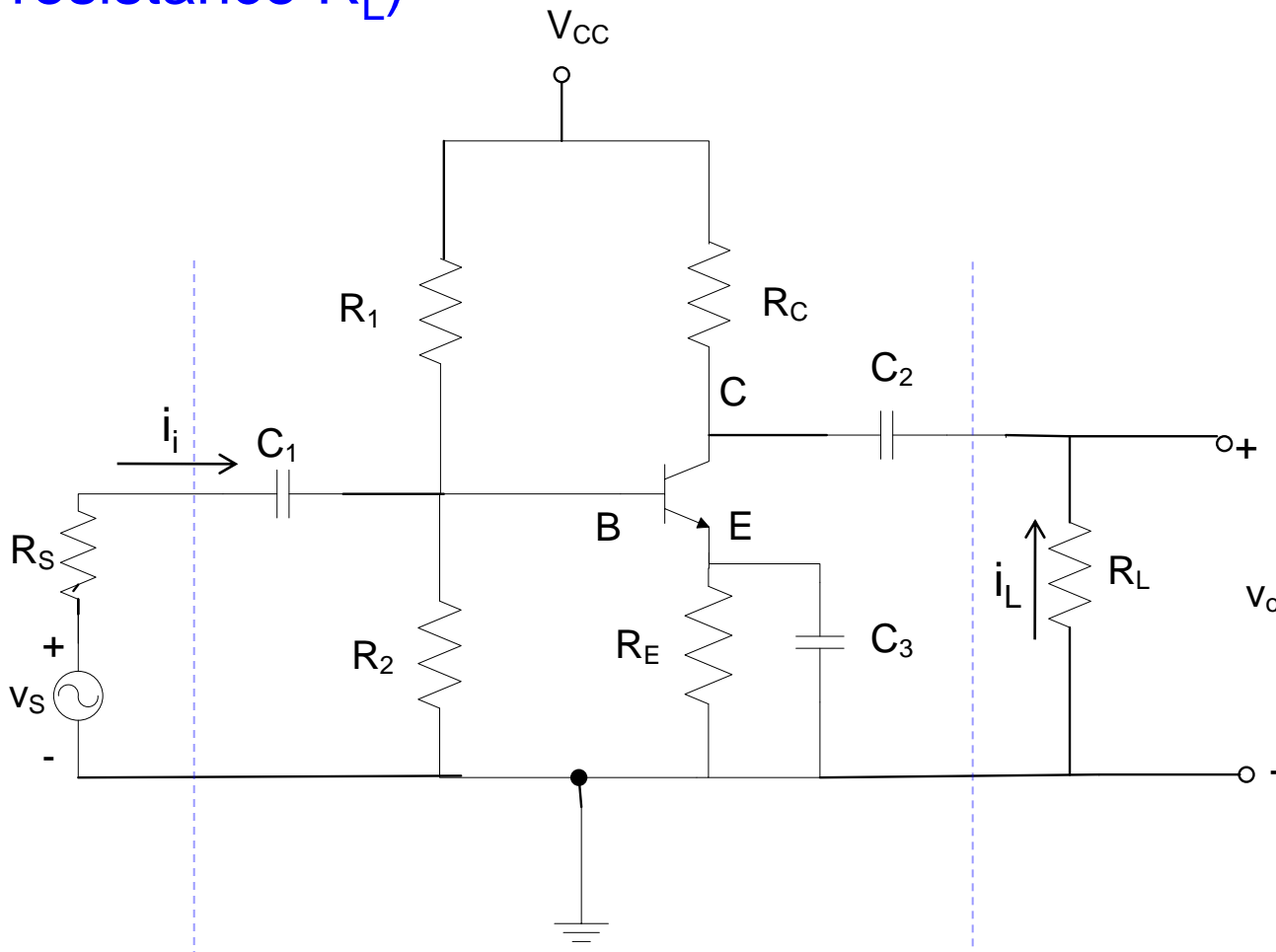
## Basic BJT Amplifier (with source resistance $R_S$ and load resistance $R_L$ )



$$A_V^* = \frac{v_o}{v_S}$$

*Note that the circuit between the dotted lines is what we have analyzed before*


# Finding $A_v$ Voltage Gain

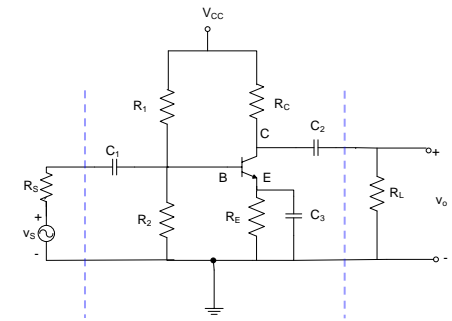

1. Use the same procedure as before except you now have to add  $R_s$  and  $R_L$  to the circuit

**Try this approach yourself!**

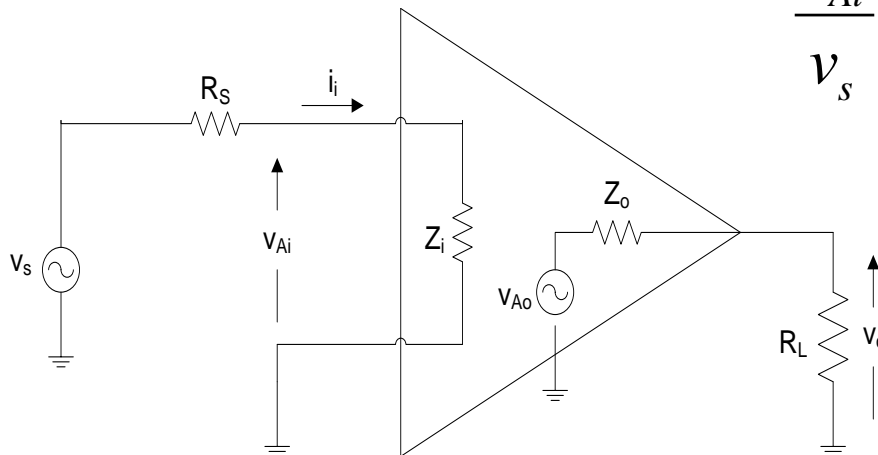2. Use the results we got for  $A_v$ ,  $Z_i$  and  $Z_o$  for the earlier case. **This approach is given below.**




$$\frac{v_{Ai}}{v_s} = \frac{Z_i}{Z_i + R_s}$$



$$\frac{v_o}{v_{Ao}} = \frac{R_L}{R_L + Z_o}$$

$$\begin{aligned} A_v^* &= \frac{v_o}{v_s} = \frac{v_o}{v_{Ao}} \frac{v_{Ao}}{v_{Ai}} \frac{v_{Ai}}{v_s} \\ &= \frac{R_L}{R_L + Z_o} A_v \frac{Z_i}{Z_i + R_s} \end{aligned}$$

# Fixed Bias Transistor Amplifier

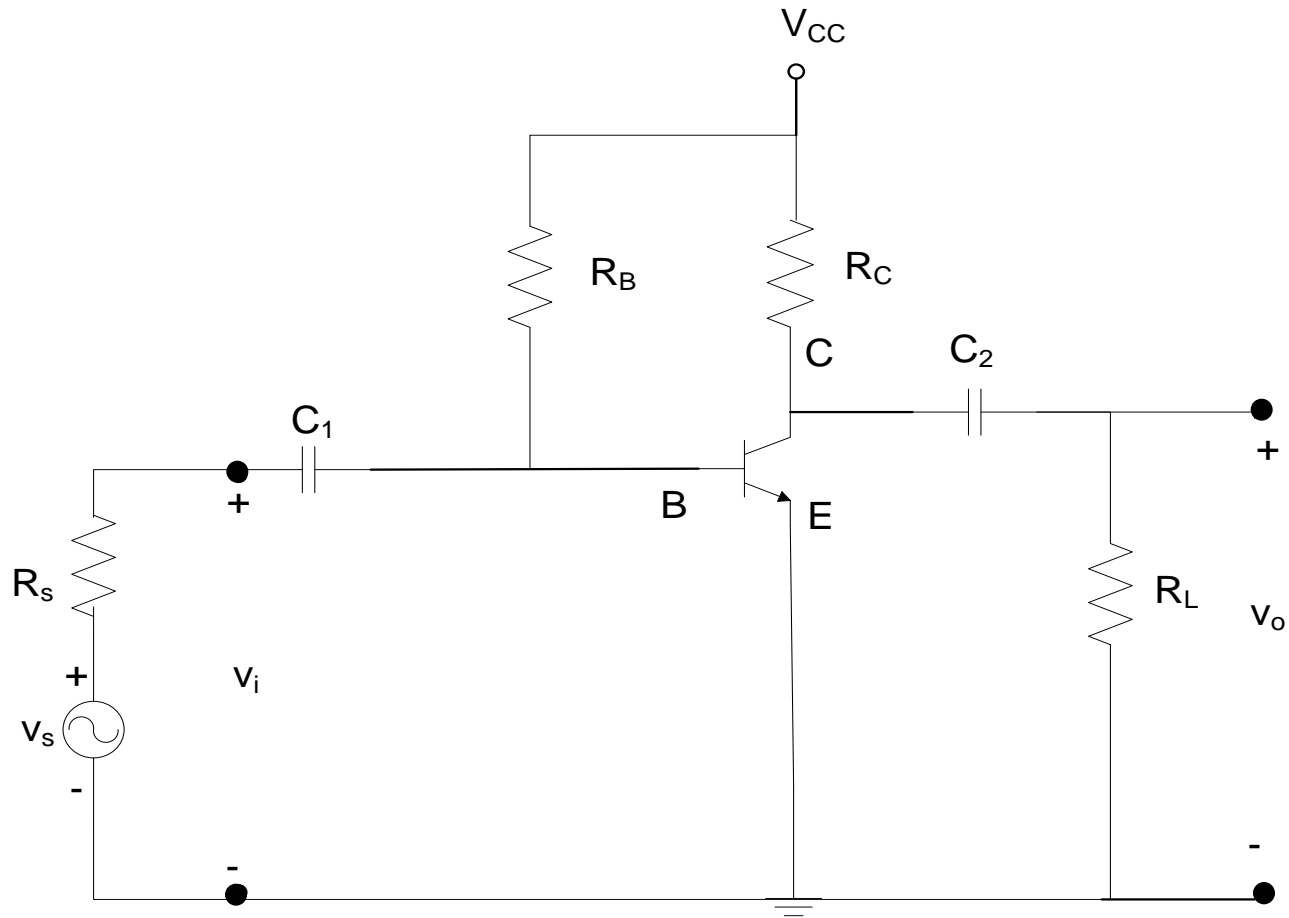


# Fixed Bias Transistor Amplifier

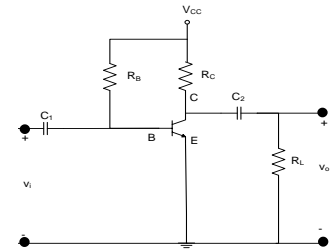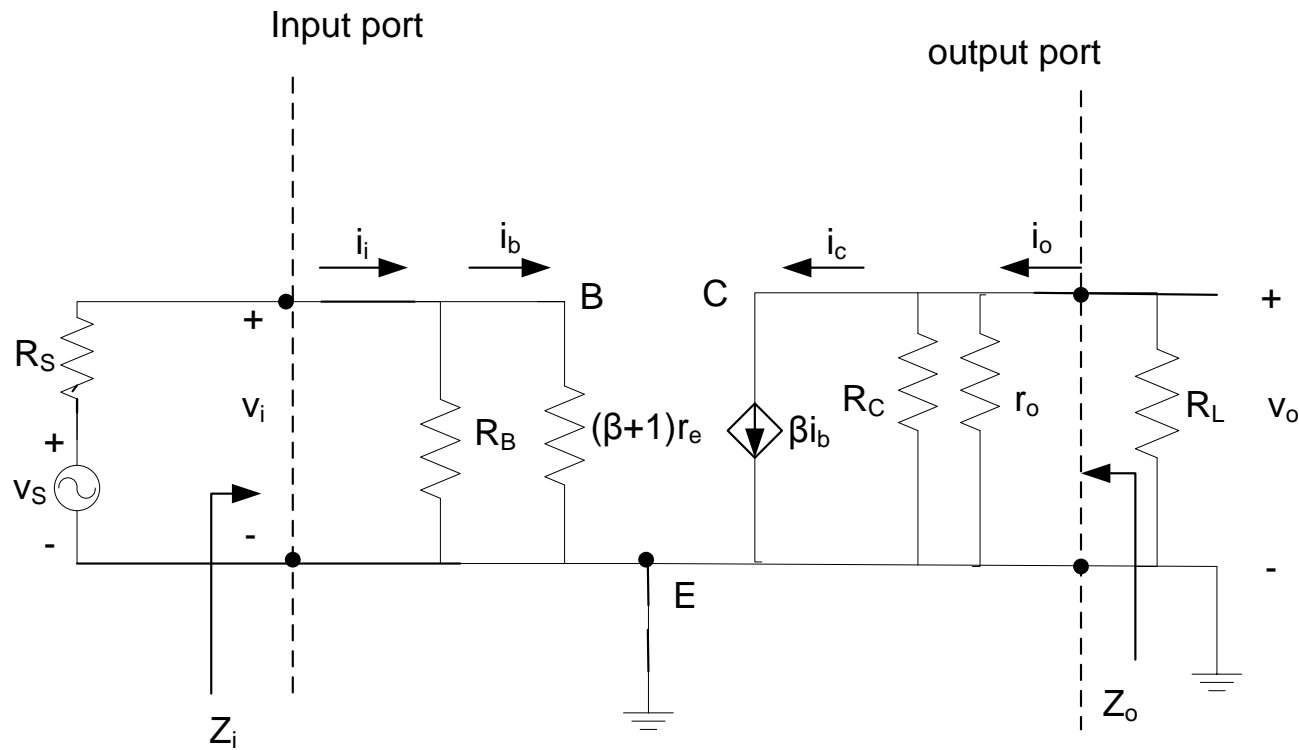

$$Z_i = R_B \parallel (\beta + 1)r_e$$

$$Z_o = R_C \parallel r_o \cong R_C \quad \text{if } r_o \gg R_C$$

# Fixed Bias Transistor Amplifier

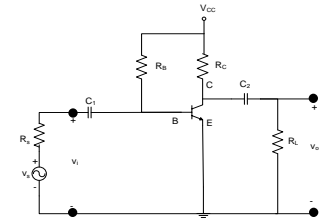


$$i_b = \left( \frac{v_s}{R_s + R_B \parallel (\beta + 1)r_e} \right) \left( \frac{R_B}{R_B + (\beta + 1)r_e} \right)$$

$$v_o = -\beta i_b (R_C \parallel r_o \parallel R_L) \cong -\beta i_b (R_C \parallel R_L)$$




$$A_V = \frac{v_o}{v_s} = - \left( \frac{\beta (R_C \parallel R_L)}{R_s + R_B \parallel (\beta + 1)r_e} \right) \left( \frac{R_B \parallel (\beta + 1)r_e}{(\beta + 1)r_e} \right)$$
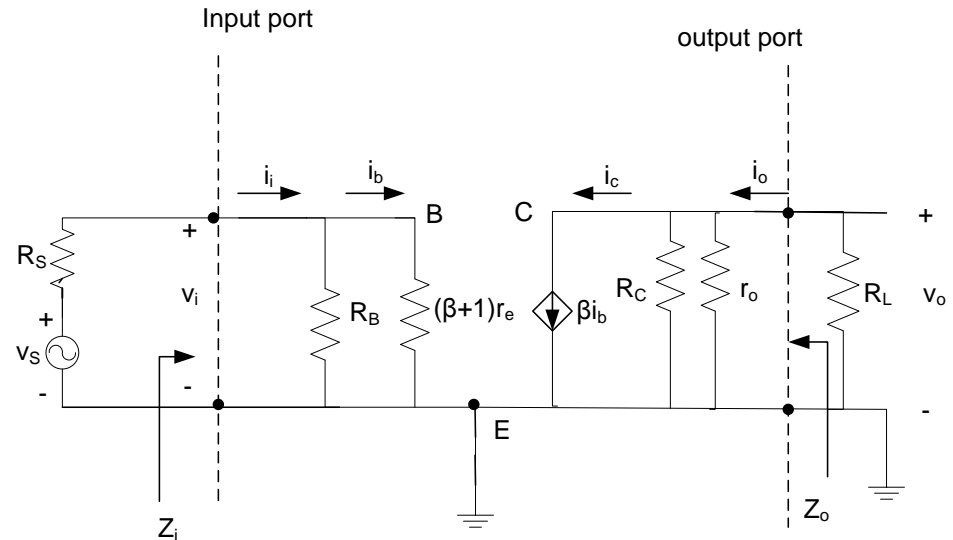
$$\cong - \frac{R_C \parallel R_L}{r_e} \quad \text{for} \quad R_B \parallel (\beta + 1)r_e \gg R_s$$





# Emitter and Collector Feedback Bias

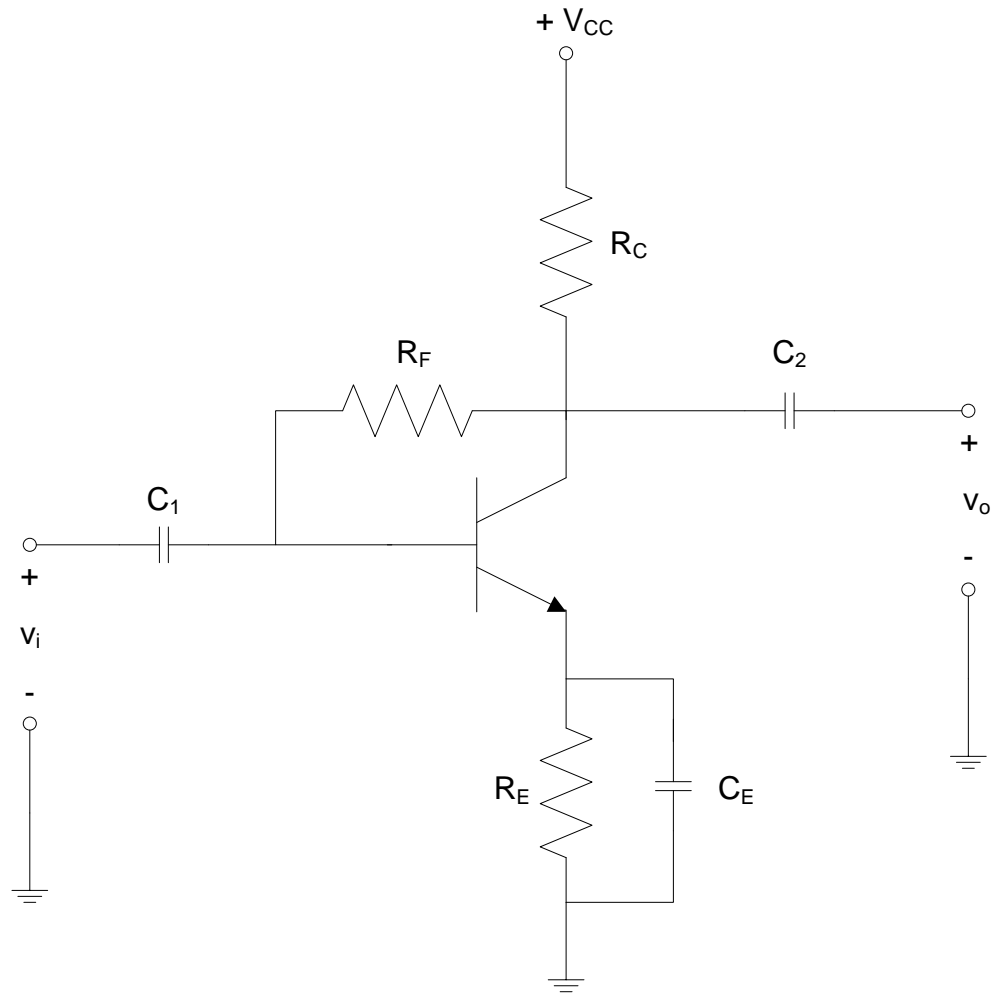

# Emitter and Collector Feedback Bias

## Voltage Gain Calculation

$$i_b = \frac{v_i}{(\beta + 1)r_e}$$

$$\frac{v_i - v_o}{R_F} - \frac{v_o}{r_o \parallel R_C} = \beta i_b = \frac{\beta}{\beta + 1} \frac{v_i}{r_e}$$

We can of course solve this to get the exact gain  $A_v = v_o/v_i$



Assuming  $\beta \gg 1$  and  $r_o \gg R_C$ , we get

$$-v_o \left[ \frac{1}{R_F} + \frac{1}{R_C} \right] = v_i \left[ \frac{1}{r_e} - \frac{1}{R_F} \right]$$

Since typically,  $r_e \ll R_F$

$$A_v = \frac{v_o}{v_i} \cong -\frac{R_F \parallel R_C}{r_e} \cong -\frac{R_C}{r_e}$$

For  
 $R_F \gg R_C$

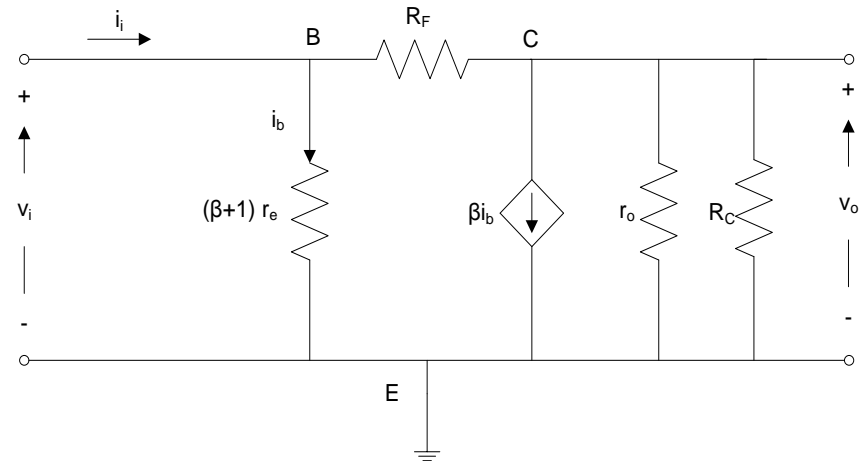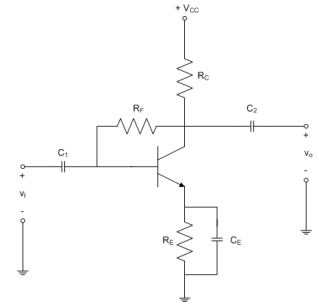

# Emitter and Collector Feedback Bias



## Calculating the Input Impedance

$$i_i = \frac{v_i}{(\beta + 1)r_e} + \frac{v_i - v_o}{R_F}$$

$$\cong v_i \left[ \frac{1}{\beta r_e} + \frac{1}{R_F} + \frac{R_C}{R_F r_e} \right]$$
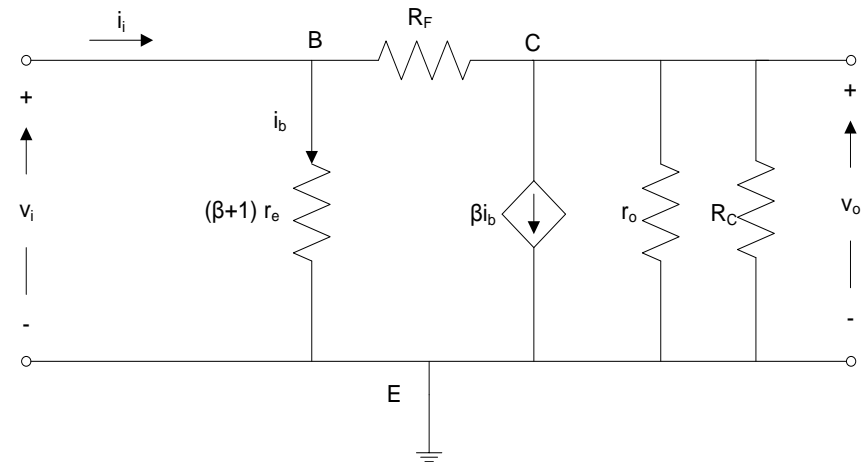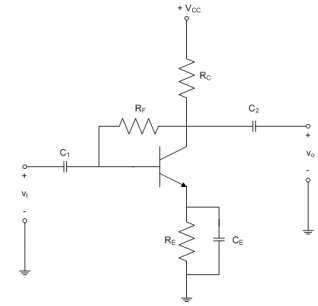
## Input Impedance

$$Z_i = \frac{v_i}{i_i} \cong \frac{1}{\left[ \frac{1}{\beta r_e} + \frac{1}{R_F} + \frac{R_C}{R_F r_e} \right]} \cong \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_F}}$$



# Emitter and Collector Feedback Bias

## Calculating the Output Impedance

We do this as  $Z_o = V_{oc} / I_{sc}$

$V_{oc} = v_o = A_v v_i$  and then use the following circuit to get  $I_{sc}$  **Ignore  $r_o$**



$$I_{sc} = \frac{v_i}{R_F} - \beta i_b = \frac{v_i}{R_F} - \frac{\beta}{\beta + 1} \frac{v_i}{r_e}$$

$$\cong -\frac{v_i}{r_e}$$


Using  $A_v = -\frac{R_C \parallel R_F}{r_e}$  we get

**Output Impedance**  $Z_o = R_C \parallel R_F$

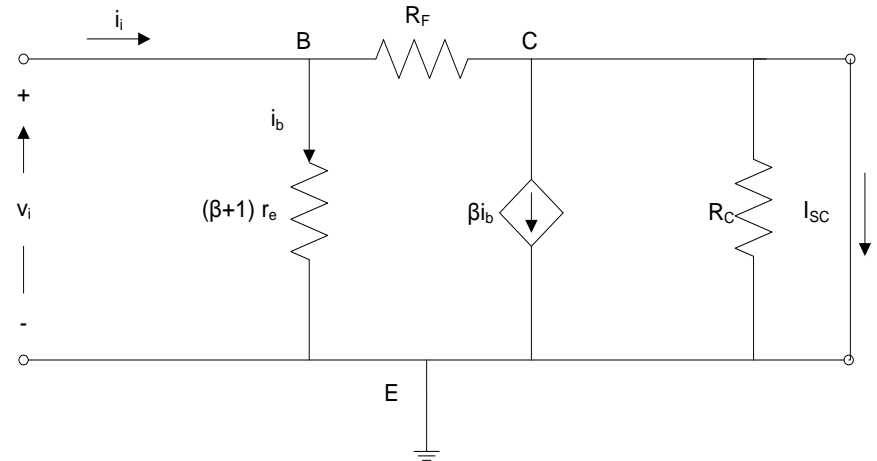
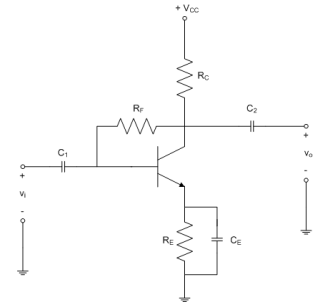
**or**  $Z_o = R_C \parallel r_o \parallel R_F$  **if we take  $r_o$  into account**


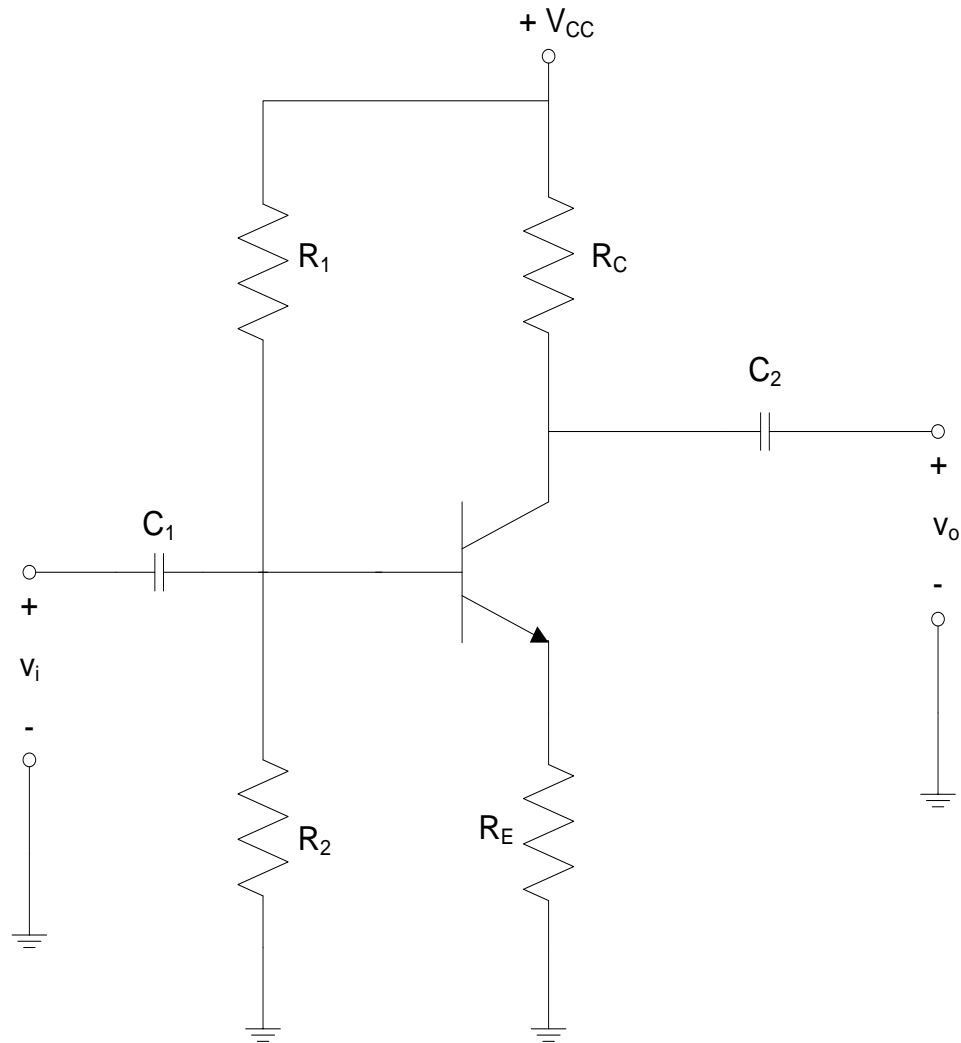
# Amplifier with Un-bypassed Emitter Resistance


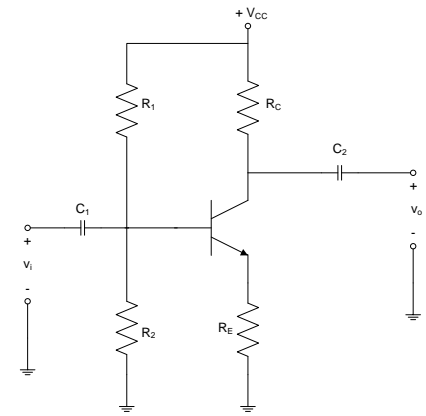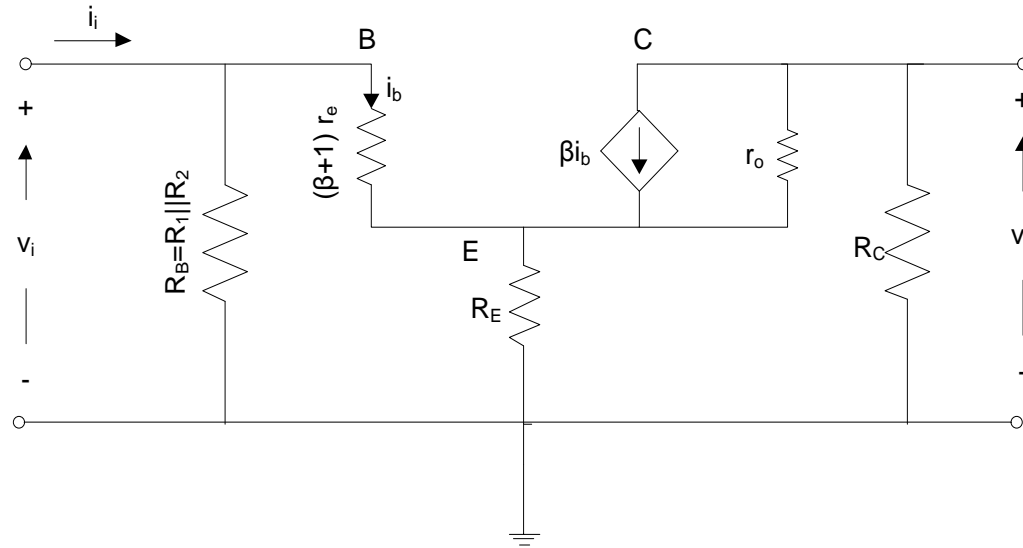
# Amplifier with Un-bypassed Emitter Resistance





$$v_i = (\beta + 1)i_b r_e + (\beta + 1)i_b R_E \quad v_o = -\beta i_b R_C \quad \text{Neglecting } r_o$$

Voltage Gain

$$A_V = \frac{v_o}{v_i} = -\left(\frac{\beta}{\beta + 1}\right) \frac{R_C}{r_e + R_E} \cong -\frac{R_C}{r_e + R_E} \cong -\frac{R_C}{R_E}$$

Note that voltage gain reduces compared to the circuit where the emitter resistance has been bypassed using a capacitor!
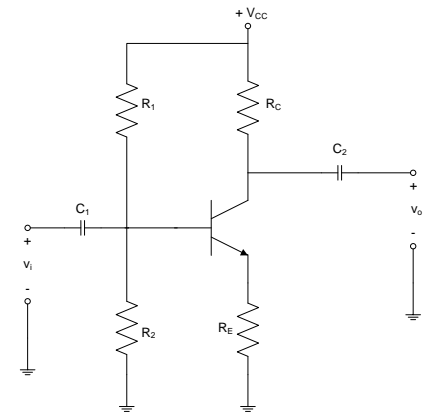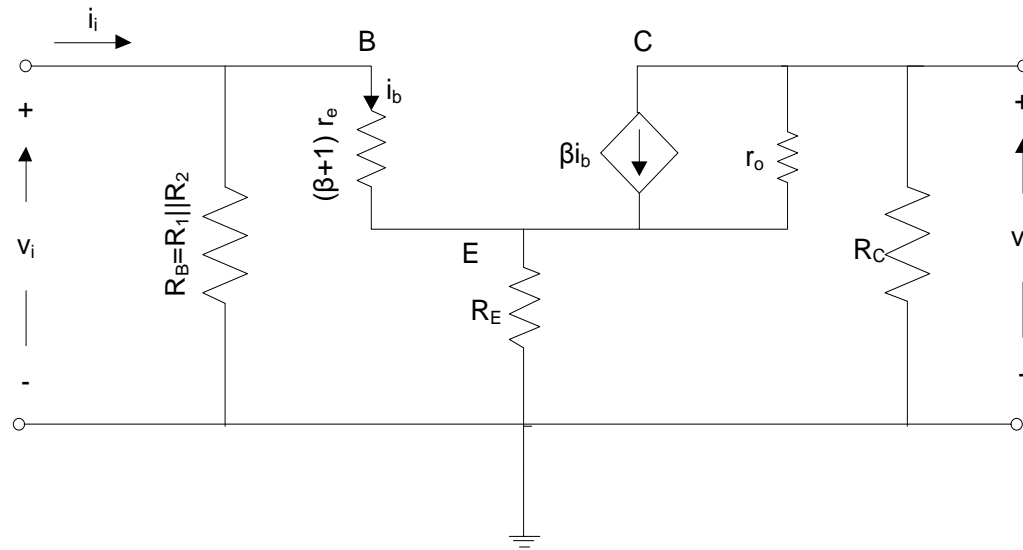
# Amplifier with Un-bypassed Emitter Resistance




Output Impedance  $Z_O = R_C$  (neglecting  $r_o$ )

$$v_i = (\beta + 1)i_b r_e + (\beta + 1)i_b R_E \Rightarrow \frac{v_i}{i_b} = (\beta + 1)(r_e + R_E) = Z_{BE} \quad (\text{say})$$

Input Impedance  $Z_i = R_B \parallel Z_{BE} = R_B \parallel [(\beta + 1)(r_e + R_e)]$   
(higher than before)

# Emitter Follower Circuit

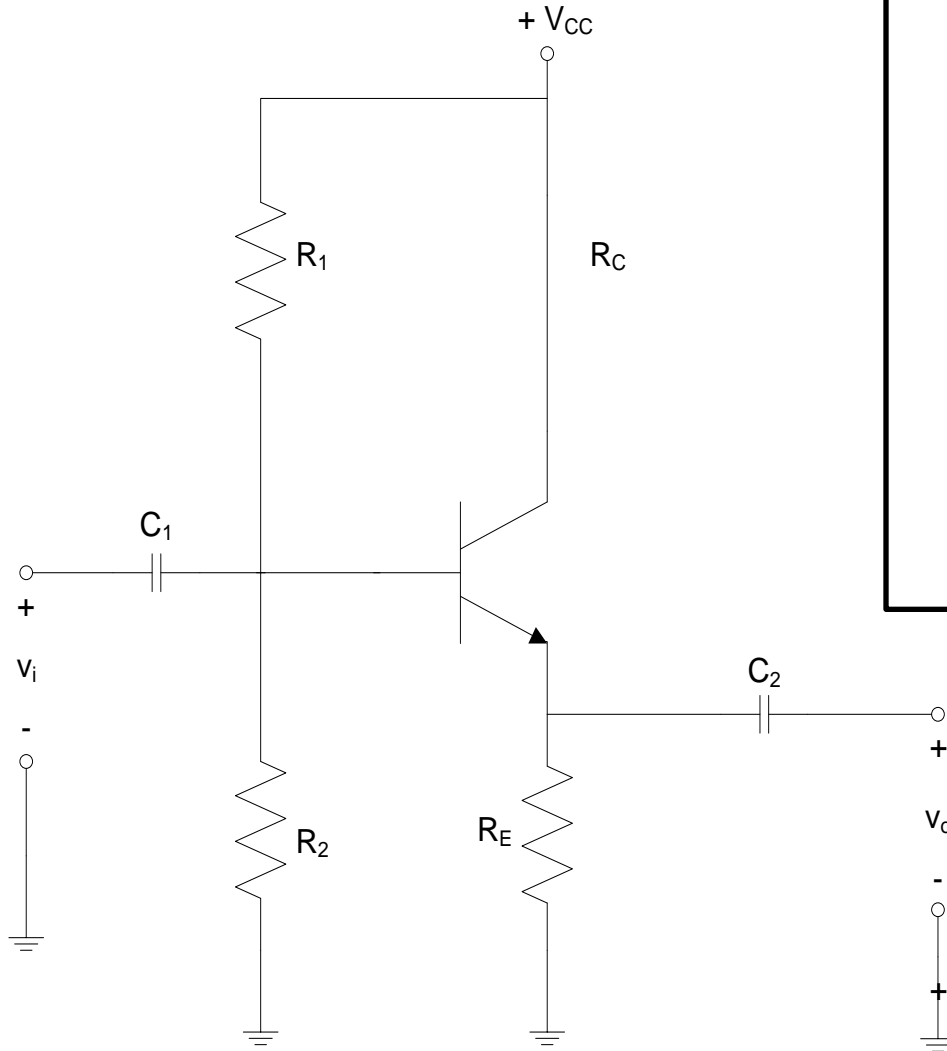

## Bias (Q-Point)

$$R_B = R_1 \parallel R_2$$

$$V_{BB} = V_{CC} R_2 / (R_1 + R_2)$$

$$I_B = \frac{V_{BB} - 0.7}{R_B + (\beta + 1)R_E}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - (\beta + 1)I_B R_E$$




# Emitter Follower Circuit

Simplified equivalent circuit omitting  $r_o$

$$v_i = i_b (\beta + 1) r_e + (\beta + 1) i_b R_E$$

$$= (\beta + 1) i_b (r_e + R_E)$$

$$v_o = (\beta + 1) i_b R_E$$

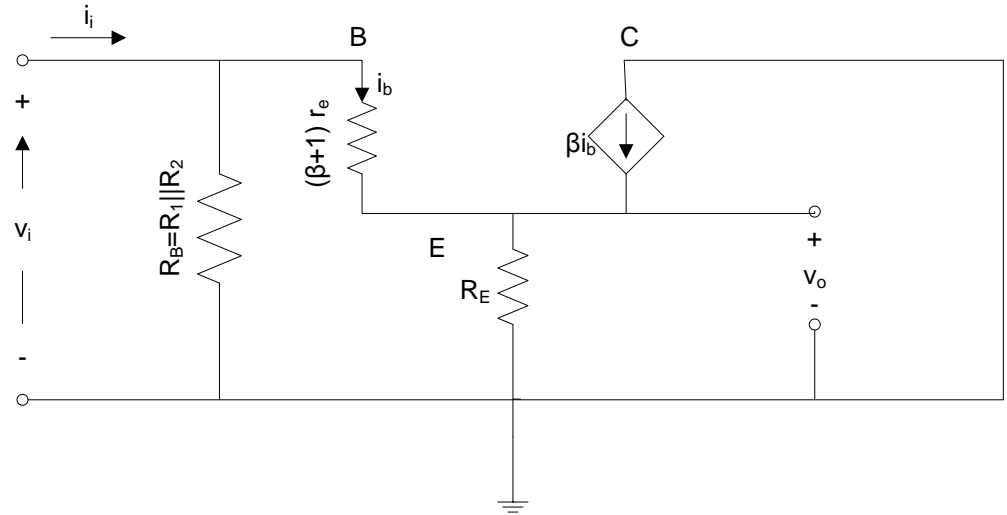

## Voltage Gain

$$A_v = \frac{v_o}{v_i} = \frac{R_E}{r_e + R_E} < 1$$

## Input Impedance

$$Z_i = \frac{v_i}{i_i} = R_B \parallel [(\beta + 1)(r_e + R_E)]$$

$$V_{OC} = v_o = v_i \frac{R_E}{r_e + R_E}$$

$$I_{SC} = (\beta + 1) i_{b,SC}$$

$$i_{b,SC} = \frac{v_i}{(\beta + 1) r_e}$$

## Output Impedance

$$Z_o = \frac{V_{OC}}{I_{SC}} = r_e \parallel R_E \cong r_e$$

# Why use the Emitter-Follower Configuration?


The Emitter Follower circuit does not provide any voltage gain (Gain  $\approx 1$ ) but is useful for impedance matching purposes.

For example, as an interface between a high-output impedance sensor and a low input impedance detection circuit.

This is because it has a high input impedance and a low output impedance – recall that impedances should be matched for maximum power transfer.
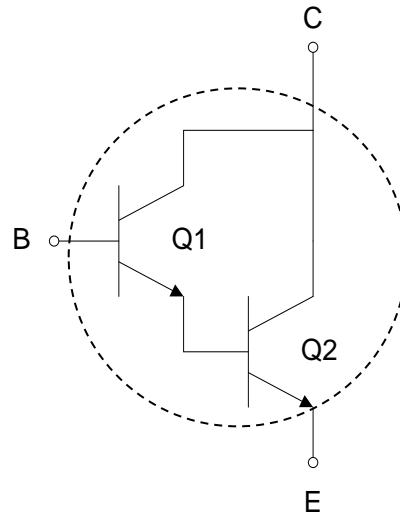
# Darlington Connection

How can we get very large values of  $\beta$ ?



$$\beta_{\text{overall}} = \beta_1 \beta_2 + \beta_1 + \beta_2$$


$$\beta_{\text{overall}} \approx \beta_1 \beta_2$$

Darlington Pair

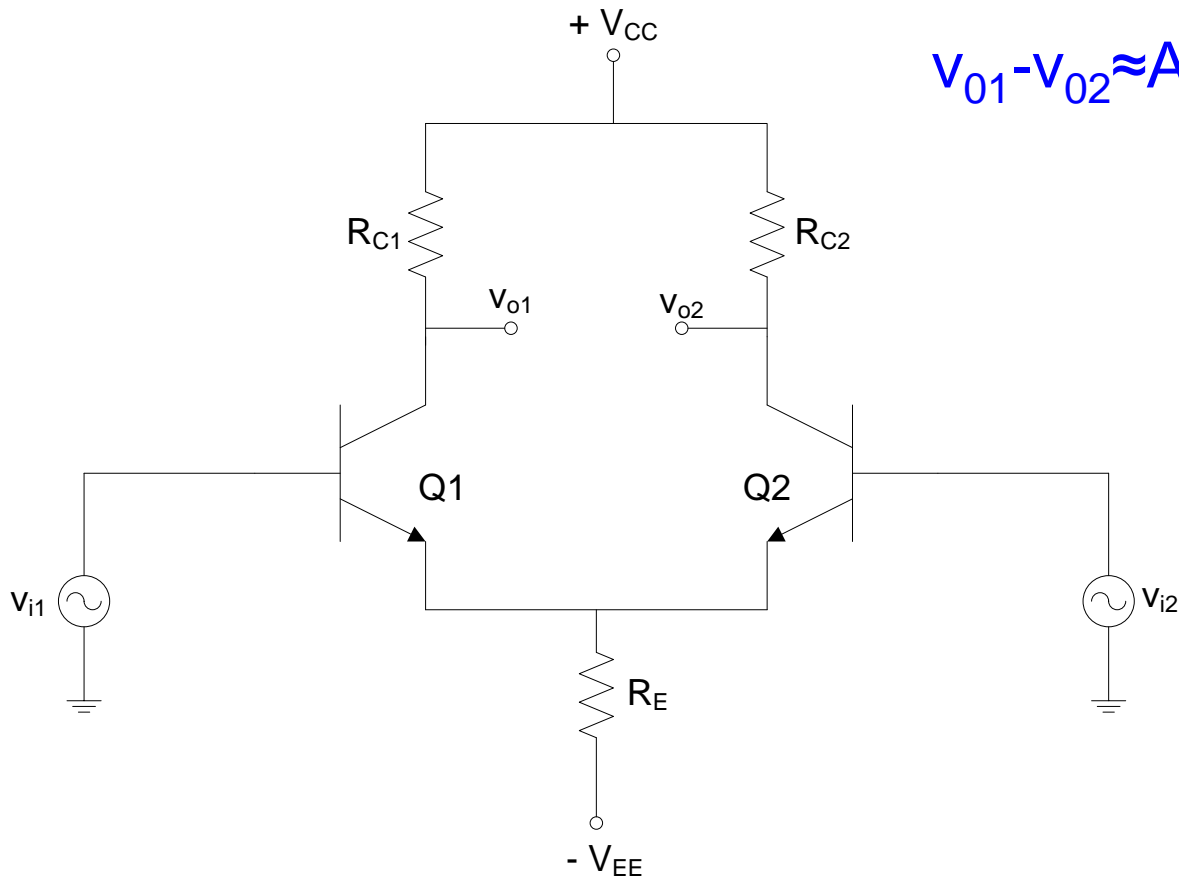
# Differential Amplifier

How to amplify differential signals? i.e.  $v_o = A_v(v_1 - v_2)$

$$v_{o1} - v_{o2} \approx A_v(v_{i1} - v_{i2})$$




# Push-Pull Configuration

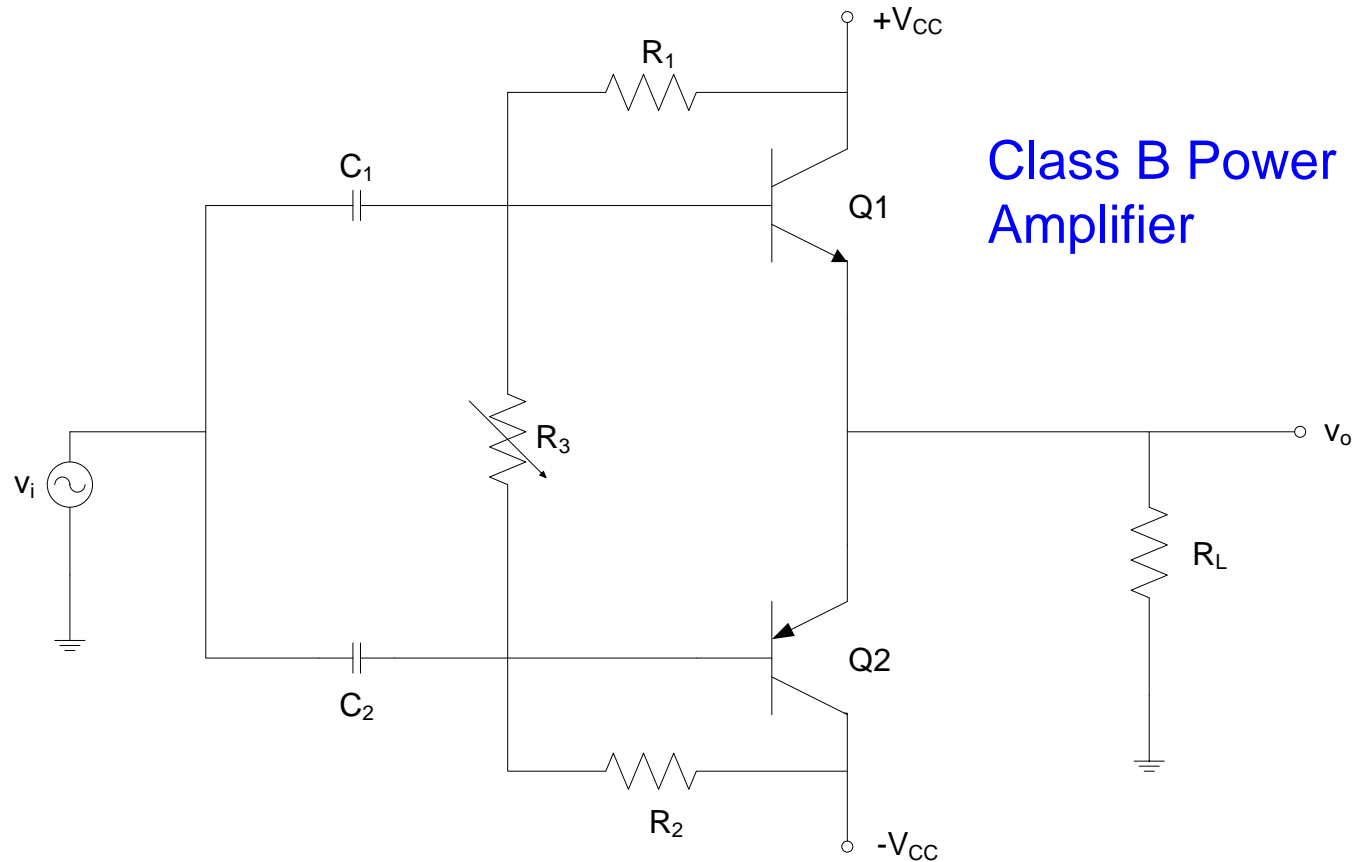


Matched npn and pnp transistors used to make amplifiers with high efficiency. Typically used as Power Amplifiers.

# Current Mirror Circuit

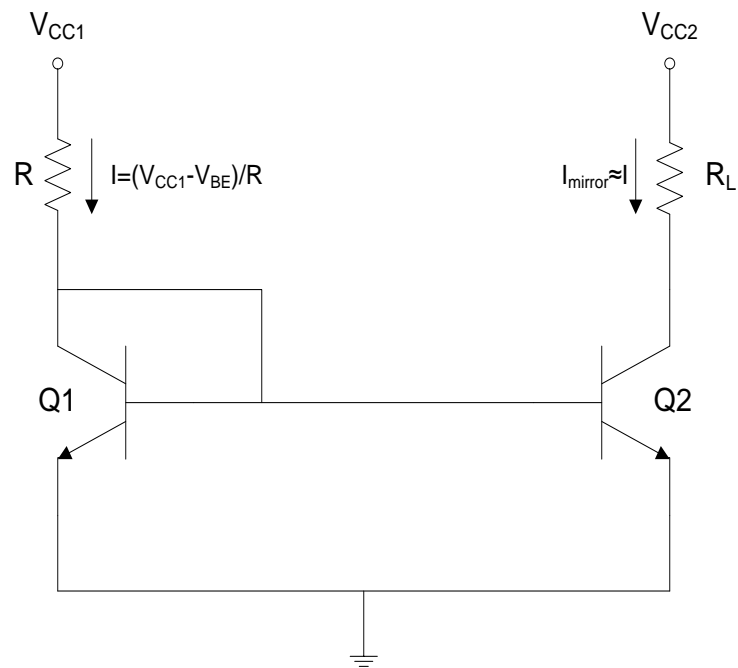

# Current Mirror Circuit

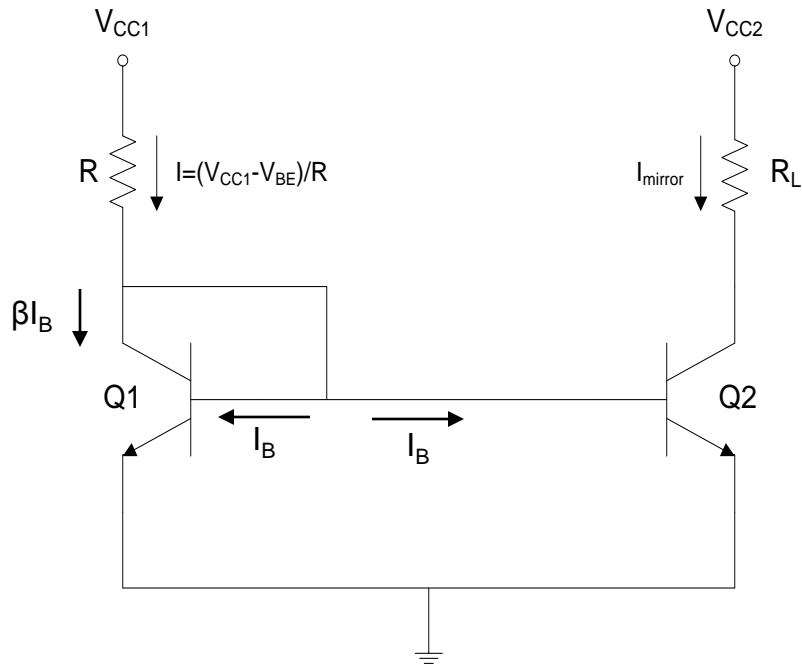


$$I = (\beta + 2)I_B$$


$$I_{\text{mirror}} = \beta I_B$$

$$I_{\text{mirror}} = \frac{1}{1 + \frac{2}{\beta}} I$$

# Transistor as a Switch

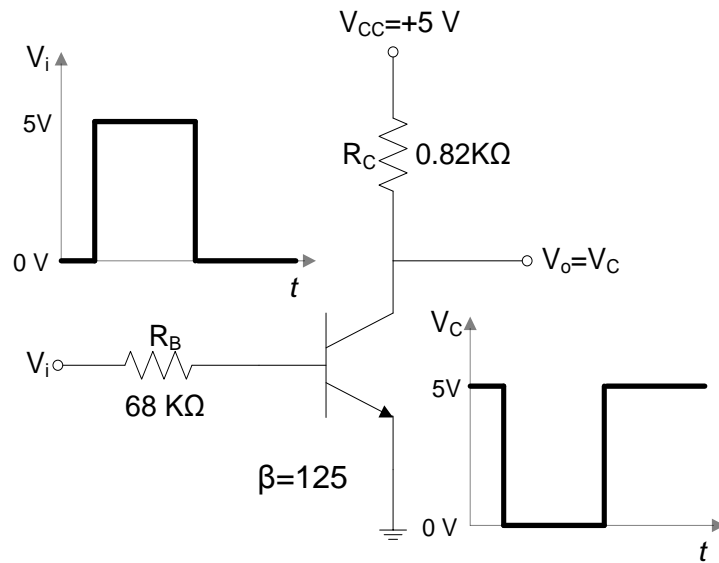

Transistor Inverter

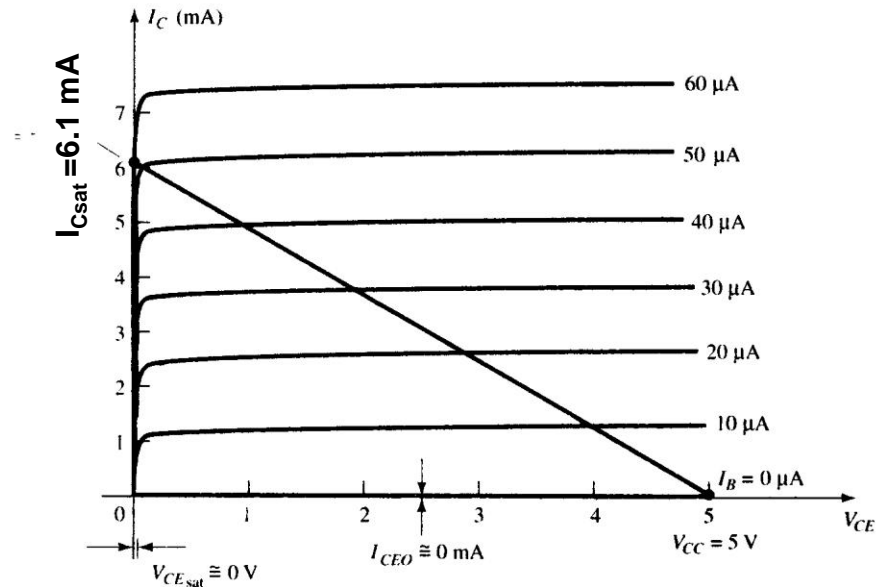


$I_C$ - $V_{CE}$  Characteristics ( $\beta = 125$ )

- Assume (a)  $I_C = I_{CE0} = 0\text{ mA}$  when  $I_B = 0\text{ }\mu\text{A}$   
 (b)  $V_{CE\text{sat}} = 0\text{ V}$  *This is more typically 0.1-0.3 V*



# Transistor as a Switch (Inverter)

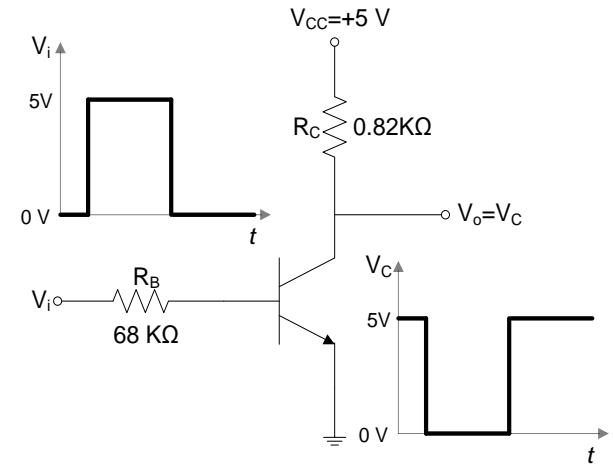

(a)  $V_i = 0 \text{ V}$  Transistor is OFF,  $I_C = 0$  and  $V_o = V_C = +5 \text{ V}$

(b)  $V_i = +5 \text{ V}$  Transistor is ON,  $V_{CE\text{sat}} = 0 \text{ V}$


$$I_B = (5 - 0.7) / 68 = 63 \text{ }\mu\text{A}$$

$$I_{C\text{sat}} = V_{CC} / R_C = 5 / 0.82 = 6.1 \text{ mA}$$

Note that  $\beta I_B = 7.88 \text{ mA} > I_{C\text{sat}} = 6.1 \text{ mA}$

Therefore, the transistor is indeed in saturation
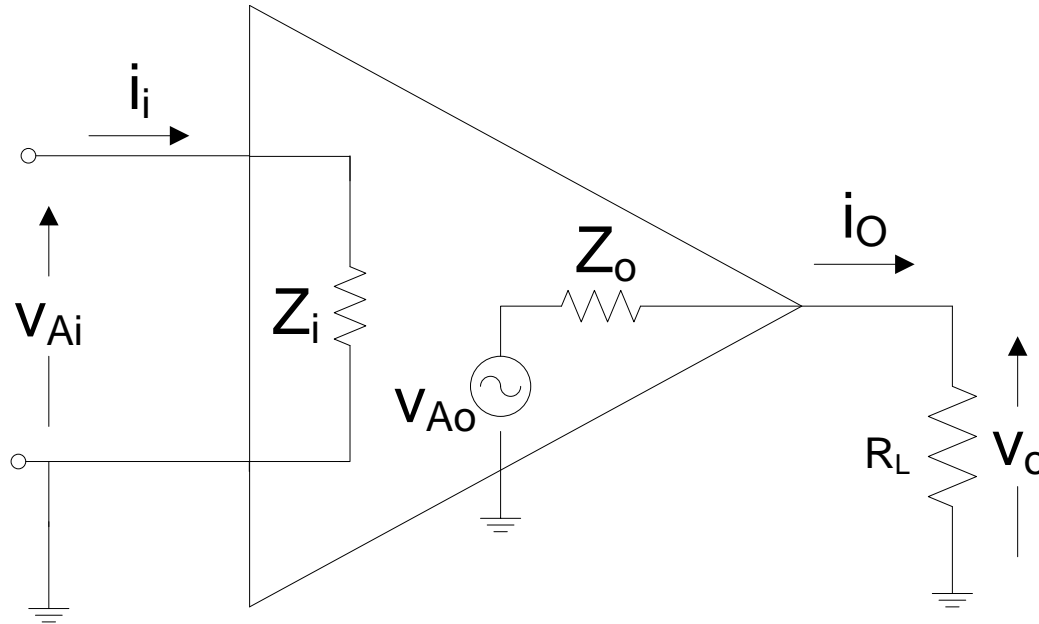
# Relationship between $A_v$ , $A_i$ , $Z_i$ and $Z_o$



$$\left. \begin{aligned} A_v &= \frac{v_{Ao}}{v_{Ai}} & Z_i &= \frac{v_{Ai}}{i_i} \\ i_o &= \frac{v_{Ao}}{Z_o + R_L} = \frac{A_v v_{Ai}}{Z_o + R_L} = \frac{A_v Z_i i_i}{Z_o + R_L} \end{aligned} \right\} \Rightarrow A_i = \frac{i_o}{i_i} = \frac{A_v Z_i}{Z_o + R_L}$$