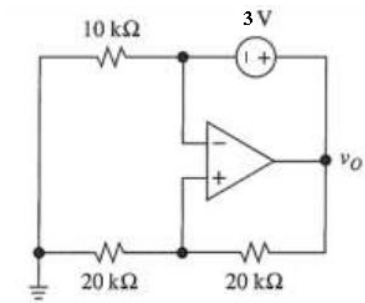



EE 101 Tutorial Sheet-9

(30 Oct 2014)


Q1: For the circuit shown below, find v_o and current through the 3V source (assume the OPAMP to be ideal)



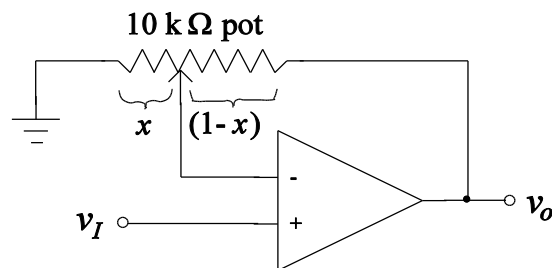Q2: The circuit shown below uses a 10 kΩ potentiometer to realize an adjustable gain amplifier. Assume the op-amp to be ideal. Derive an expression for the gain of the amplifier as a function of the potentiometer setting 'x'. What is the range of gain obtained? Show how to add a fixed resistor so that the gain range gets limited to 1 – 21 V/V. What should be the resistor value be?



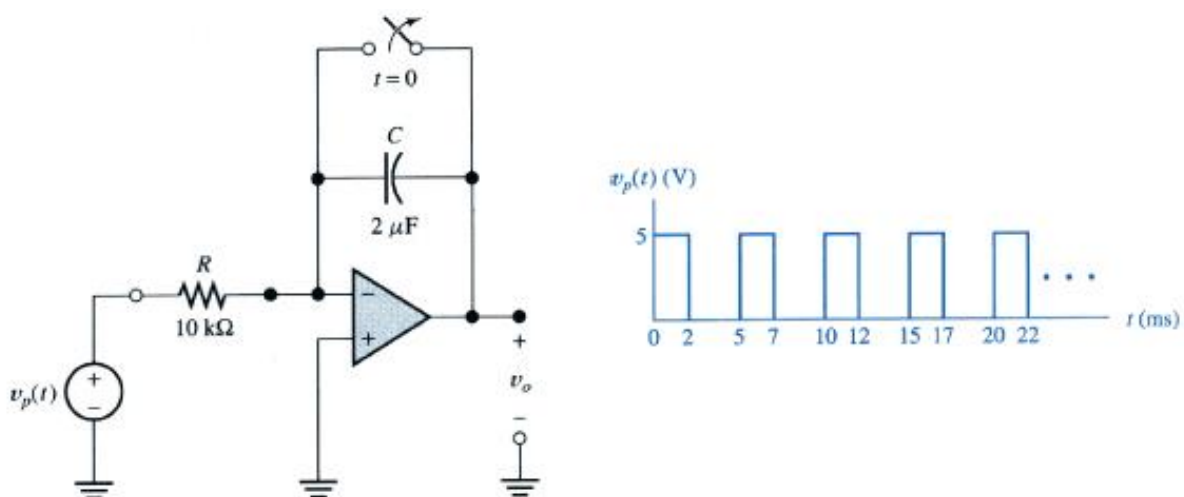Q3: For the circuit shown below, sketch the output voltage and find the number of input pulses for which the output voltage reaches a value of -5V. Assume the OPAMP to be ideal, the initial voltage across the capacitor is 0 V and the switch is opened at $t=0$, and kept opened thereafter. (Assume that the capacitor does not discharge when the applied input becomes zero)



Q4: Find the binary, octal and hexadecimal equivalent of 182.8125_{10} .