
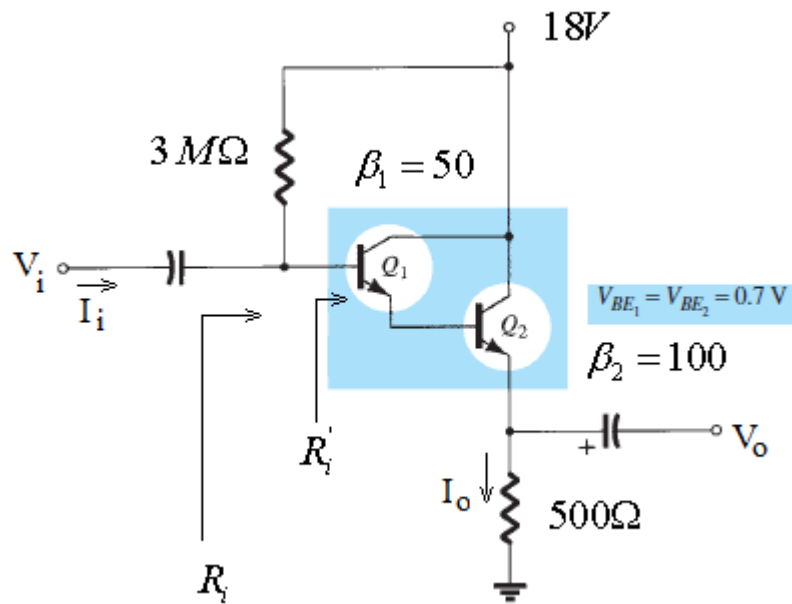


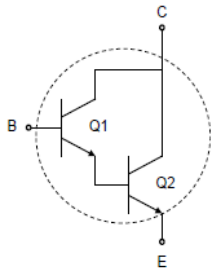1. For the circuit shown, find input resistance  $R_i$  and the voltage gain  $A_v = \frac{v_o}{v_i}$ . Assume  $V_T = 26$  mV and neglect the effect of  $r_o$ .



### Solution

For the Darlington pair



$$I_C = I_{c1} + I_{c2} = \beta_1 I_B + \beta_2 (\beta_1 + 1) I_B$$

$$\beta_D = \frac{I_C}{I_B} = \beta_1 \beta_2 + \beta_1 + \beta_2$$

For the given transistor configuration

$$\beta_D = 5150$$


$$I_C \approx I_E$$

$$V_{CC} = I_B R_B + V_{BE1} + V_{BE2} + I_E R_E$$

$$I_B \approx \frac{V_{CC} - (V_{BE1} + V_{BE2})}{R_B + \beta_D R_E} = \frac{18 - 1.4}{3 + 2.575} \approx 3 \mu A$$

$$I_{E1} = 51 \times 3 = 153 \mu A \quad r_{e1} = \frac{26 \times 10^{-3}}{153 \times 10^{-6}} \cong 164 \Omega$$
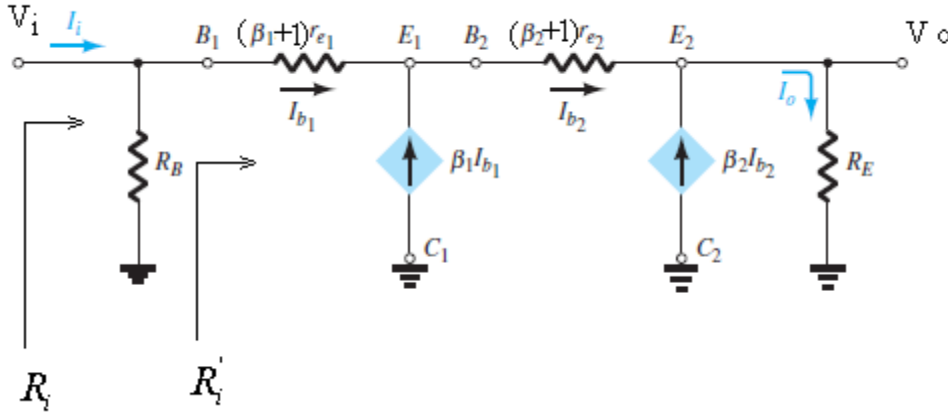
$$I_{E2} = 5150 \times 3 = \mu A \quad r_{e2} = \frac{26 \times 10^{-3}}{15450 \times 10^{-6}} \cong 1.7 \Omega$$



For transistor  $Q_2$ , the current flowing through the emitter resistance  $R_E$  is  $(\beta_2 + 1)i_{b2}$ . Therefore the input resistance for transistor  $Q_2$  can be deduced as  $R_{i_{Q2}} = (\beta_2 + 1)(r_{e2} + R_E)$ .

Note that transistor  $Q_1$  sees  $R_{i_{Q2}}$  as an external resistance connected at its emitter terminal. So the input resistance for transistor  $Q_1$  can be given as

$$R_i' = [r_{e1} + (\beta_2 + 1)(r_{e2} + R_E)](\beta_1 + 1) \cong 2.6 M\Omega$$

$$R_i = R_B \parallel R_i' = 1.4 M\Omega$$

### Current gain and voltage gain

$$I_0 = (\beta_1 + 1)(\beta_2 + 1)i_{b1} \quad i_{b1} = \frac{R_B}{R_B + R_i'} I_i \quad A_I = \frac{I_0}{I_i} = (\beta_1 + 1)(\beta_2 + 1) \frac{R_B}{R_B + R_i'} \cong 2760$$


$$V_o = I_0 R_E$$

$$V_i = R_i I_i$$


$$A_v = \frac{V_o}{V_i} = A_I \frac{R_E}{R_i} = 0.986$$

Note: Despite large current gain achieved due to Darlington configuration, the voltage gain turns out to be **unity** as the given circuit is an emitter follower.

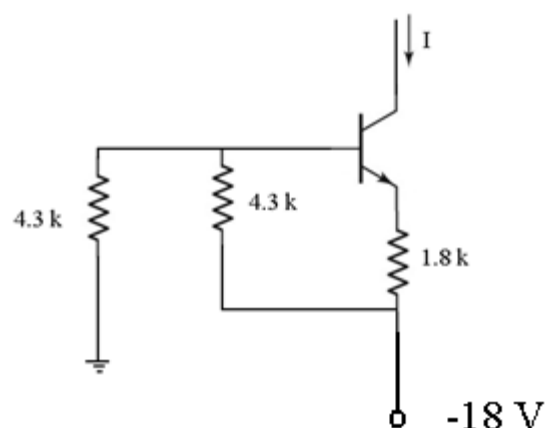2. Find the current  $I$  for the circuit shown below. The transistor has  $\beta = 100$ . Assume that the transistor is in active region and  $V_{BE} = 0.7 \text{ V}$ .



### Solution

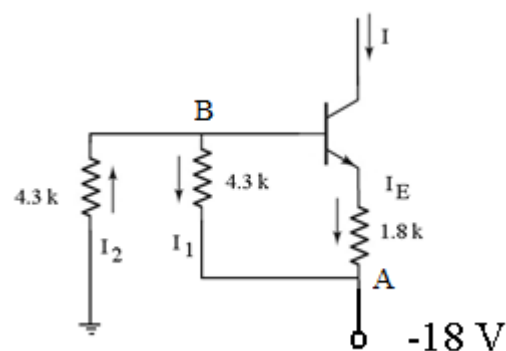

Consider that the currents  $I_1$ ,  $I_2$ ,  $I_E$  marked in the circuit are in mA.

Applying KVL in outer loop we have

$$4.3(I_1 + I_2) = 18 \quad (1)$$

On applying KCL at node B, we have

$$I_2 = I_1 + \frac{I_E}{101} \quad (2)$$

From (1) and (2) we have

$$2I_1 + \frac{I_E}{101} = \frac{18}{4.3} \quad (3)$$

On equating the voltage drop across terminals A-B, we have

$$4.3I_1 = V_{BE} + 1.8I_E = 0.7 + 1.8I_E \quad (4)$$

From (3) and (4) on solving for  $I_E$ , we get

$$I \simeq I_E = 4.56 \text{ mA}$$