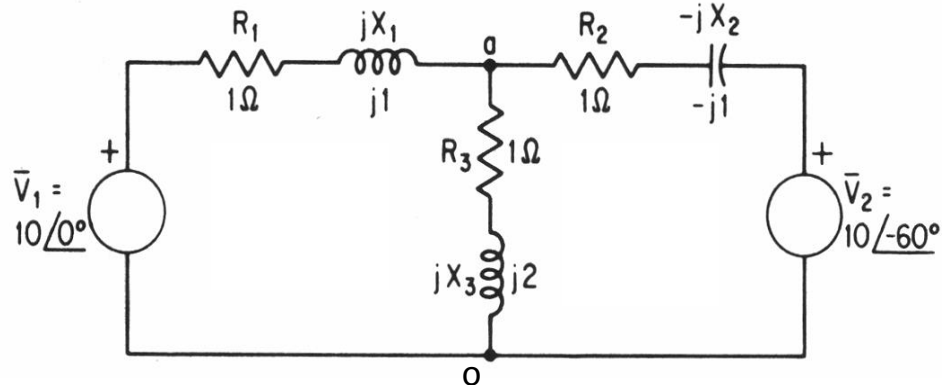


EE101
Tutorial-5 (11 Sep 2014)

Q1. Use Norton's theorem to find the current through R_3 , X_3 branch in the circuit shown below.



Q2. For the transistor amplifier circuit with collector-emitter feedback biasing shown in Figure 1, find the value of

- I_B
- V_C
- V_E
- V_{CE}

(Assume that $V_{BE} = 0.7\text{ V}$ in forward biased condition)

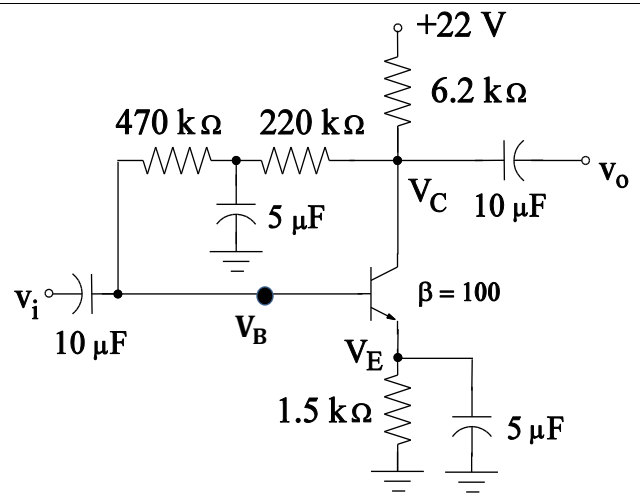


Figure 1

Q3. In Figure 2, the transistor is in active region with the quiescent C-E voltage $V_{CEQ} = 4\text{ V}$. Assume that $V_{BE} = 0.7\text{ V}$, $V_T = 26\text{ mV}$, BJT output resistance r_o is very high ($> 100\text{ k}\Omega$), and all capacitors are short-circuited at applied signal frequency. Find the value of

- R_1
- r_e
- $A_v = \frac{v_o}{v_i}$
- A_v , if a load $R_L = 2\text{ k}\Omega$ is connected across A-B.
- $A_{v_s} = \frac{v_o}{v_s}$, if $R_L = 2\text{ k}\Omega$ is connected across A-B and assuming that applied voltage source has a resistance of $R_s = 0.5\text{ k}\Omega$.

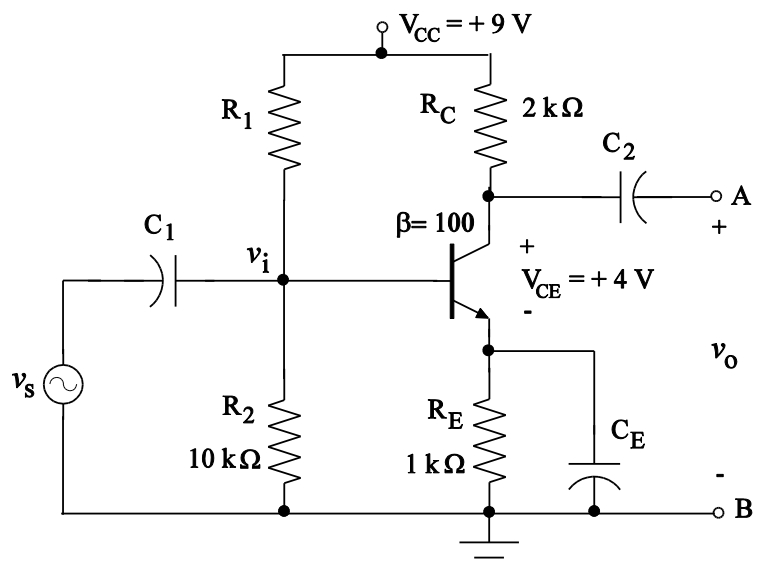


Figure 2