

Department of Electronics and Electrical Engineering
Indian Institute of Technology Guwahati


EE101

Quiz1

Maximum Marks: 10

Time: 45Minutes

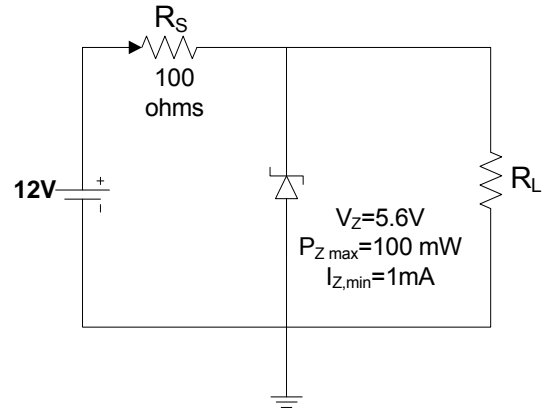- 1.** In the circuit shown in figure1, the load resistance R_L is allowed to vary.
 (a) What would be the range of R_L for which this circuit will operate properly? [3]
 (b) When R_L varies over the range where the circuit works properly, what will be the minimum and maximum values of the current through the Zener diode (I_Z) and the power dissipated (P_Z) dissipated by it? [2]



Solution:

- (a) To satisfy the condition that $I_Z > I_{Z,min}$, we need

$$\frac{12 - 5.6}{100} - \frac{5.6}{R_L} > 0.001 \quad \text{or } R_L > 88.89 \, \Omega$$

(1+0.5)

To satisfy the condition that $P_{Z,max} < 0.1 \, W$, we need

$$\left[\frac{12 - 5.6}{100} - \frac{5.6}{R_L} \right] 5.6 < 0.1 \quad \text{or } R_L < 121.48 \, \Omega \quad \text{(1+0.5)}$$

- (b) $I_{Z,min} = 1 \, mA$
 $I_{Z,max} = \frac{12 - 5.6}{0.1} - \frac{5.6}{0.12148} = 17.8 \, mA$ (or trivially, $\frac{100}{5.6}$)
 $P_{Z,min} = 5.6 \times 0.001 = 0.0056 \, W$
 $P_{Z,max} = 0.1 \, W$
- 4x0.5**

2. Consider the active linear network shown in figure 2.

(a) Find the Thevenin equivalent circuit of the network at terminal a-b. [3]

(b) Find the maximum power that the network can deliver to a resistive load at a-b. [2]


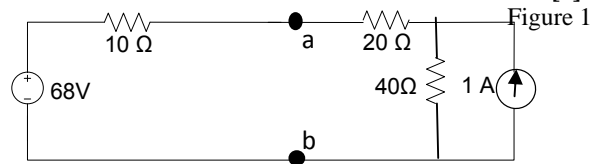


Figure 2

Solution:


(a) To find the Thevenin equivalent circuit:

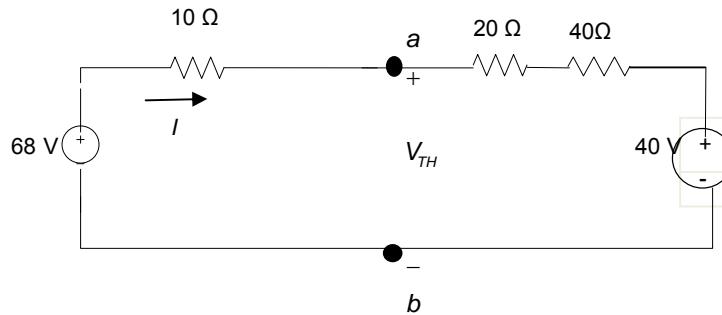(i) First apply source transformation to the right-hand current source




$$I = \frac{68 - 40}{10 + 20 + 40} = 0.4 \text{ A} \Rightarrow \therefore V_{TH} = 68 - 10 \times 0.4 = 64 \text{ V}$$

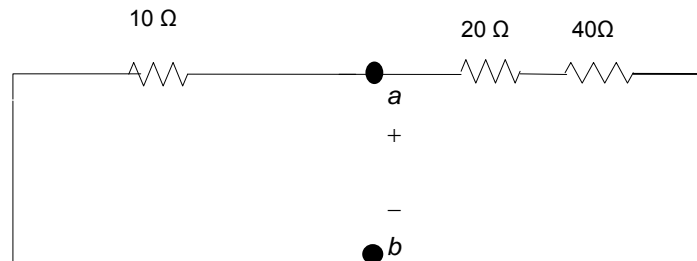(ii) Switch off the voltage and current source to get the circuit below:



$$\therefore R_{TH} = (20 + 40) \parallel 10 = \frac{60}{7} \Omega$$

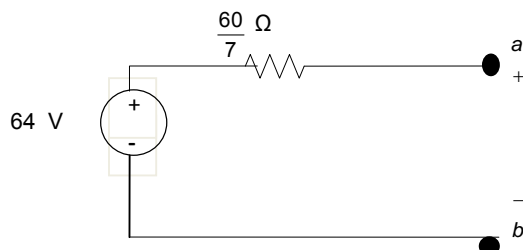Therefore, the Thevenin equivalent circuit is as shown in the figure below:



(b) The maximum power that can be delivered by the network

$$= \frac{V_{TH}^2}{4R_{TH}} = 64 \times 64 / (4 \times 60 / 7) = 119.47 \text{ W}$$