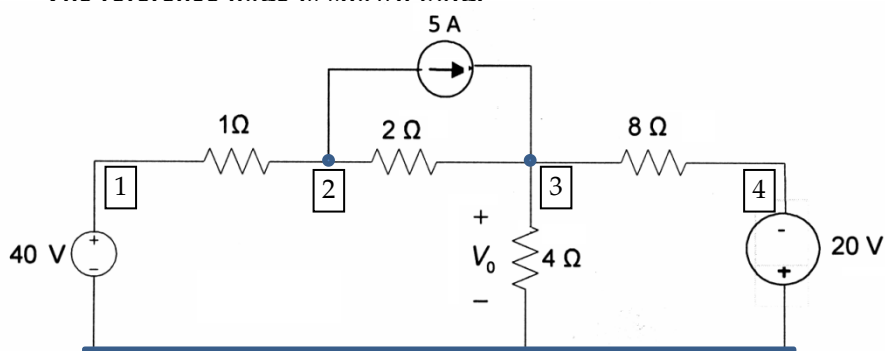


EE 101 Tutorial Problems 2 Solutions
(14 August 2014)

Q 1. The reference node is shown bold.




At node 1, $v_1 = 40 \text{ V}$, At node 4, $v_4 = -20 \text{ V}$

Node equation at node 2, $\frac{v_2 - 40}{1} + \frac{v_2 - v_3}{2} + 5 = 0$ (1)

Node equation at node 3, $\frac{v_3 - v_2}{2} + \frac{v_3}{4} + \frac{v_3 - (-20)}{8} - 5 = 0$ (2)

Solving (1) and (2), $v_3 = 20 \text{ V} = V_0$

Q 2.

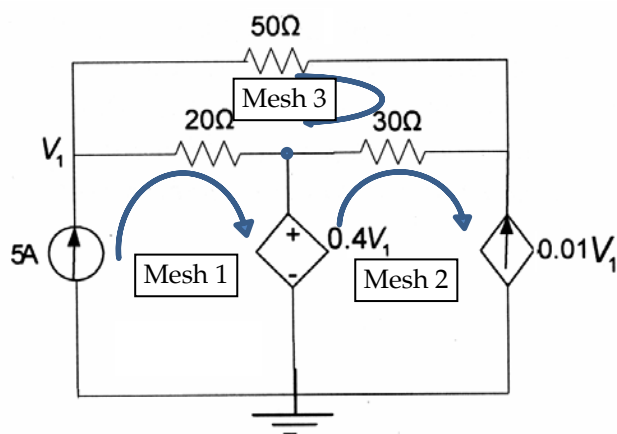

Mesh 1: $i_1 = 5 \text{ A}$

Mesh 2: $i_2 = -0.01V_1 \text{ A}$

KVL in Mesh 3: $(50+30+20)i_3 - 20i_1 - 30i_2 = 0$ (1)

KVL in Mesh 1: $V_1 - 20(5-i_3) - 0.4V_1 = 0$ (2)

Solving (1) and (2), $V_1 = 148 \text{ V}$

Voltage across dependent source $= 0.4V_1 = 59.2 \text{ V}$


Current through dependent source $= i_2 - i_1 = 5 \text{ A} - 0.01V_1 \text{ A} = 6.48 \text{ A}$

Therefore, power output $= 59.2 \times 6.48 = 383.6 \text{ W}$

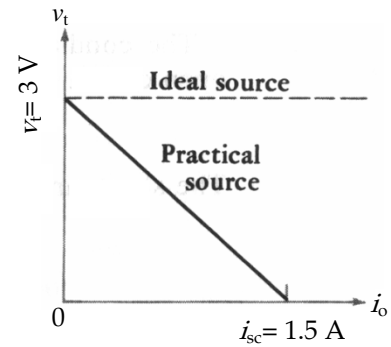
Q 3. From figure 3b,

Open circuit voltage of the source = 3 V

Internal resistance of the source = $3/1.5 = 2 \Omega$



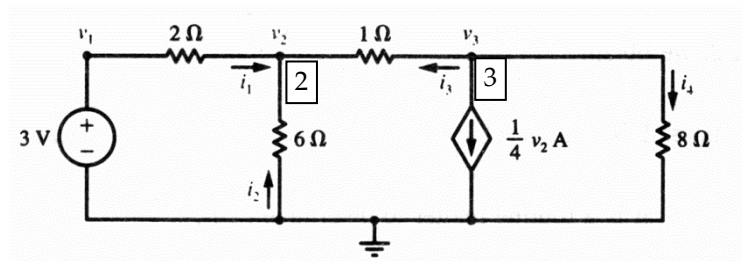Therefore the circuit may be redrawn as shown with $(0 \leq i_1 \leq 1.5 \text{ A})$



$$\begin{aligned} \text{KCL at node 2,} \quad & \frac{v_1 - v_2}{2} + \frac{-v_2}{6} + \frac{v_3 - v_2}{1} = 0 \\ & \Rightarrow -10v_2 + 6v_3 = -9 \quad (1) \end{aligned}$$

$$\begin{aligned} \text{KCL at node 3,} \quad & \frac{v_2}{4} + \frac{v_3 - v_2}{1} + \frac{v_3}{8} = 0 \\ & \Rightarrow -6v_2 + 9v_3 = 0 \quad (2) \end{aligned}$$

Solving, (1) and (2),

$$v_2 = 1.5 \text{ V}, \quad \text{and} \quad v_3 = 1 \text{ V}$$

$$\begin{aligned} \text{Then, } i_1 &= 0.75 \text{ A} & i_2 &= -0.25 \text{ A} \\ i_3 &= -0.5 \text{ A} & i_4 &= 0.125 \text{ A} \end{aligned}$$