

# EE 101 Endsem Exam 24 Nov '14

## Solutions

Q1 (a)

$$v_- = v_+ = 4V$$

[ Virtual ground ]

On applying KCL,

$$\frac{v_o - v_-}{1k\Omega} + 1mA = 0 \Rightarrow v_o - 4 + 1 = 0$$

$$\therefore v_o = 3V$$

2 Marks  
for final  
answer.

(b)  $v_i = R_i i_s$  and  $i_o = \frac{A_v v_i}{R_o + R_L}$

Thus,  $i_o = \frac{A_v R_i i_s}{R_o + R_L} \Rightarrow A_v = \frac{(i_o/i_s)(R_o + R_L)}{R_i}$

$$\therefore A_v = \frac{(120)(40\Omega + 20\Omega)}{2000\Omega} = 3.6 \text{ V/V}$$

2 Marks  
for final  
answer

(c)  $127_8 = (001010111)_2$   
 $5E_{16} = (01011110)_2$   


---

Sum =  $(10110101)_2$   
 $= (11101111)_{\text{Gray}}$

Alternative way:

$$127_8 = 87_{10}$$

$$5E_{16} = 94_{10}$$

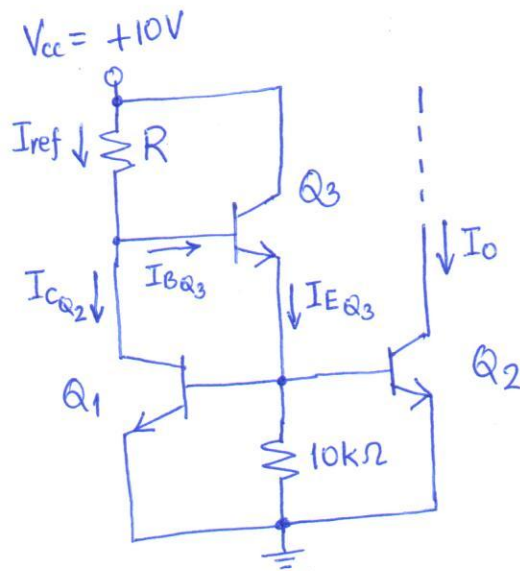

---


$$\text{Sum} = 181_{10} = 10110101_2$$

$$= 11101111_{\text{Gray}}$$

2 Marks for  
obtaining the  
sum value in  
binary  
+ 1 Mark for  
Gray Conversion

Q1 (d)



$Q_1$  and  $Q_2$  are matched, and have same base-emitter voltage. Thus, they both have same collector current, namely  $I_0 = 0.7 \text{ mA}$ . They also have the same base currents of  $I_0/\beta$ .

KCL equation:

$$I_{EQ3} = \frac{I_0}{\beta} + \frac{I_0}{\beta} + \frac{V_{BE}}{10 \text{ k}\Omega}$$

$$= \frac{2(0.7 \times 10^{-3})}{80} + \frac{0.7 \text{ V}}{10 \text{ k}\Omega} = 87.5 \mu\text{A}$$

Then,  $I_{BQ3} = I_{EQ3}/(1+\beta) = \frac{87.5 \mu\text{A}}{1+80} = 1.08 \mu\text{A}$

Now  $I_{ref} = I_{BQ3} + I_{CQ2} = 1.08 \mu\text{A} + 0.7 \text{ mA} = 0.7011 \text{ mA}$

$$\therefore R = \frac{V_{CC} - V_{BEQ3} - V_{BEQ1}}{I_{ref}}$$

$$= \frac{(10 - 2 \times 0.7) \text{ V}}{0.7011 \times 10^{-3} \text{ A}} = 12.27 \text{ k}\Omega.$$

Alternate Solution:

$I_{ref} \approx I_0$  (Student should justify the base current  $I_{BQ3}$  is neglected)

1 + 1 (for justification)

Q2. (a) Let 'x' be the fraction of the full range of the potentiometer. ~~Then~~ w.r.t grounded end.

$$V_+ = \frac{xR_3}{R_3} V_i = xV_i = V^-, \quad 0 \leq x \leq 1$$

On applying KCL at node between  $R_1$ - $R_2$ , we have

$$\frac{V_i - xV_i}{R_1} = \frac{xV_i - V_o}{R_2}$$

$$\therefore R_1 = R_2, \quad \therefore V_o = (2x-1)V_i$$

$$\text{When } x=1, \quad V_{o\max} = V_i = +1V$$

$$\text{When } x=0, \quad V_{o\min} = -V_i = -1V$$

(b) Now when switch is closed

$$\frac{V_i - xV_i}{R_1} = \frac{xV_i}{R_4} + \frac{xV_i - V_o}{R_2}$$

$$\frac{R_2}{R_1} (V_i - xV_i) = \frac{R_2}{R_4} xV_i + xV_i - V_o$$

$$\therefore V_o = \left[ x + \frac{R_2}{R_4} x - \frac{R_2}{R_1} (1-x) \right] V_i$$

$$\text{When } x=0, \quad V_{o\min} = -\frac{R_2}{R_1} V_i = -1V$$

$$\text{When } x=1, \quad V_{o\max} = [1+4+0]1 = 5V$$

(c) From part (b), ~~to~~ setting absolute of  $V_{o\min}$  to 5

$$|V_{o\min}| = \left| -\frac{R_2}{R_1} V_i \right| = 5$$

$$\Rightarrow \frac{R_2}{R_1} = 5 \quad \text{or} \quad R_1 = \frac{R_2}{5} = \frac{10k\Omega}{5} = 2k\Omega$$

Q3 (a)  
(i)

BCD Input				Output
a	b	c	d	$f(a,b,c,d)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X


K-map

cd \ ab				
	00	01	11	10
00			X	
01		1	X	1
11	1	1	X	X
10		1	X	X


Minimized logic ckt  $\rightarrow f(a,b,c,d) = cd + bc + bd + ad$

2

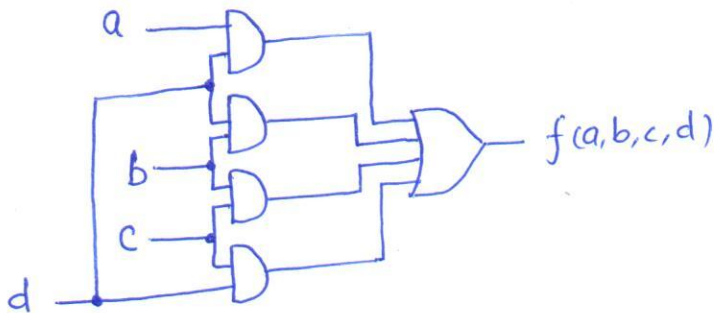(ii) ~~do~~ Realization using AND, OR gates




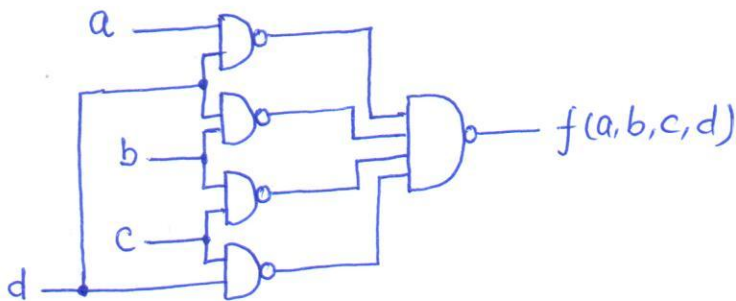(iii) ~~do~~ Realization using ONLY NAND gates





Q3(b)

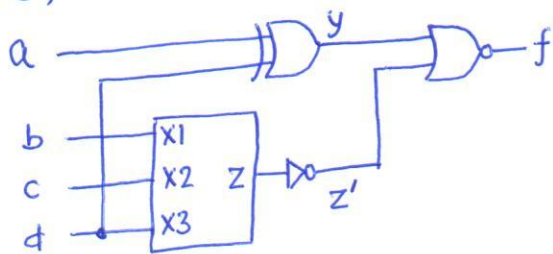


(i) Truth Table


a	b	c	d	y	z'	f
0	0	0	0	0	0	1
0	0	0	1	1	0	0
0	0	1	0	0	1	0
0	0	1	1	1	1	0
0	1	0	0	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	0	1
0	1	1	1	1	0	0
1	0	0	0	1	0	0
1	0	0	1	0	0	1
1	0	1	0	1	1	0
1	0	1	1	0	1	0
1	1	0	0	1	0	0
1	1	0	1	0	0	1
1	1	1	0	1	0	0
1	1	1	1	0	0	1

2

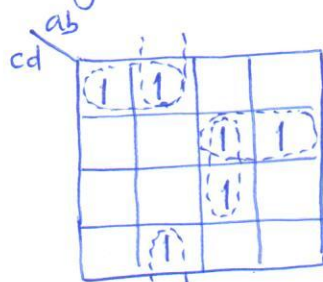(ii) The logic circuit contains 6 minterms or 10 maxterms. Thus on plotting in K-map, we can note that POS form of logic expression leads to better minimization



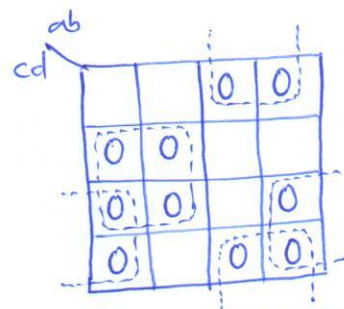
(A)  $f = \bar{a}\bar{c}\bar{d} + \bar{a}b\bar{d} + abd + a\bar{c}d$



(B)  $f = \bar{a}d + a\bar{d} + \bar{b}c$

1 Mark for either (A) or (B)


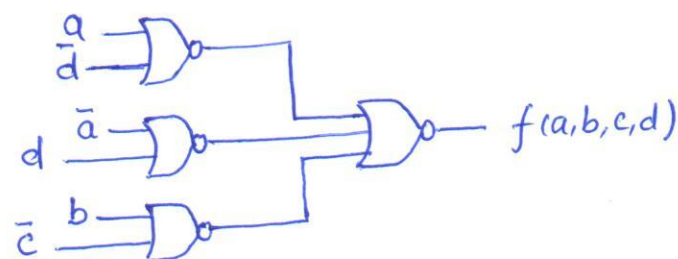
(iii) Realization of POS expression using only NOR gates with the assumption that complemented and uncomplemented logic variables are available.






1 Mark

Alternate non-minimum NOR only realization →

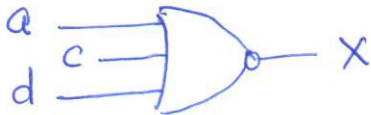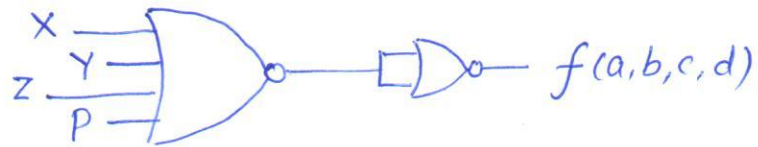NOR only realization for SOP, expression (A)



1 Mark

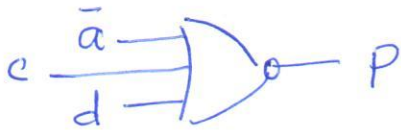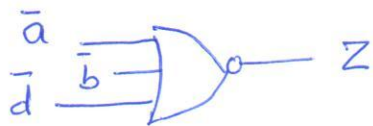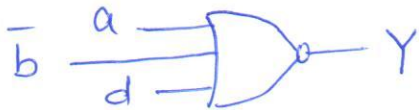

Q. 1

①  $B = 1.5 \sin 377t$

$$A = 4 \times 4 \times 10^{-4} \text{ m}^2$$

$$\therefore \phi = 1.5 \times 16 \times 10^{-4} \sin 377t \quad [1]$$

$$\lambda = N\phi = 200 \times 1.5 \times 16 \times 10^{-4} \sin 377t \quad [1]$$

$$\therefore e = \frac{d\lambda}{dt} = 4800 \times 10^{-4} 377 \cos 377t$$

$$= 0.48 \times 377 \cos 377t$$

$$= \underline{181 \cos 377t} \quad [1]$$

② Peak value of the flux =  $\frac{1.5 \times 1.6 \times 10^{-3}}{\sqrt{2}} = \text{wb}$

$$= \underline{1.70 \text{ mwb}}$$

$$\text{Reluctance} = \frac{l}{\mu A} = \frac{0.80}{4\pi \times 10^{-7} \times 3000 \times 16 \times 10^{-4}}$$

$$= \frac{0.8}{4\pi \times 3 \times 16} \times 10^7 \text{ H}^{-1} = 13262.9 \text{ H}^{-1} [1]$$

$$NI_p = 1.70 \times 10^{-3} \times 13262.9$$

$$\therefore I_{\text{max}} = \frac{1.70 \times 13262.9}{200} = \underline{0.113 \text{ A}} \quad [2]$$

③  $L = \frac{N^2}{R} = \frac{200^2}{13262.9} = 3.016 \text{ H} \quad [1]$

$$W_f = \frac{1}{2} i_m^2 L = \frac{1}{2} 0.113^2 \times 3.016 \text{ J}$$

$$= 0.0192 \text{ (J)} \quad [1]$$

2


a.

$$Z = \frac{150}{25} = 4 \Omega$$

$$i^2 R = 1280 \rightarrow R = \frac{1280}{252} = 2.048 \Omega \quad [1]$$

$$\therefore X = \sqrt{Z^2 - R^2} = 3.436 \Omega \quad [1]$$

Referred to the hv side.

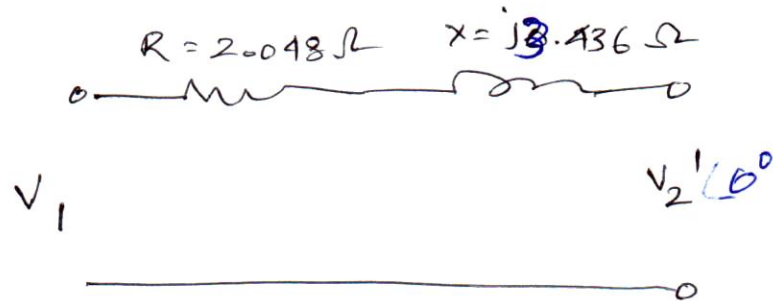

[1]

b) At 40 kW load at 0.8 pf. lag,  $V_2' = 2400 V$ .

$$S = 40 \times 10^3 \angle 36.87^\circ$$

$$I_2' = \frac{40 \times 10^3}{0.8 \times 2400} \angle -36.87^\circ$$

$$= 20.83 \angle -36.87^\circ A.$$

[2]

$$\text{Copper loss} = 20.83^2 \times 2.048 = 888.6 W \quad [1]$$

$$\therefore \eta = \frac{40}{40 + 0.8 + 0.888.6} = 0.9595 = 95.95\% \quad [1]$$

$$\text{Input mWge} = V_2' \angle 0^\circ + I_2' (R + jX).$$

$$= 2400 \angle 0^\circ + 20.83 \angle -36.87^\circ \times (2.048 + j3.436).$$

$$= 2400 \angle 0^\circ + 83.32 \angle 22.33^\circ$$

$$= 2400 \angle 0^\circ + 77.03 + j 31.65$$

$$= 2477.03 + j 31.65$$

$$= 2477.7 \angle 0.73^\circ$$

[2]



(3)

$$a) \quad N_s = \frac{120f}{P} \approx N_m = 1470$$


$$P \approx \frac{120 \times 50}{1470} = 4.08$$

$$\therefore P = 4 \text{ poles}$$

[1]

$$\text{and } N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm.}$$
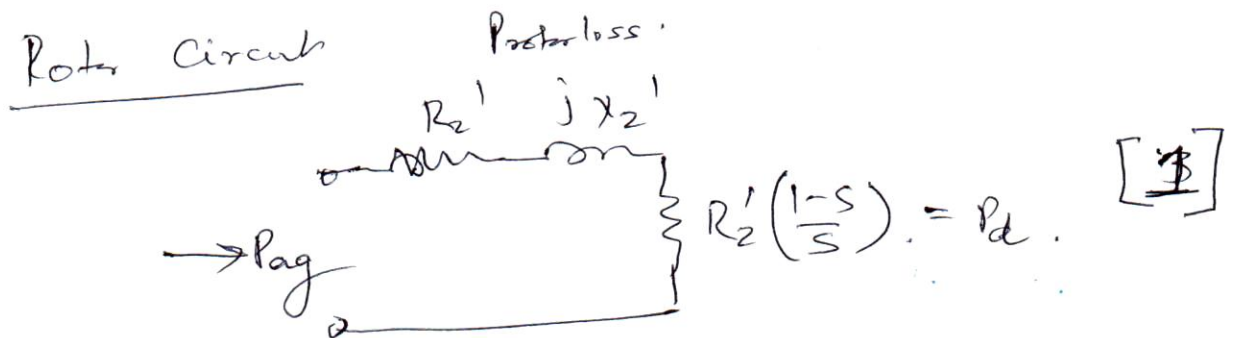
$$\text{and } s = \frac{N_s - N_m}{N_s} = \frac{1500 - 1470}{1500} = 0.02 \text{ pu. [1]}$$



b) Frequency of the rotor current

$$f_r = sf = 0.02 \times 50 = 1 \text{ Hz}$$

[1]

Speed of the rotor flux w.r.t rotor

$$= \frac{120f_r}{P} = \frac{120 \times 1}{4} = 30 \text{ rpm.}$$

[1]

c)  $P_d = 50 \text{ kW} = 50 \times 10^3 \text{ W}$

$$= 3 I_2'^2 r_2' \left( \frac{1-s}{s} \right)$$

[1]

$$\therefore \text{Rotor Copper loss} = 3 I_2'^2 r_2' = \frac{P_d \times s}{1-s}$$

[1]

$$= \frac{5 \times 0.02}{0.98} = 0.102 \text{ kW.}$$

$$\text{Air gap power} = 3 \frac{I_2'^2 r_2'}{s} = \frac{P_d}{1-s} = \frac{5}{0.98} \text{ kW} = 5.102 \text{ kW [1]}$$