

EE101
Tutorial 3 (23-AUG-2013)

- For the circuit shown in Figure for Problem 1, what will be the state of the two diodes, D1 and D2? What will be the voltages V_A , V_B and the currents I_{D1} and I_{D2} ? Show that the other states of the two diodes will not be acceptable. Assume that a diode has a forward bias voltage of 0.7 V when it is conducting (i.e. when it is ON).
- Sketch the transfer characteristics of the given circuit in Figure for Problem 2, assuming that the cut-in voltage of the diodes is 0.5 V and their voltage drop is 0.7 V for conducting current $i_D \geq 1\text{mA}$

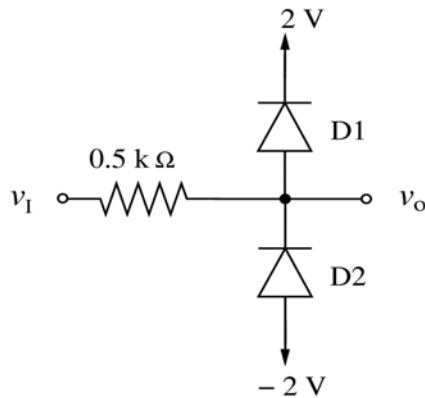


Figure for Problem 2

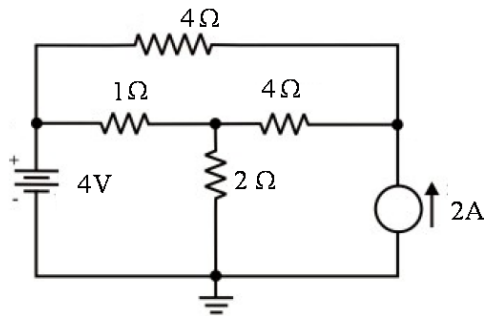


Figure for Problem 4

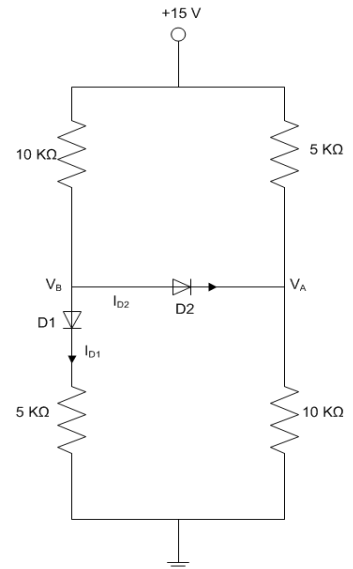


Figure for Problem 1

3.

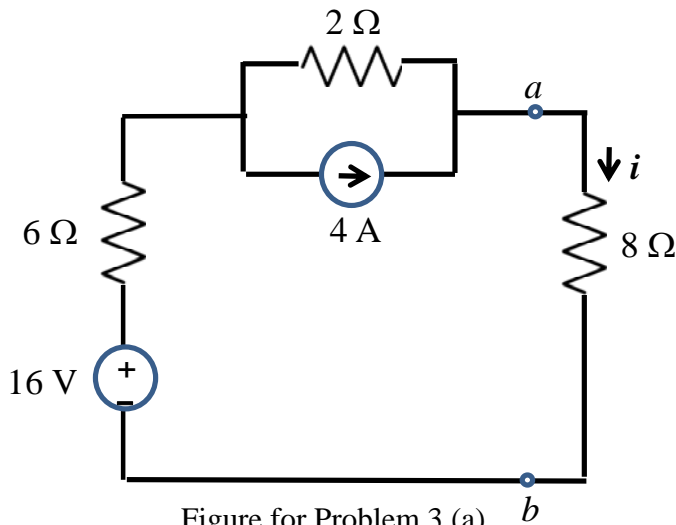


Figure for Problem 3 (a)

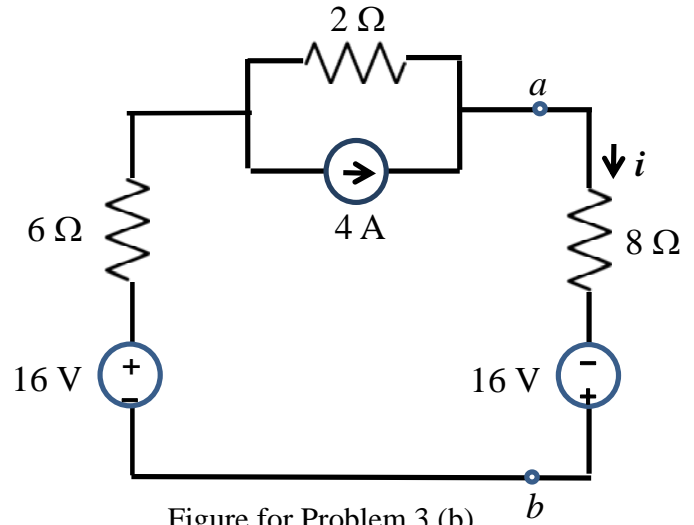


Figure for Problem 3 (b)

- For the circuit shown in Figure for Problem 3 (a), find the Thevenin's equivalent across terminals $a-b$, and therefore find the current i through the 8Ω resistor.
 - If 16 V source were added in series with the 8Ω resistor as shown in Figure for Problem 3 (b), use superposition theorem to find the current through the resistor.
- For the circuit shown in Figure for Problem 4, apply Norton's theorem to find the current through the 1Ω resistance