

# EE101

## Tutorial 1 and Tutorial 2 (16-AUG-2013 and 20-AUG-2013)

1. In the circuit shown in Figure for problem 1, calculate  $V_O$ - $V_i$  characteristic assuming the forward voltage drop across the diodes to be 0.7 volts. (Use your  $V_O$ - $V_i$  characteristic to draw the output voltage waveform. i.e.  $V_O(t)$ .)

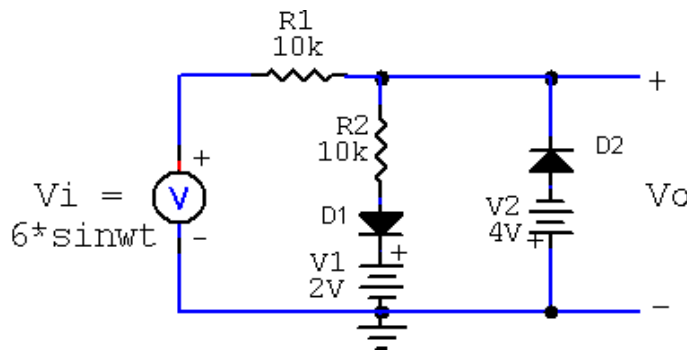


Figure for Problem 1

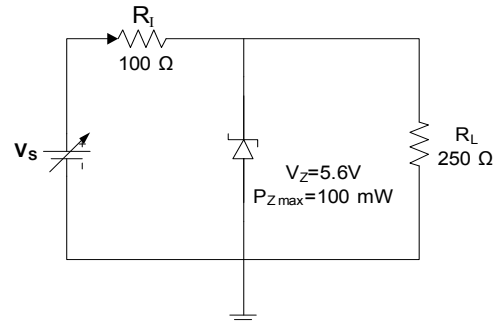


Figure for Problem 2

2. (a) For the circuit shown in figure for problem 2, what is the maximum value of the source voltage  $V_S$  for which the voltage across the load resistance  $R_L$  can be maintained at 5.6V?  
(b) If the Zener diode is such that a minimum current of 1 mA is required for the Zener action to take place, what is the minimum source voltage  $V_S$  that can be used?
3. For the circuit, given in Figure for problem 3 using the simple on/off model of diode with knee voltage  $V_k = 0.7V$  for both the diodes, find  $v_D$ ,  $v_R$  and the total diode current (= resistor current). Could the individual diode currents  $i_{D1}$  and  $i_{D2}$  be also determined?

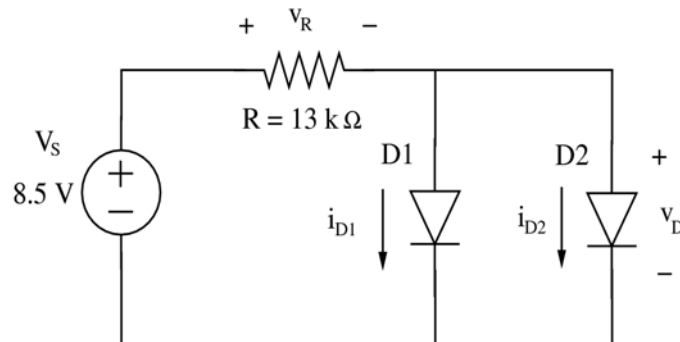


Figure for Problem 3

4. For the circuit shown in Figure for problem 4 find (a)  $I$  and (b) the power dissipated in the  $4\Omega$  resistor.

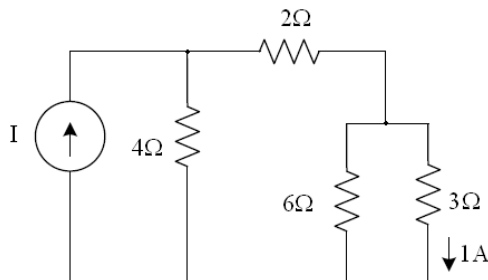


Figure for Problem 4

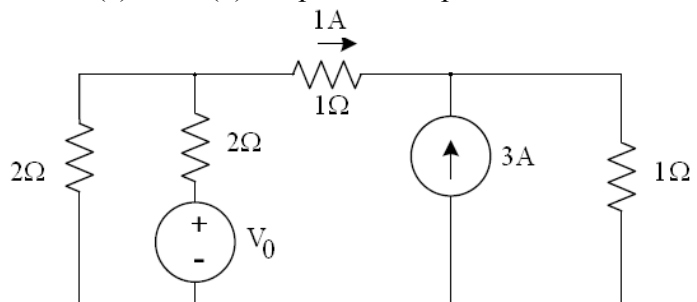


Figure for Problem 5

5. For the circuit shown in Figure for problem 5, find  $V_0$  (1 A current flows through 1 Ohm resistance as shown)

6. For the circuit shown in Figure for problem 6, find the mesh currents  $I_1$  and  $I_2$

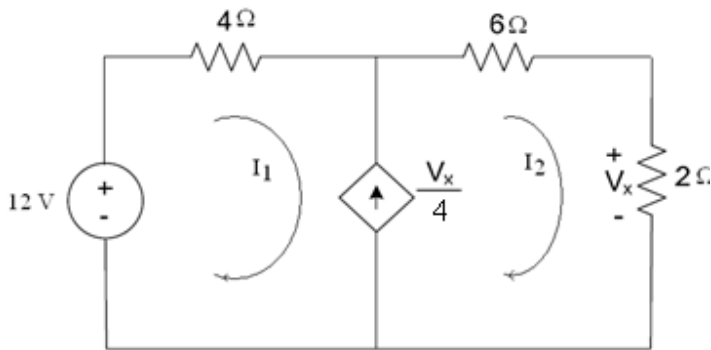


Figure for Problem 6

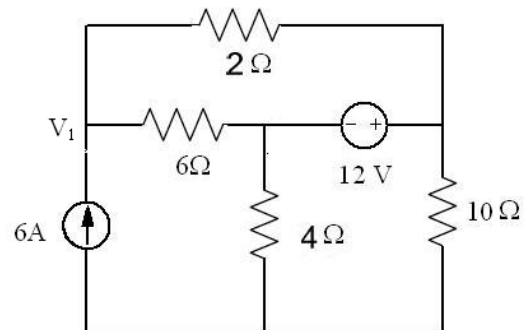


Figure for Problem 7

7. Using nodal analysis, find node voltage  $V_1$  in the circuit shown in Figure for problem 7.

8. For the given circuit, shown in Figure for Problem 8 sketch the output voltage  $v_o$  and determine the dc voltage available at the output.

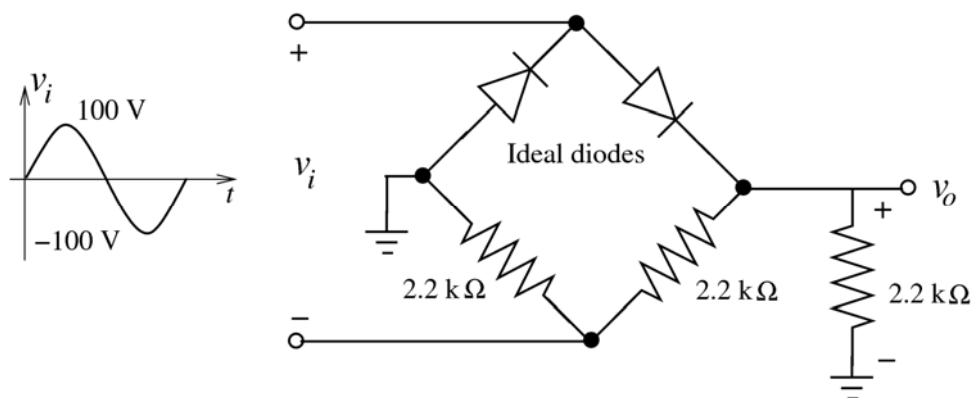


Figure for Problem 8