

EE 101 Tutorial Problems 6  
(18 September 2014)

- Find the voltage  $v_o$  in the circuit shown in Fig. 1. (Note that the two sources have two different frequencies).

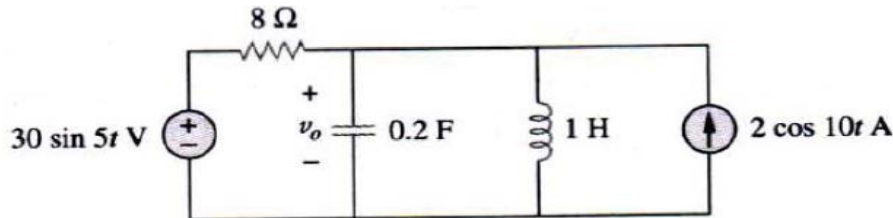


Figure 1

- Find the expression for the current through the inductance in the circuit shown in Figure 2, using operational impedances (with operator  $p$ ) when the switch  $S$  is closed. Hence find the expression for the current through the inductance as a function of time. Find
  - The initial value of the current through the inductance
  - The steady state value of the current through the inductance
  - The time constant of the circuit
  - Time taken by the current through the inductance to reach a value of 1 A.

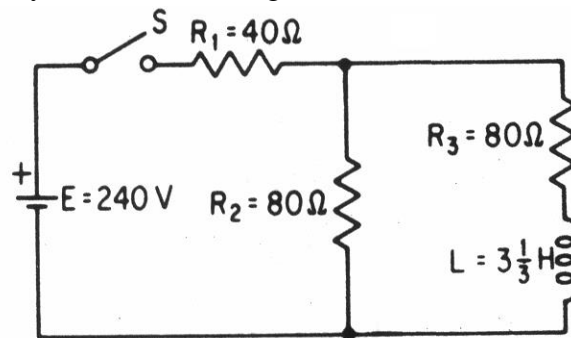


Figure 2

- Draw the per-phase equivalent circuit for the three phase circuit shown in Figure 3. If  $R = 6 \Omega$  and  $X = j24 \Omega$ , find
  - The current supplied by the source and the power factor
  - The total real and reactive powers drawn by the load
  - The voltage across  $R$  in Figure 3
  - The voltage across  $X$  in Figure 3

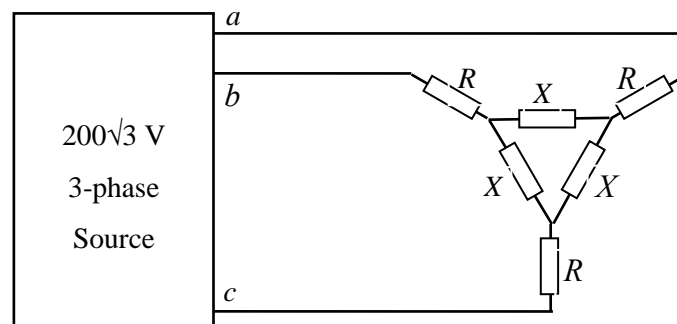


Figure 3